

# HW #4 Solutions

2X 5X

1/10X

	0.45 $\mu\text{m}$	0.90 $\mu\text{m}$	2.25 $\mu\text{m}$	4.5 $\mu\text{m}$
NMOS: $C_{GD} = 1.885 \text{ fF}/\mu\text{m} \cdot W$	0.366 fF	0.720 fF	1.8 fF	3.6 fF
$C_{db} = K_{eff} A_{db} C_j (K_{eff} 0.5 \text{ nm} \cdot W \cdot W \cdot W)$	$K_{eff} 0.225 \text{ fF}$	$K_{eff} 0.45 \text{ fF}$	$K_{eff} 1.125 \text{ fF}$	$K_{eff} 2.25 \text{ fF}$
$C_g = C_{ox} W L_n = \frac{C_{ox}}{0.025} (W)(L_n)$	0.704 fF	1.418 fF	3.544 fF	7.09 fF
$C_{dsW} = K_{psw} P_{sw} C_{jsw}$	$K_{psw} 0.348 \text{ fF}$	$K_{psw} 0.696 \text{ fF}$	$K_{psw} 1.74 \text{ fF}$	$K_{psw} 3.48 \text{ fF}$
$R_s = R_d = \frac{L}{W} \cdot R_{sh}$	2.8 $\Omega$	1.4 $\Omega$	0.56 $\Omega$	0.28 $\Omega$
PMOS: $C_{GD}$	0.292 fF	0.585 fF	1.463 fF	2.925 fF
$C_{db} = K_{eff} (0.5 \text{ nm} \cdot W \cdot W)$	$K_p 0.270 \text{ fF}$	$K_p 0.540 \text{ fF}$	$K_p 1.35 \text{ fF}$	$K_p 2.7 \text{ fF}$
$C_g = C_{ox} W_p L_p$	0.708 fF	1.418 fF	3.544 fF	7.09 fF
$C_{dsW} = K_{psw} P_{sw} C_{jsw}$	$K_{psw} 0.275 \text{ fF}$	$K_{psw} 0.55 \text{ fF}$	$K_{psw} 1.375 \text{ fF}$	$K_{psw} 2.75 \text{ fF}$
$R_s = R_d = \frac{L}{W} \cdot R_{sh}$	2.8 $\Omega$	1.4 $\Omega$	0.56 $\Omega$	0.28 $\Omega$

$$2) \dots -K_{eff} = \frac{-\beta_0^m}{(V_H - V_L)^{(1-m)}} \left[ (V_H - V_{in})^{1-m} - (V_H - V_{low})^{1-m} \right]$$

- $\square$  nmos:  $V_H = -1.5 \quad V_L = -0.9$   
 $K_{eff} = 0.696$   
 $K_{psw} = 0.863$
- $\square$  pmos:  $V_H = -1.5 \quad V_L = -0.9$   
 $K_{eff} = 0.849$   
 $K_{psw} = 0.869$
- $\square$  nmos:  $V_H = -1.5 \quad V_L = -0.9$   
 $K_{eff} = 0.678$   
 $K_{psw} = 0.717$
- $\square$  pmos:  $V_H = -0.9 \quad V_L = 0$   
 $K_{eff} = 0.847$   
 $K_{psw} = 0.934$

PMOS w/  $W = 1.0 \mu\text{m}$

$$C_{GD} = 0.649 \text{ fF}$$

$$C_{db} = K_{eff} 0.6 \text{ fF}$$

$$C_g = 1.5733 \text{ fF}$$

$$C_{dsW} = K_{psw} 0.38 \text{ fF}$$

$$\square \Rightarrow C = C_n + C_p = 1.144 + 3.546 = 5.49 \text{ fF}$$

$$\square \Rightarrow C = C_n + C_p = 1.885 + 3.71 = 5.596 \text{ fF}$$

$$\Delta t \approx C \frac{\Delta V}{I_{avg}}$$

$\Rightarrow$  Find average currents

- $\square \Rightarrow$  PMOS saturated  $\Rightarrow$  then linear  
 $\odot$   $I = K_p (V_{GT} - V_{min})^2 \frac{W}{L}$   
 $I = 36 \mu\text{A} (1.8 - 0.5)^2 \frac{1}{2} = 30.42 \mu\text{A} \left( \frac{1}{0.18} \right)$   
 $I = 36 \mu\text{A} (1.8 - 0.5)^2 \frac{1.25}{2} = 30.37 \mu\text{A} \left( \frac{1}{0.18} \right)$   
 $I_{avg} = 165.83 \mu\text{A}$
- $\square \Rightarrow$  NMOS saturated  $\Rightarrow$  then linear  
 $I = 180 \mu\text{A} (1.8 - 0.5)^2 \frac{0.4}{2} = 79.2 \mu\text{A} \left( \frac{0.15}{0.18} \right)$   
 $I_{avg} = 192 \mu\text{A}$

4231  
 10 SHEETS PER PLATE 5 SQUARE  
 10 SHEETS PER PLATE 5 SQUARE  
 200 SHEETS PER PLATE 5 SQUARE  
 4231  
 10 SHEETS PER PLATE 5 SQUARE  
 10 SHEETS PER PLATE 5 SQUARE  
 200 SHEETS PER PLATE 5 SQUARE  
 Mineral Brand

$$\tau_{p1n} \approx 5.49 \text{ fF} \left( \frac{0.9 \text{ V}}{168.83 \mu\text{A}} \right)$$

$$= 29.27 \text{ ps}$$

$$\tau_{p1p} \approx 5.576 \text{ fF} \left( \frac{0.9 \text{ V}}{192.26 \mu\text{A}} \right)$$

$$\approx 26.23 \text{ ps}$$

$V_M$ : Assume both transistors are in normal saturation:

$$\frac{1}{2} K_n \frac{W}{L} (V_{GS})^2 = \frac{1}{2} K_p \frac{W}{L} (V_{GS})^2$$

$$\frac{1}{2} (1.8 \times 10^{-4}) \frac{0.45}{0.14} (V_{in} - 0.5)^2 = \frac{1}{2} 3.6 \times 10^{-5} \left( \frac{1}{0.18} \right) (1.8 - V_{in} - 0.5)^2$$


$$450 (V_{in}^2 - V_{in} + 0.25) = 200 (V_{in}^2 - 2.6V_{in} + 1.69)$$

$\Rightarrow$  Solve quadratic for  $V_{in}$

$$\Rightarrow V_{in} = 0.82 \text{ V} = V_M$$

Ans:  $V_{min} = 0.82 - 0.5 = 0.32$ , so it is in normal saturation ✓

3

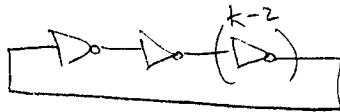

Schmidt Key

Problem 2 data

$$Y_{PL \rightarrow H} = 29.27 \text{ pS}$$

$$Y_{PH \rightarrow L} = 26.23 \text{ pS}$$

Assume 50% in gates & other low  
this this approx is valid

$$Y_p = \frac{Y_{PL \rightarrow H} + Y_{PH \rightarrow L}}{2}$$

Period =  $Y_p \cdot k \cdot 2$  ← you must wait for twice the number of stages to have the oscillator "settles" to the final period

$$\text{Period} = (55.5 \text{ pS}) \cdot k$$

$$f_0 = \frac{1}{\text{Period}} \Rightarrow f_0 = \frac{1.8018 \times 10^{10}}{k} \text{ Hz}$$

For one inverter

$$P = I_{avg} \cdot V$$

$$I_{avg} = \frac{I_{avg \rightarrow H} + I_{avg \rightarrow L}}{2} = \frac{168.83 \mu\text{A} + 12 \mu\text{A}}{2}$$

$$I_{avg} = 180.415 \mu\text{A}$$

$$P = (180.415 \mu\text{A}) \cdot (1.8 \text{ V})$$

$$P = 324.7 \mu\text{W}$$

$$\text{Power dissipation} = P \cdot k \Rightarrow P_{diss} = (324.7 \mu\text{W}) \cdot k$$

With too few inverters in the oscillator the circuit may not achieve full voltage swings and eventually stabilize to a non-oscillating state. One inverter will stabilize in the metastable state of VDD/2 constantly dissipating power.