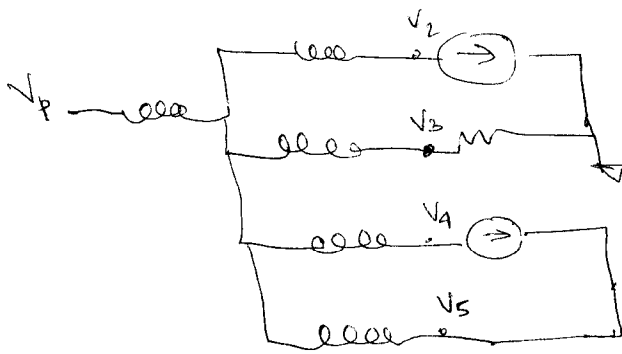


5.1)

HW-6 solution



$$V_2 = 2.5 - 10 \text{ mH} \times 2 \times \frac{1}{10 \text{ ns}} = 0.5 \text{ V}$$

$$I_A (\text{current through resistor}) = \frac{2.5}{10} = 0.25 \text{ initially}$$

$$= \frac{1.5}{10} = 0.15 \text{ after } I_1 \text{ is switched.}$$


$$V_3 = 1.5 - 10 \times \frac{0.1}{10} = 1.4 \text{ V}$$

$$V_4 = 1.5 - 10 \times \frac{1}{10} = 0.5$$

$$V_5 = 1.5 + 10 \times \frac{1}{10} = 2.5$$


When they are connected
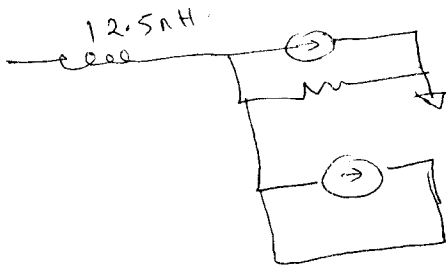
$$\frac{1}{L} = \frac{1}{10} + \frac{1}{10} + \frac{1}{10} + \frac{1}{10} \Rightarrow L = 2.5 \text{ nH.}$$



$$V_2 = V_3 = 2.5 - 12.5 \times \frac{1}{10} = 1.25.$$

$$V_4 = V_5 = V_2$$

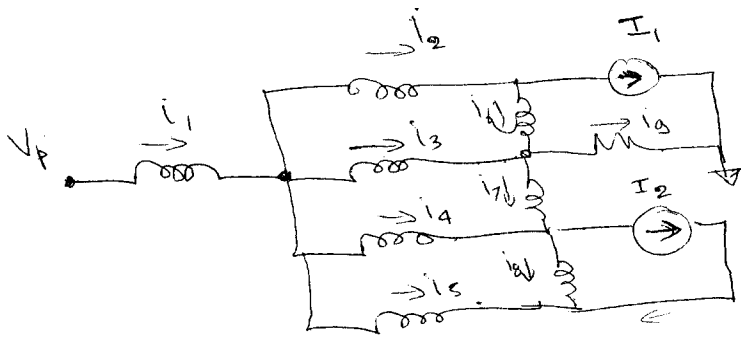

$$i_1 = i_2 + i_3 + i_4 + i_5$$

$$i_2 = i_6 + I_1$$

$$i_3 + i_6 = i_7 + i_8$$

$$i_4 + i_7 = I_2 + i_8$$

$$i_5 + i_8 - I_2 = 0$$

$$L = 60 \text{ mH}$$

$$L' = 5 \text{ mH}$$

$$V_p - L \frac{di_1}{dt} - L \frac{di_3}{dt} = i_6 R$$



$$V_p - L \frac{di_1}{dt} - L \frac{di_4}{dt} - L' \frac{di_8}{dt} = V_p - L \frac{di_1}{dt} - L \frac{di_5}{dt}$$

$$V_p - L \frac{di_1}{dt} - L \frac{di_2}{dt} - L' \frac{di_6}{dt} = i_7 R$$

$$V_p - L \frac{di_1}{dt} - L \frac{di_4}{dt} = i_8 R - L' \frac{di_7}{dt}$$

9 equations \Rightarrow 9 unknowns, solve to get currents and voltages at V_2, V_3, V_4, V_5

B.2

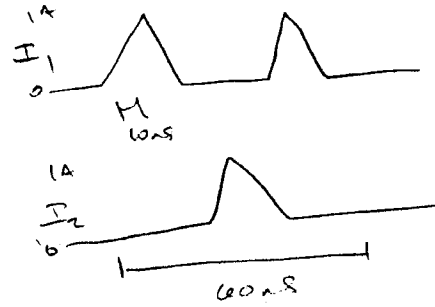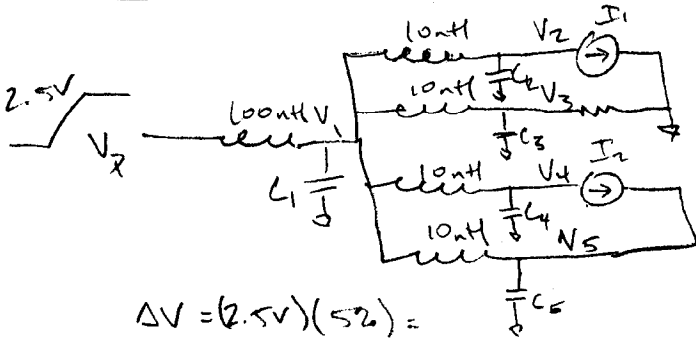

$$\Delta V = (2.5V)(5\%) = 0.125V$$

$$C > L \left(\frac{I_{avg}}{\Delta V} \right)^2$$

$$C_{B1} > 100nH \left(\frac{0.5A}{0.125V} \right)^2$$

$$C_{B1} = 1.6 \mu F$$

$$C_{B2,3} > 10nH \left(\frac{0.334A}{0.125V} \right)^2$$

$$C_{B2,3} = 71.1 nF$$

$$C_{B4,5} > 10nH \left(\frac{0.167A}{0.125V} \right)^2$$

$$C_{B4,5} = 17.8 nF$$

$$I_{avg} = (\# \text{ Transfers}) \cdot (\text{Area of triangle}) / \Delta T$$

$$= 3 \cdot \frac{1}{2} \cdot 20ns \cdot 1A / 60ns$$

$$I_{avg1} = 0.5A$$

$$I_{avg} V_{2,3} = 2 \cdot \frac{1}{2} \cdot 20ns \cdot 1A / 60ns = 0.334A$$

$$I_{avg} V_{3,4} = 1 \cdot \frac{1}{2} \cdot 20ns \cdot 1A / 60ns = 0.167A$$

5.11



~~secret~~
Key

(A)


Assume gate with parameters

$$V = 2.5V$$

$$I_{avg} = 1.3mA$$

$$I_{peak} = 1.4mA$$

$$T = 200pS$$

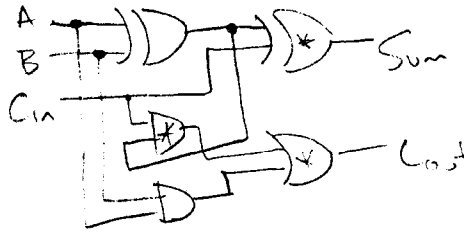


$$T_p = C_{out} = 3 \text{ gate delays} = 600pS$$

Worst case delay



$$C_{out} \text{ delay} (\# \text{ cells}) \Rightarrow (600pS)(32) = 19.2nS$$

$$I_{avg} = (3 \text{ gates}) (1.4mA) = ~~2.8mA~~ 4.2mA$$
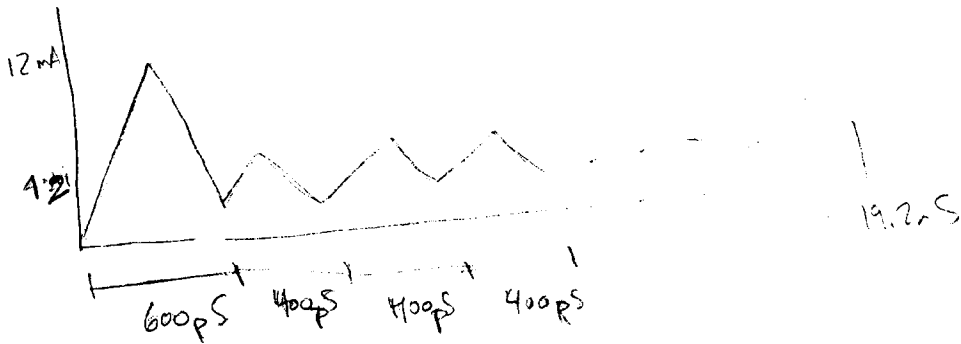
$$I_{peak} = (5 \text{ gates}) (1.4mA) = 12mA$$



5.12

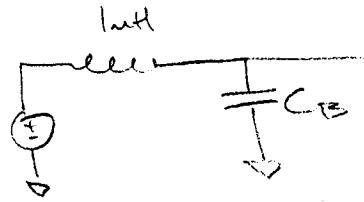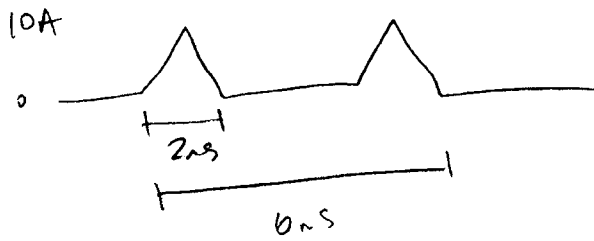

Assume 2.5V

$$\Delta V = (2.5V)(5\%) = 0.125V$$

$$f = \frac{1}{T} = 167 \text{ MHz}$$

$$I_{\text{avg}} = \frac{\frac{1}{2} \cdot 2\text{ns} \cdot 10\text{A}}{6\text{ns}} = 1.67 \text{ A}$$

$$C_B > \frac{I_{\text{avg}}}{\Delta V} \left(k_i t_{ck} + \frac{L \cdot I_{\text{avg}}}{\Delta V} \right) \quad k_i = \frac{1}{4} \text{ for triangle wave}$$

$$C_B = \frac{1.67\text{A}}{0.125\text{V}} \left(0.25 \cdot 6\text{ns} + \frac{1\mu\text{H} \cdot 1.67\text{A}}{0.125\text{V}} \right) = 179 \mu\text{F}$$

SMT

$$C > \frac{k_i \cdot I_{\text{avg}} t_{ck}}{\Delta V} = \frac{\frac{1}{2} \cdot 1.67 \cdot 6\text{ns}}{0.125} = 40 \text{ nF}$$

Use 40 - 1nF, 0.1Ω, 1nH SMT at 160MHz

Aluminum Electrolytic

$$C > L \left(\frac{I_{\text{avg}}}{\Delta V} \right)^2 = 1\mu\text{H} \left(\frac{1.67\text{A}}{0.125} \right)^2 = 178 \mu\text{F}$$

Use 18 - 10μF, 1Ω, 10nH at 160kHz & 16MHz

5.13

15mm x 15mm with 1M gates $\sim 4444 \text{ gates/mm}^2$
100 MHz = 60ns period

Switches every 30ns this
for gates for period



$$f = \frac{1}{60\text{ns}} = 16.7 \text{ MHz}$$

$$P = (C V \Delta V f)$$

$$= (200\text{fF})(2.5)(2.5)(16.7\text{MHz})$$

$$P_{\text{gate}} = 20.8 \mu\text{W}$$

$$P_{\text{chip}} = P_{\text{gate}} \times 1 \times 10^6$$

$$P_{\text{chip}} = 20.8 \text{ W}$$

fraction of metal devoted to gates
but for one polarity

$$V_{\text{IR}} = \frac{J_{\text{pk}} \cdot r_w \cdot L_p^2}{8 \cdot k_p} \Rightarrow k_p = \frac{J_{\text{pk}} \cdot r_w \cdot L_p^2}{8 \cdot V_{\text{IR}}}$$

$$\frac{I_{\text{peak}}}{I_{\text{avg}}} = 4$$

$$V_{\text{IR}} = 10\% \cdot 2.5\text{V} = 250\text{mV}$$

Assume $r_w = 40 \text{ m}\Omega/\text{square}$ - thin thick alum wire

$$L_p = 15\text{mm}$$

From book pg 241

$$P = \pm V$$

$$I_{\text{gate}} = \frac{P_{\text{gate}}}{V} = \frac{20.8 \mu\text{W}}{2.5\text{V}} = 8.4 \mu\text{A}$$

$$I_{\text{avg}} = 8.4 \mu\text{A} / \text{gate}$$

$$I_{\text{peak}} = 8.4 \mu\text{A} \cdot 4 = 33.6 \mu\text{A} / \text{gate}$$

$$J_{\text{pk}} = (4444 \text{ gates/mm}^2)(33.6 \mu\text{A/gate})$$

$$J_{\text{pk}} = 148 \text{ mA/mm}^2$$

$$k_p = \frac{(148 \text{ mA/mm}^2)(40 \text{ m}\Omega/\text{sq})(15\text{mm})^2}{(8)(250\text{mV})}$$

$$k_p = 0.668$$


thus you need

$$1.34 \text{ metal layers}$$

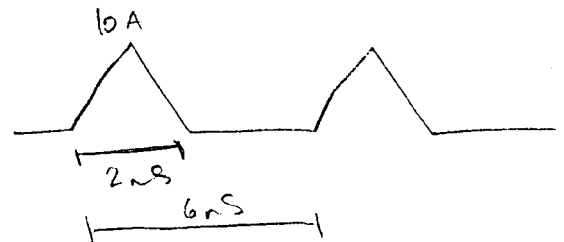5.15

sup -

$$C > L \left(\frac{I_{avg}}{\Delta V} \right)^2 = \frac{k_i Q_{ck}}{\Delta V}$$



$$I_{avg} = \frac{Q_{ck}}{T} = \frac{\frac{1}{2} \cdot 10A \cdot 2ns}{6ns} = 1.67A$$

$$C_{B1} > \frac{(0.25) \left(\frac{1}{2} \cdot 10A \cdot 2ns \right)}{0.25V} \Rightarrow 10nF \text{ on chip}$$

$$C_{B2} > 100nF \left(\frac{1.67A}{0.25} \right)^2 \Rightarrow 4.4mF$$

$$C_{B_{total}} = 4.4mF + 10nF = 4.4mF$$

Much too large to bypass
using on chip capacitors

$$7) a) i = \frac{2.5}{60 \text{ s}} = 40 \text{ mA}$$

$$\text{total current } I = 80 \times 40 \text{ mA} = 3.2 \text{ A}$$

$$\left. \frac{dI}{dt} \right|_{\text{worst}} = \frac{3.2 \text{ A}}{1 \text{ ns}} = 3.2 \text{ A/ns}$$

$$b) L \frac{dI}{dt} = 0.25$$

$$L = \frac{0.25}{3.2} = 0.078 \text{ nH}$$

$$\text{no of bumps} = \frac{0.078}{0.5} = 0.156$$

$$c) \text{ avg power} = \frac{0.15 T \times VI}{T}$$

$$= 0.15 V I$$

$$= 1.2 \text{ Watts}$$