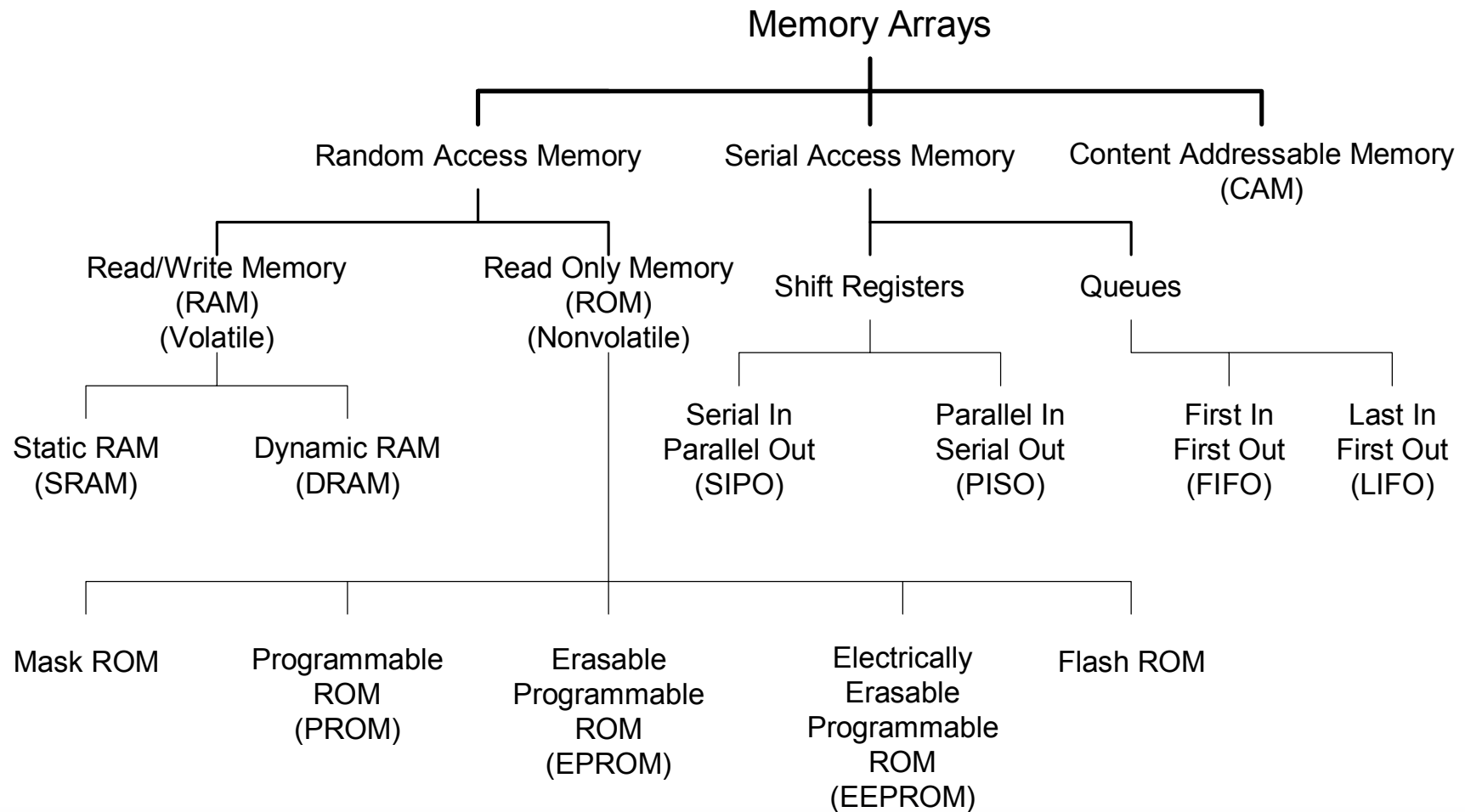


Array Structured Memories

STMicro/Intel
UCSD CAD LAB
Weste Text


Memory Arrays



Feature Comparison Between Memory Types


Memory Type	SRAM	DRAM	Flash
Speed	Very fast	Fast	Very slow
Density	Low	High	Very high
Endurance	Better	Better	Poor
Power	Low	High	Very low
Refresh	No	Yes	No
Retention	Volatile	Volatile	Non-volatile
Scalable	Good	Bad	Good
Mechanism	Bi-stable latch	Capacitor	FN tunneling, HCI

The Memory Hierarchy

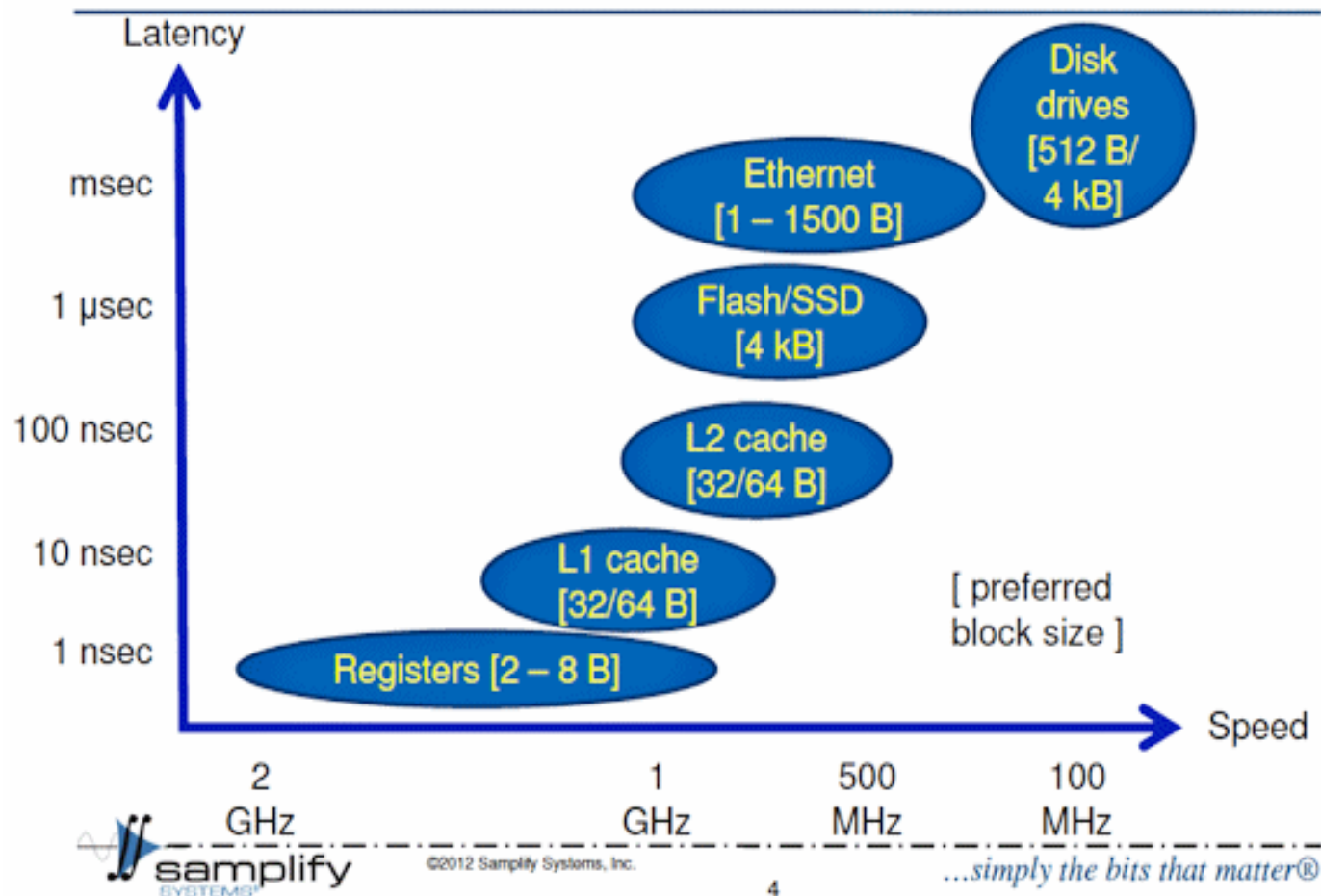

Array Architecture

 
- 2^n words of 2^m bits each
- If $n \gg m$, fold by 2^k into fewer rows of more columns




- Good regularity – easy to design
- Very high density if good cells are used

Memory - Real Organization

Array of $N \times K$ words

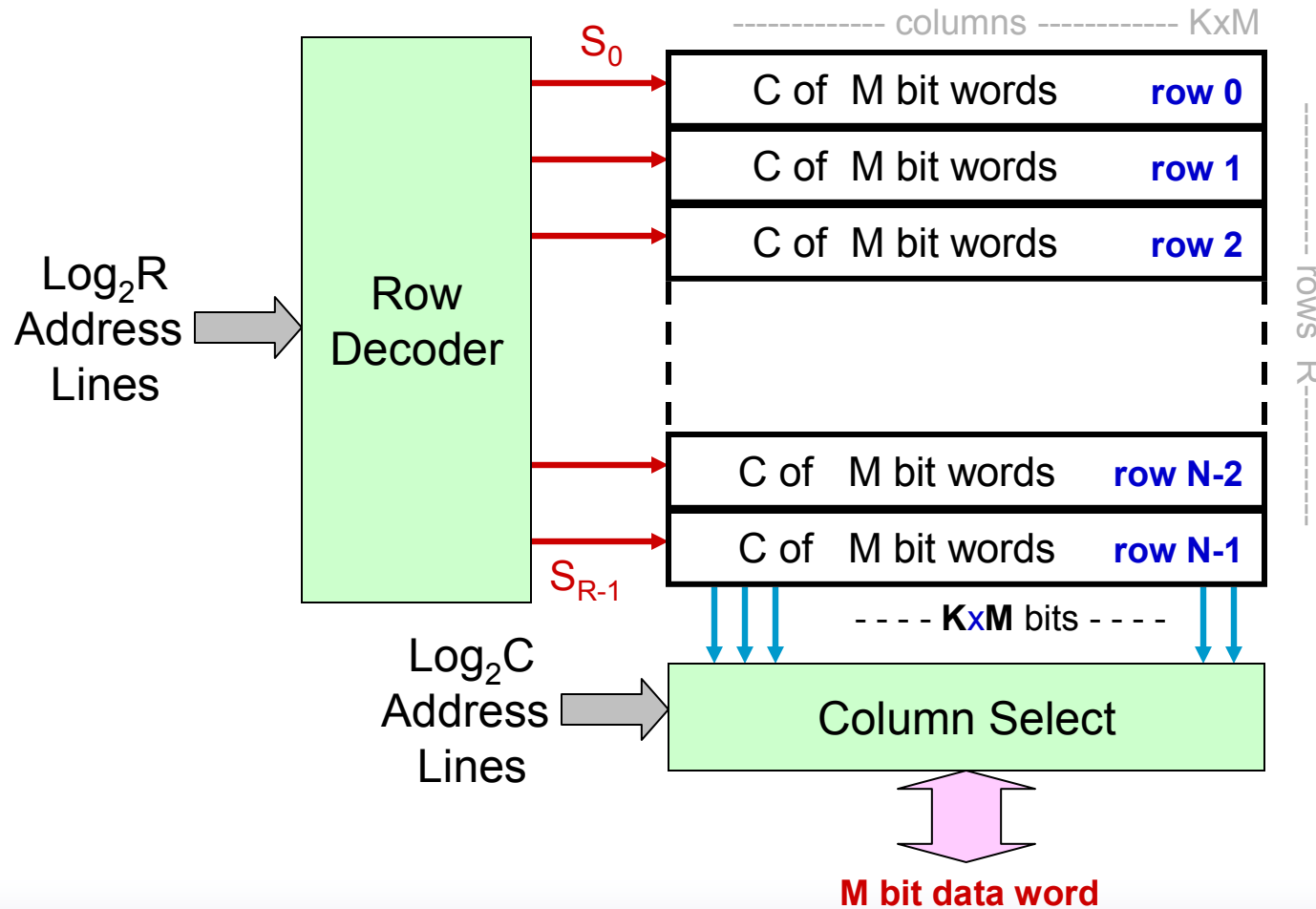

Hierarchical Memory Architecture

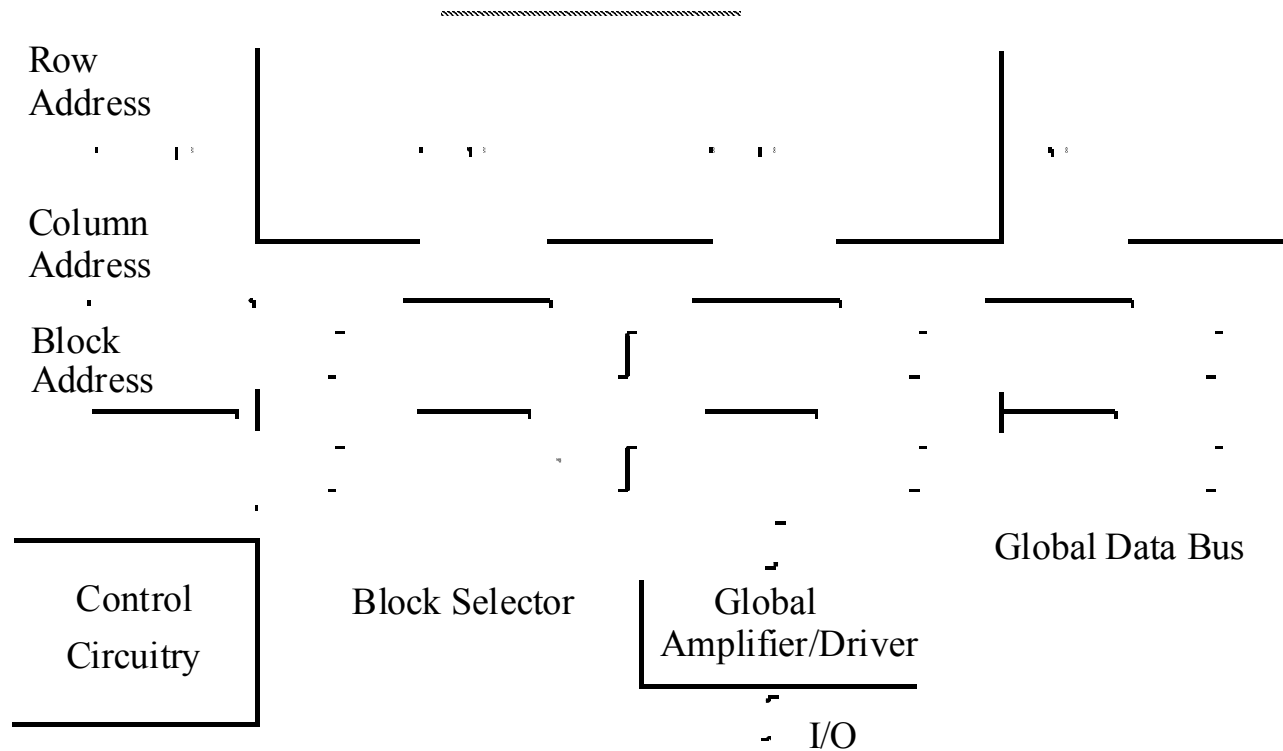


Advantages:

1. Shorter wires within blocks
2. Block address activates only 1 block => power savings

Array Organization Design Issues

- **aspect ratio should be relative square**
 - **Row / Column organisation (matrix)**
 - **$R = \log_2(N_{\text{rows}})$; $C = \log_2(N_{\text{columns}})$**
 - **$R + C = N$ ($N_{\text{address_bits}}$)**
- **number of rows should be power of 2**
 - **number of bits in a row need not be...**
- **sense amplifiers to speed voltage swing**
- **1 -> 2^R row decoder**
- **1 -> 2^C column decoder**
 - **M column decoders (M bits, one per bit)**
 - **M = output word width**


Simple 4x4 SRAM Memory

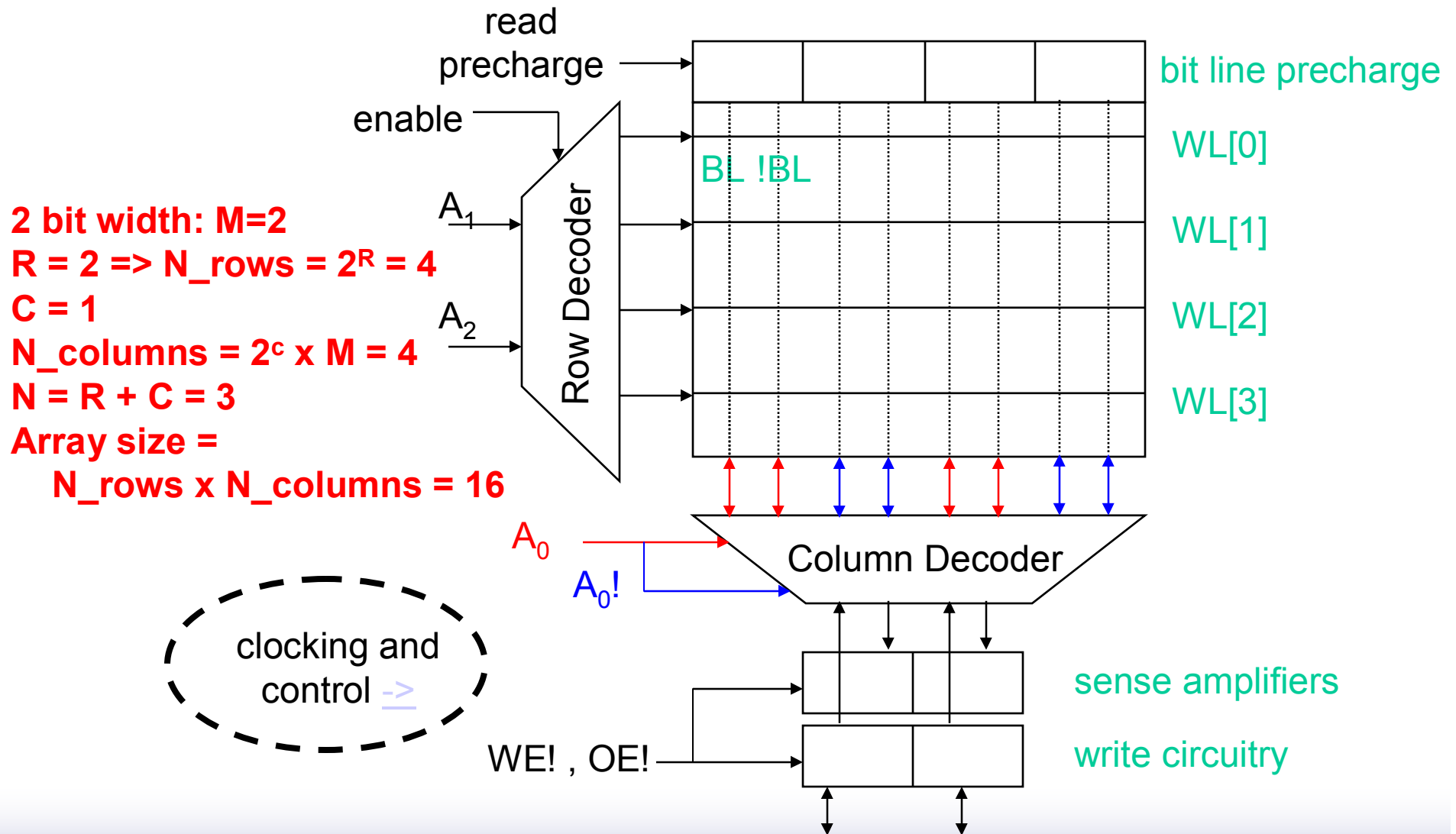



SRAM Read Timing (typical)

- ❑ **t_{AA} (access time for address):** time for stable output after a change in address.
- ❑ **t_{ACS} (access time for chip select):** time for stable output after CS is asserted.
- ❑ **t_{OE} (output enable time):** time for low impedance when OE and CS are both asserted.
- ❑ **t_{OZ} (output-disable time):** time to high-impedance state when OE or CS are negated.
- ❑ **t_{OH} (output-hold time):** time data remains valid after a change to the address inputs.

SRAM Read Timing (typical)

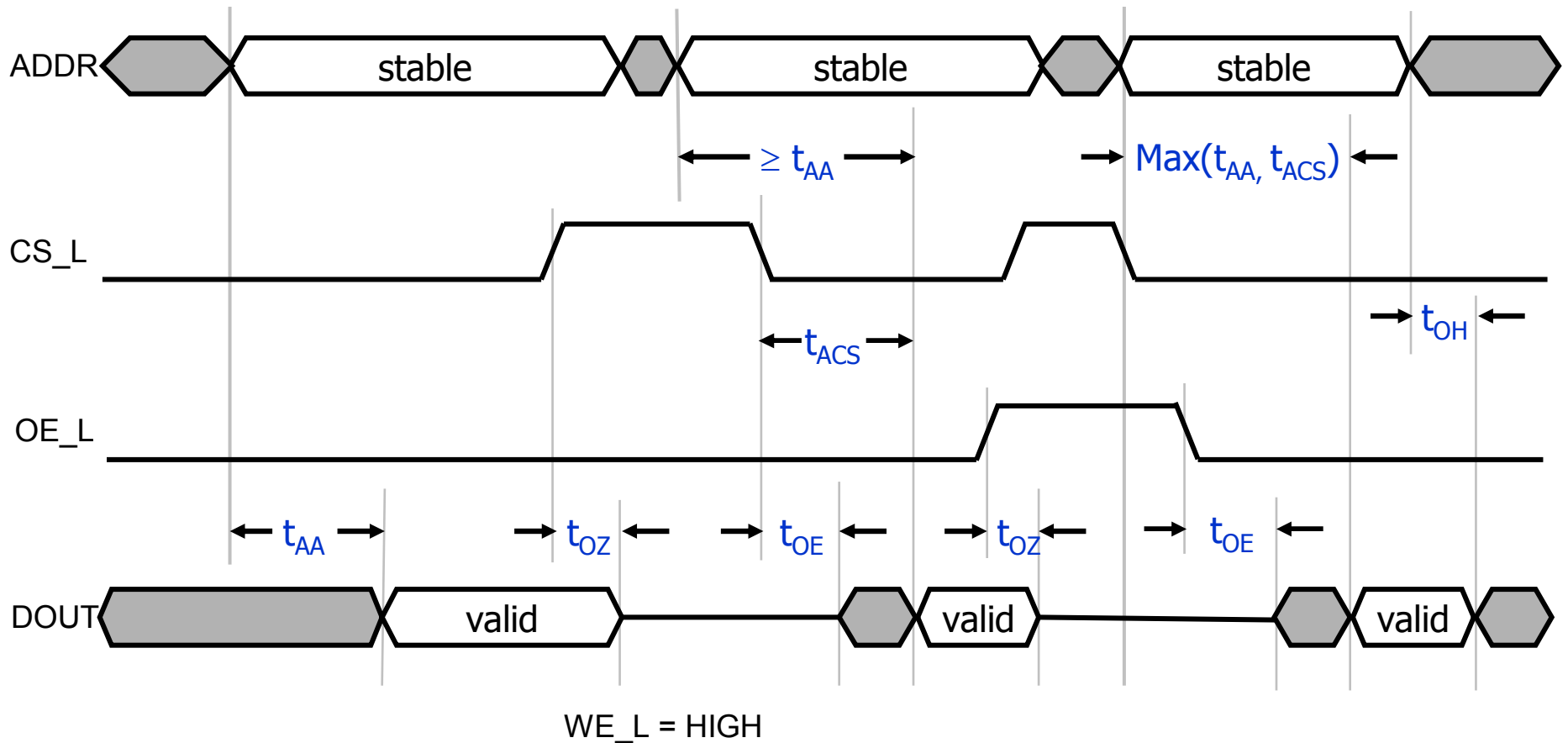


SRAM write cycle timing

 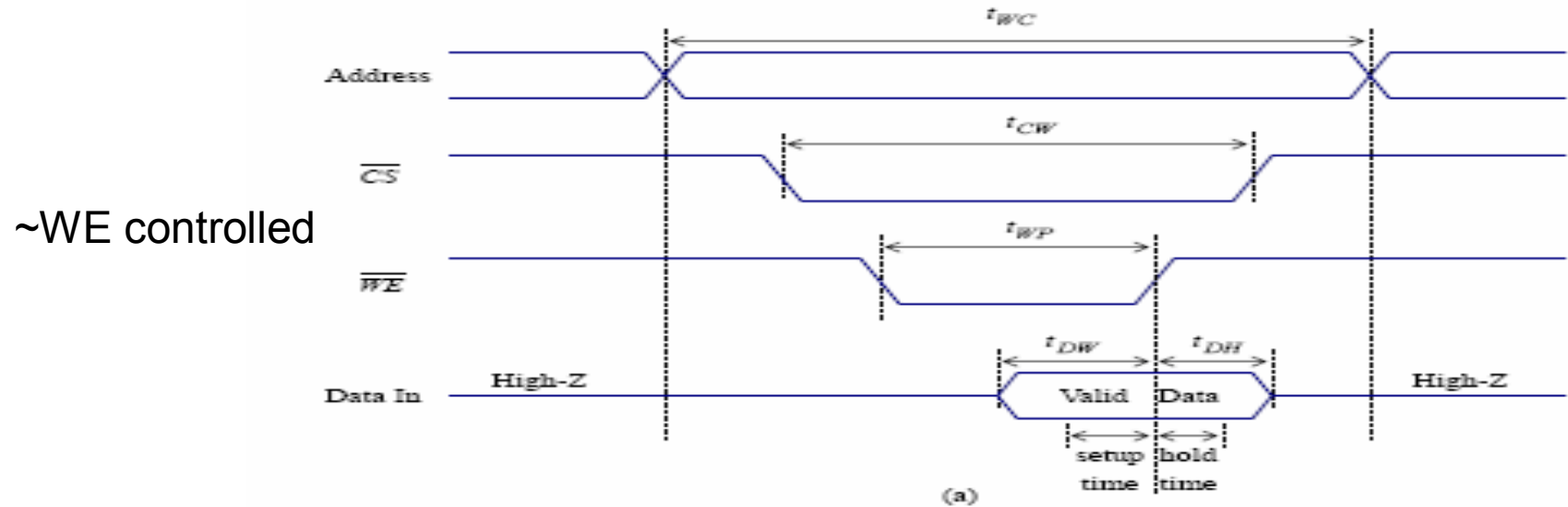


SRAM Cell Design

- Memory arrays are large
 - Need to optimize cell design for area and performance
 - Peripheral circuits can be complex
 - 60-80% area in array, 20-40% in periphery
- Classical Memory cell design
 - 6T cell full CMOS
 - 4T cell with high resistance poly load
 - TFT load cell

Anatomy of the SRAM Cell

 

Stable Configurations

 

Terminology:

bit line: carries data
word line: used for addressing


Write:

- set bit lines to new data value
 - $b' = \sim b$
- raise word line to “high”
 - sets cell to new state
 - Low impedance bit-lines


Read:

- set bit lines high
- set word line high
- see which bit line goes low
- High impedance bit lines



SRAM Cell Operating Principle

 

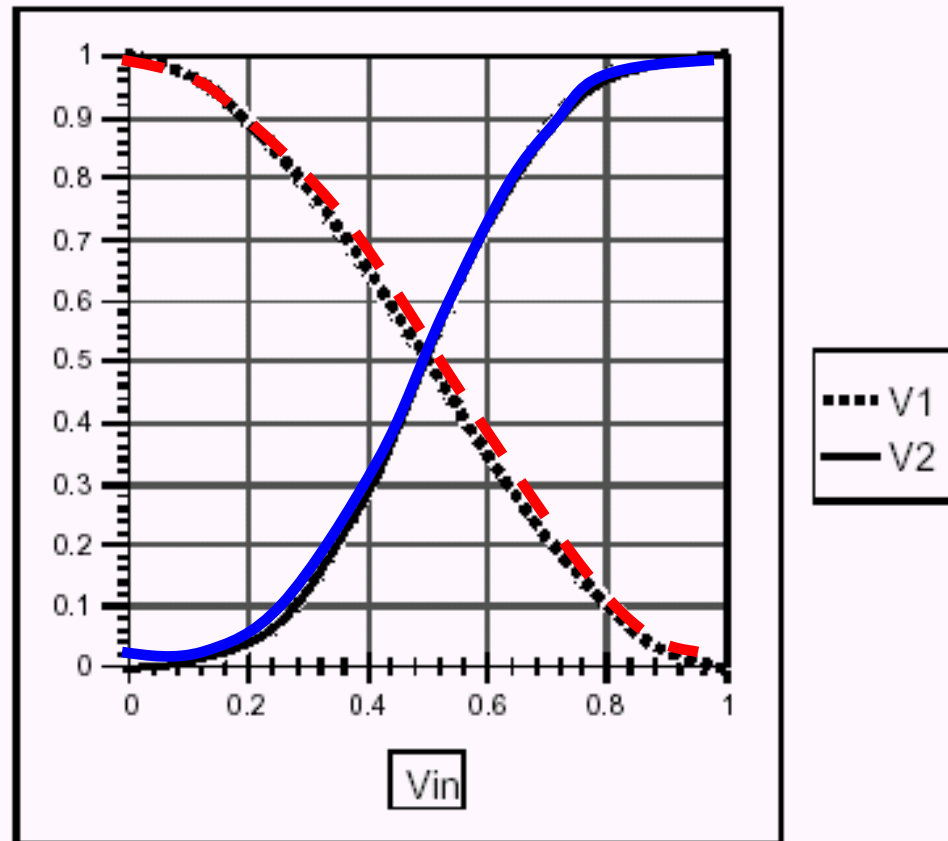- **Inverter Amplifies**
 - Negative gain
 - Slope < -1 in middle
 - Saturates at ends
- **Inverter Pair Amplifies**
 - Positive gain
 - Slope > 1 in middle
 - Saturates at ends




Bistable Element

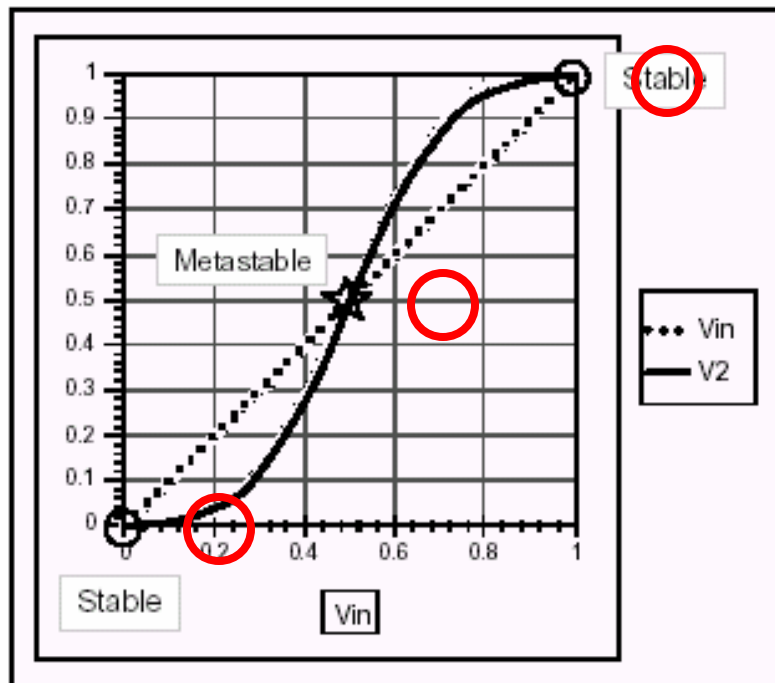 

Stability

 - Require $V_{in} = V_2$
- Stable at endpoints
recover from perturbation
- Metastable in middle
Fall out when perturbed



Ball on Ramp Analogy

Cell Static Noise Margin


Cell state may be disturbed by

•DC

- Layout pattern offset
- Process mismatches
 - non-uniformity of implantation
 - gate pattern size errors

•AC

 - Alpha particles
- Crosstalk
- Voltage supply ripple
- Thermal noise




V_n : Static Noise Source

SNM (static noise margin)
= Maximum Value of V_n
not flipping cell state


SNM: Butterfly Curves

V_{O1}, V_{I2}
 V_{O1}, V_{I2}

 

SNM for Poly Load Cell

 - Q1, Q2, Q3 : Saturation Region
- Q4 : Linear Region





Results

$$\text{SNM } (V_{n(\text{MAX})}) = \frac{\sqrt{\gamma} - 1}{\sqrt{\gamma} + 1} V_{\text{th}} + \frac{\gamma + 1 - \sqrt{2\gamma^3 + \gamma + 1}}{\gamma(\sqrt{\gamma} + 1)} (V_{\text{dd}} - V_{\text{th}})$$

where γ (Cell Ratio) = β_d / β_a


12T SRAM Cell

 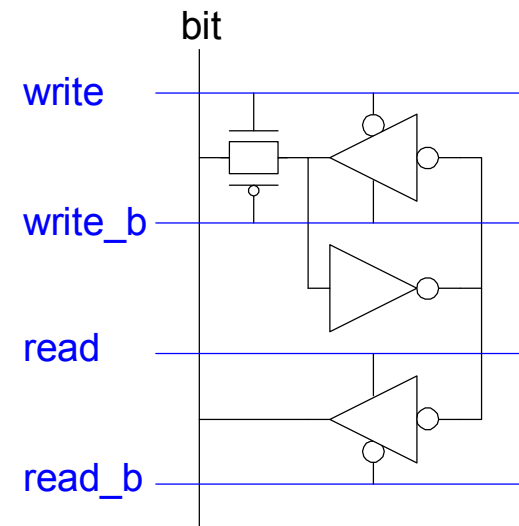- **Basic building block: SRAM Cell**
 - **1-bit/cell (noise margin again)**
- **12-transistor (12T) SRAM cell**
 - **Latch with TM-gate write**
 - **Separately buffered read**




6T SRAM Cell

 
- ❑ Cell size accounts for most of array size
 - Reduce cell size at cost of complexity/margins
- ❑ 6T SRAM Cell
- ❑ Read:
 - Precharge bit, bit_b
 - Raise wordline
- ❑ Write:
 - Drive data onto bit, bit_b
 - Raise wordline




SRAM Design

 

TI 65nm:
0.46x1.06 μm^2

 


IBM 65nm:
0.41x1.25 μm^2

 


Intel 65nm:
0.46x1.24 μm^2

* Figures courtesy A. Chatterjee et al., P. Bai et al., and Z. Luo et al.,
Int. Electron Device Meeting Tech. Digest, 2004


Vertical 6T Cell Layout

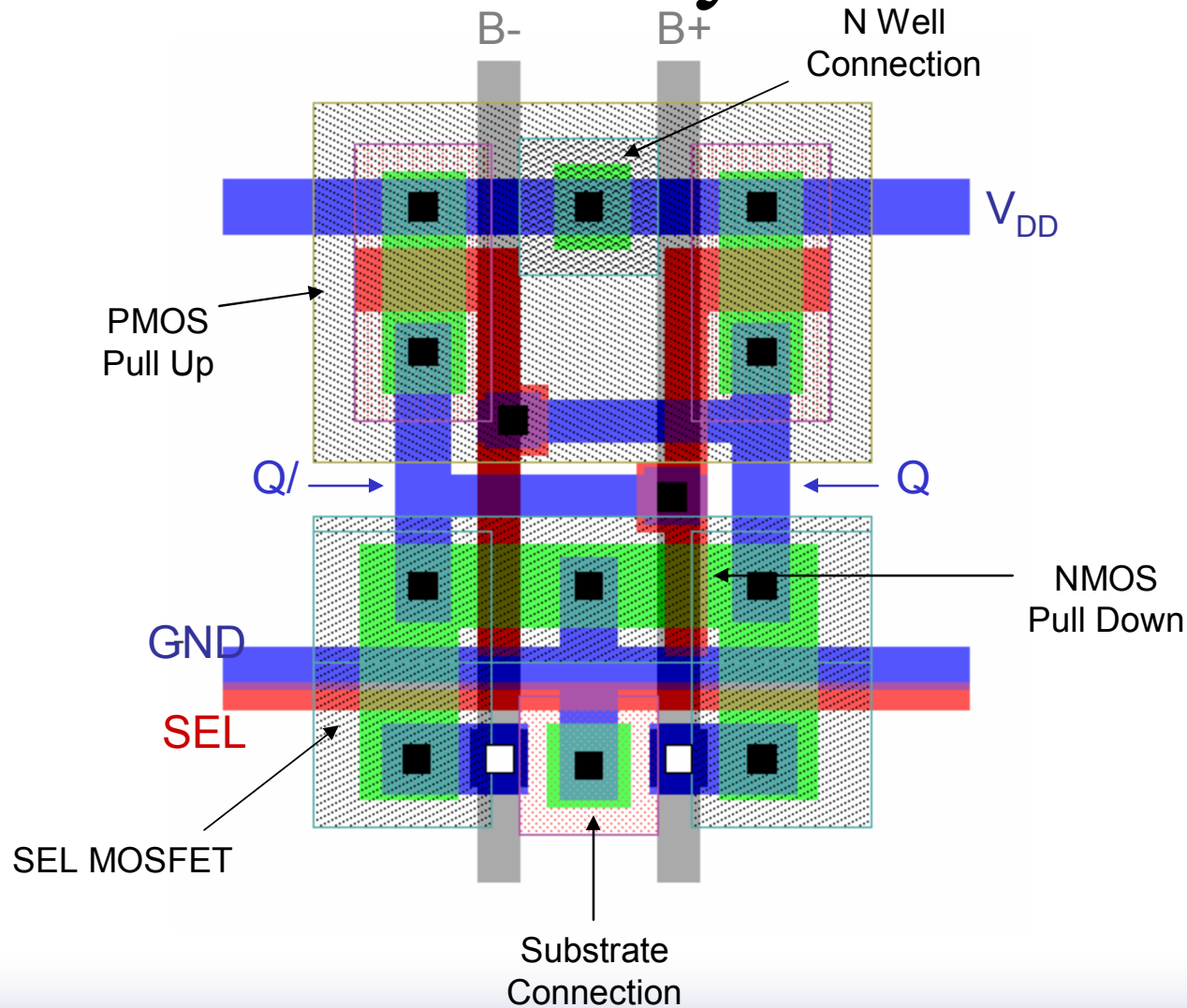


6T SRAM Array Layout

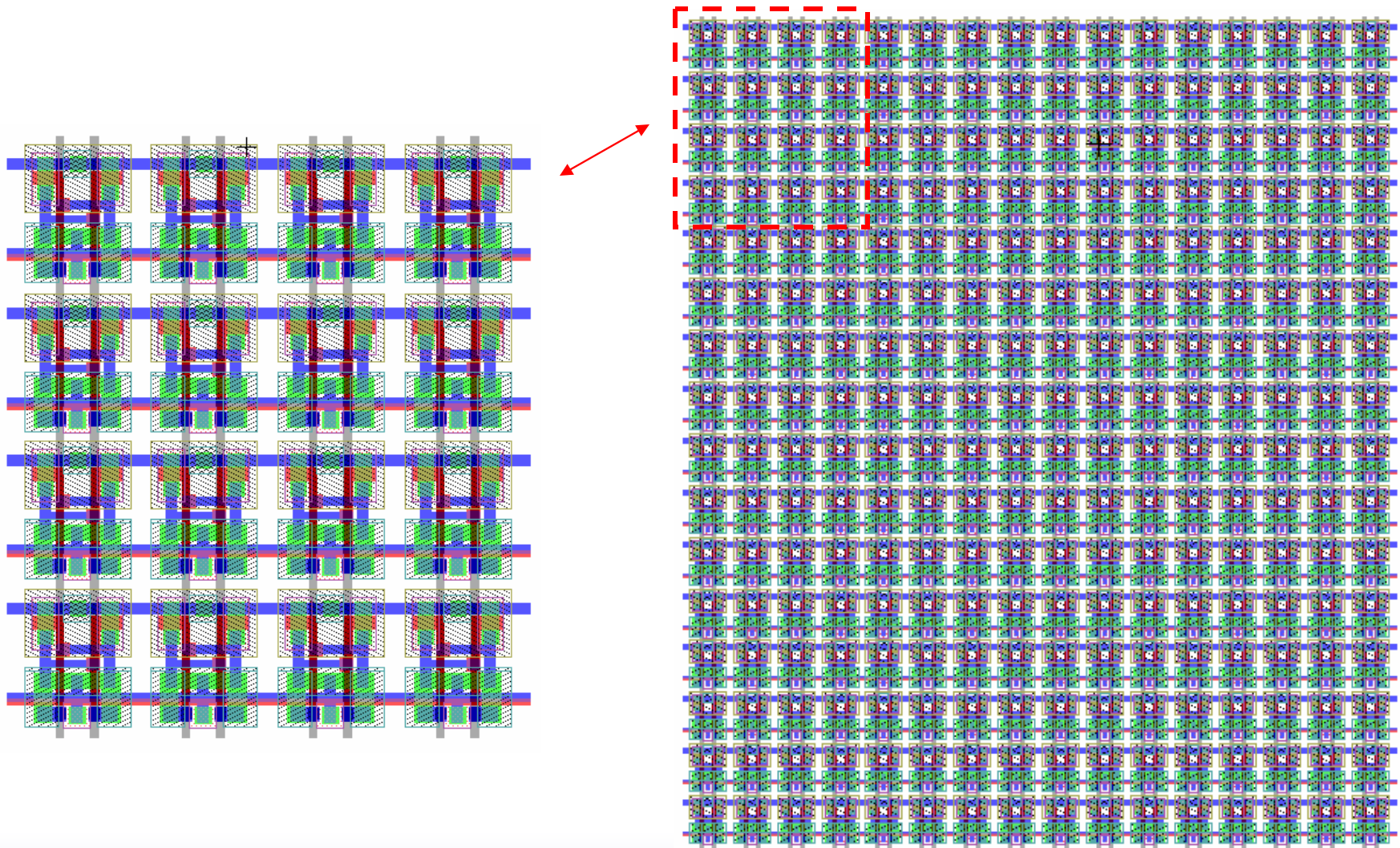


SRAM Bitcell Design

 

Schematic

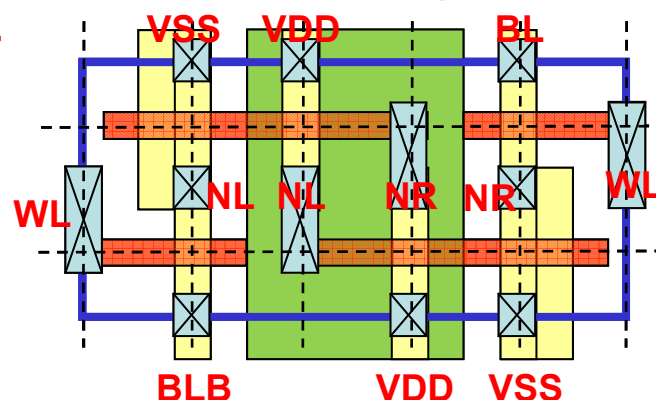

Layout

 

Micrograph


□ Requirements of SRAM bitcell design

- **Stable read operation:** Do not disturb data when reading
- **Stable write operation:** Must write data within a specified time
- **Stable data retention:** Data should not be lost

□ Typical transistor sizing

- Cell ratio ($= I(\text{PD}) / I(\text{PG}) = 1.5 \sim 2.5$)
- Pull-up ratio ($= I(\text{PU}) / I(\text{PG}) = 0.5$)


Bitcell Assembly

 


STMicro/Intel/UCSD/THNU

Memory

Bitcell Array

 


Detailed SRAM Bitcell Layout

 


- Vertical: 2 poly pitch
- Horizontal: 5 contact pitch
- Poly-to-contact space > overlay + spacer + strain_layer + CD_control
 $(6.4\text{nm}^*) (\approx 8\text{nm}^{**}) (\approx 10\text{nm}^{**}) (\approx 2.6\text{nm}^*) = 27\text{nm}$
- **1 poly pitch** = 2 poly_to_contact + poly_width + contact_width
 $\approx 54 + 32 + 45^{**} = 131\text{ nm}$


 
A pitch is a multiple of a **drawing grid** for fine-grain pattern placement



SRAM Read

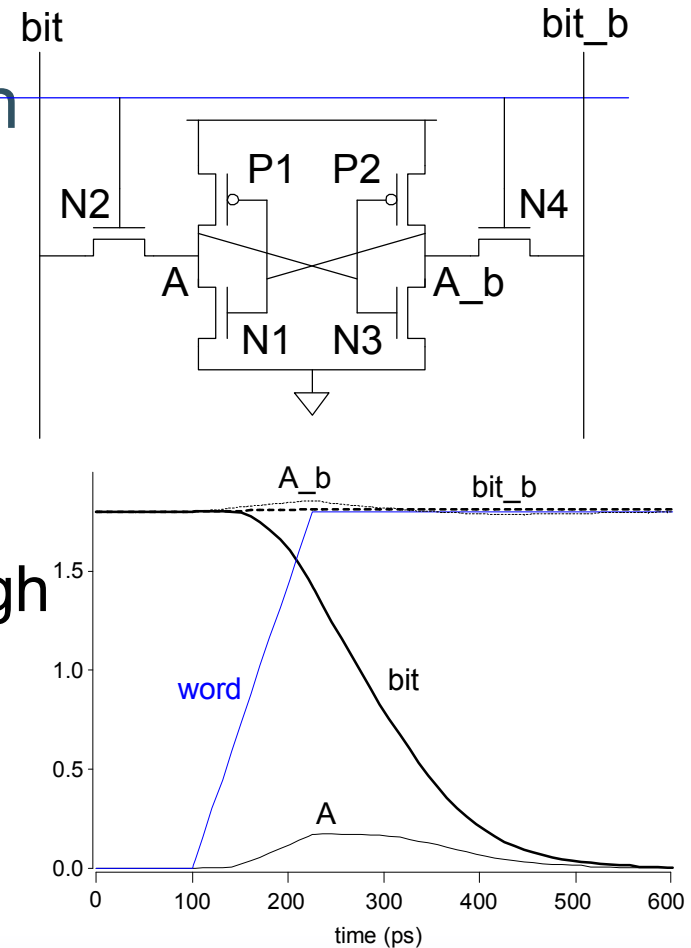- Precharge both bitlines high
- Then turn on wordline
- One of the two bitlines will
 - be pulled down by the cell
- Ex: $A = 0, A_b = 1$
 - bit discharges, bit_b stays high
 - But A bumps up slightly
- *Read stability*
 - A must not flip
 - $N1 \gg N2$





 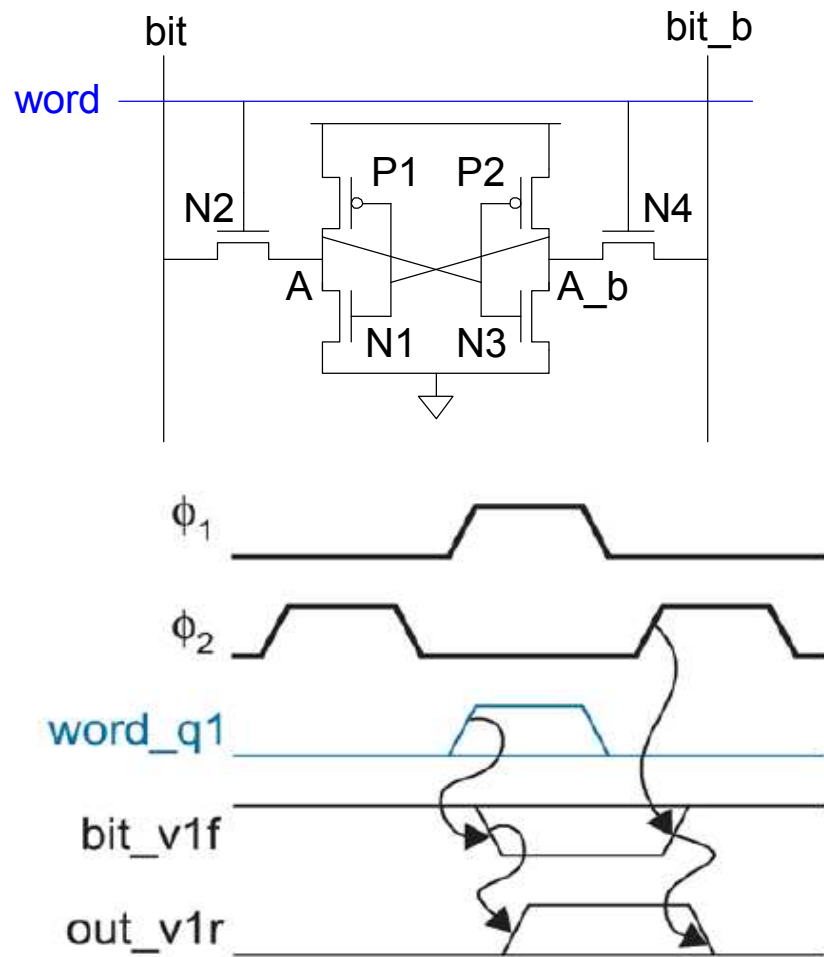

SRAM Read, 0 is stored in the cell


SRAM Write

 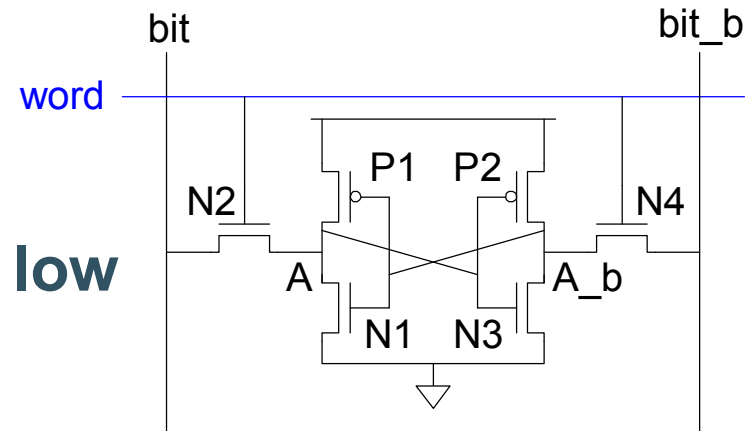- Drive one bitline high, other low
- Then turn on wordline
- Bitlines overpower cell
- Ex: $A = 0$, $A_b = 1$, $\text{bit} = 1$, $\text{bit}_b = 0$
 - Force A_b low, then A rises high
- *Writability*
 - Must overpower feedback
 - $P2 \ll N4$ to force A_b low,
 - $N1$ turns off, $P1$ turns on,
 - raise A high as desired




SRAM Sizing

 - High bitlines must not overpower inverters during reads
- But low bitlines must write new value into cell




SRAM Column Example

read

 


write

 


Decoders

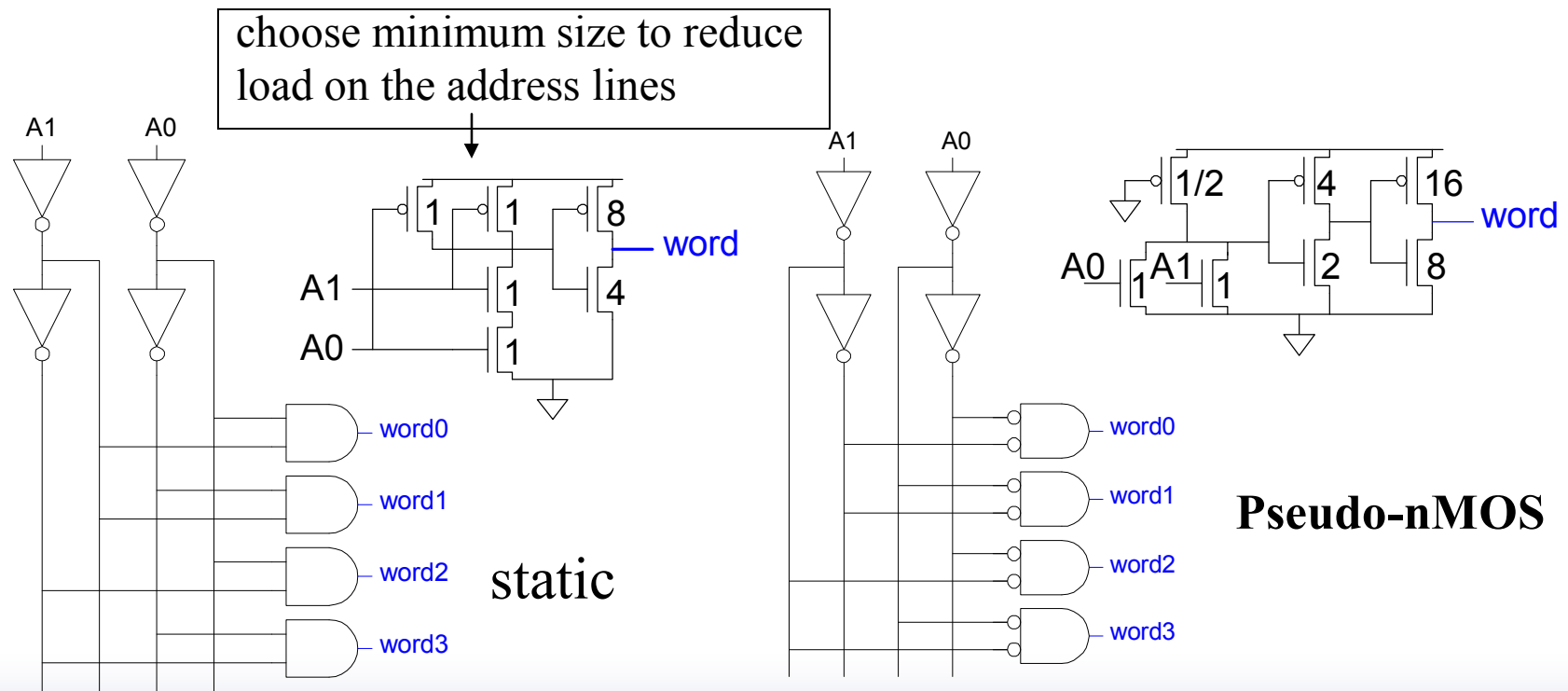- $n:2^n$ decoder consists of 2^n n -input AND gates
 - One needed for each row of memory
 - Build AND from NAND or NOR gate




Single Pass-Gate Mux

 

bitlines propagate
through 1 transistor


Decoder Layout

 - Decoders must be pitch-matched to SRAM cell
 - Requires very skinny gates



Large Decoders

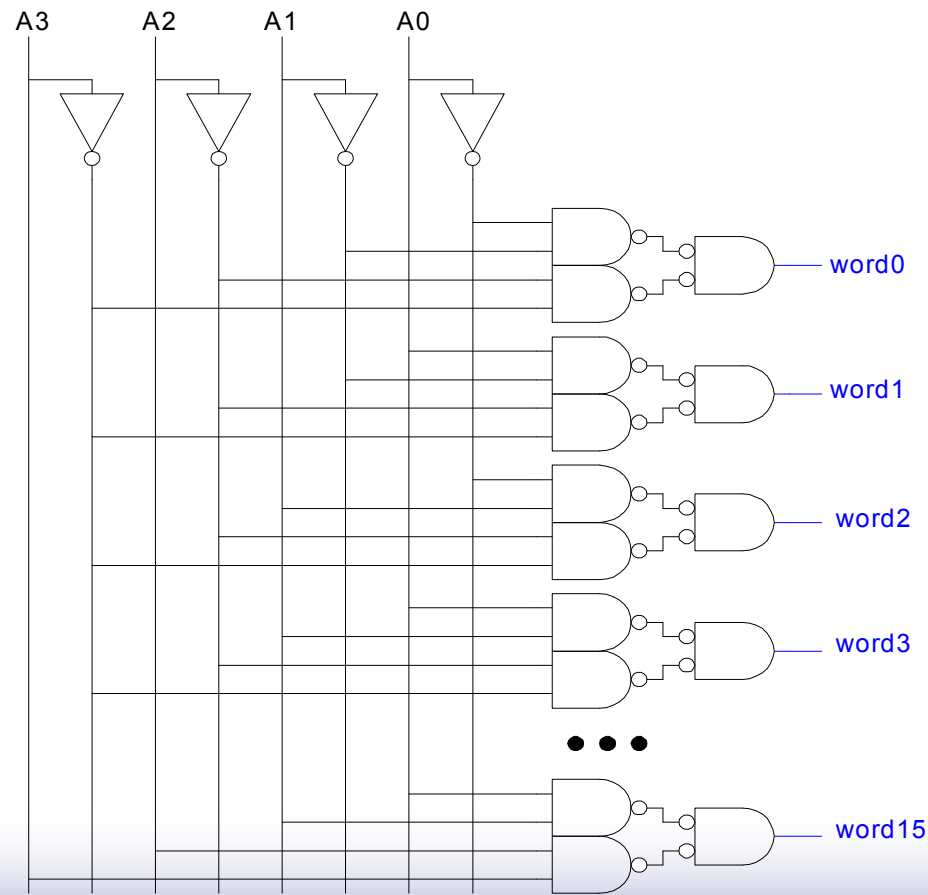
- For $n > 4$, NAND gates become slow
 - Break large gates into multiple smaller gates



Predecoding

□ Many of these gates are redundant

- Factor out common gates into predecoder
- Saves area
- Same path effort

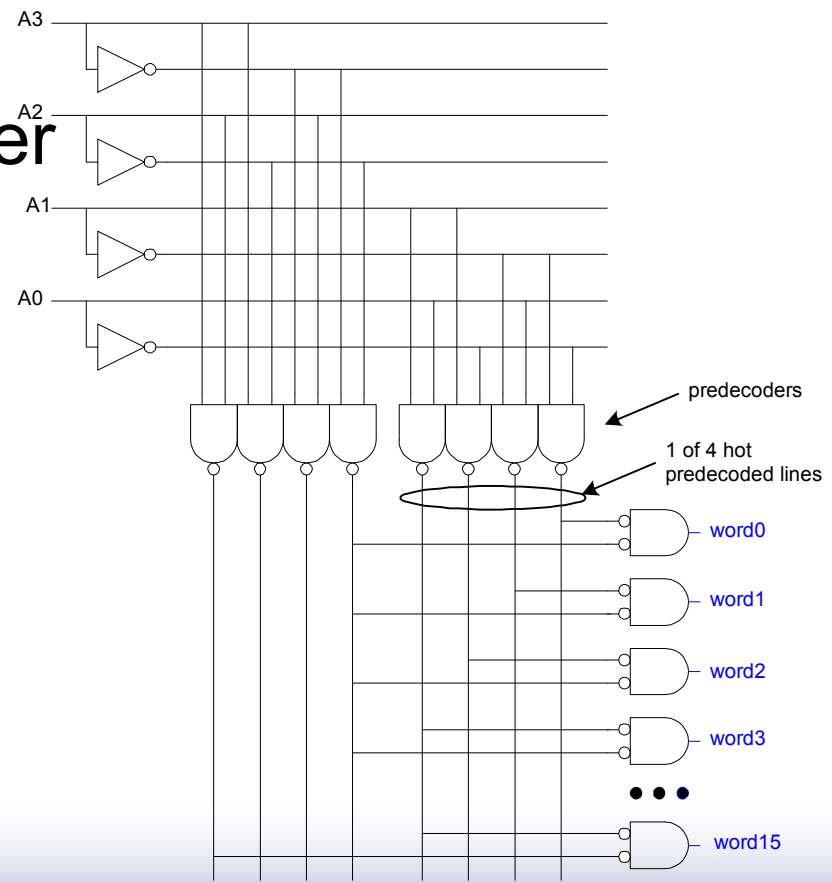

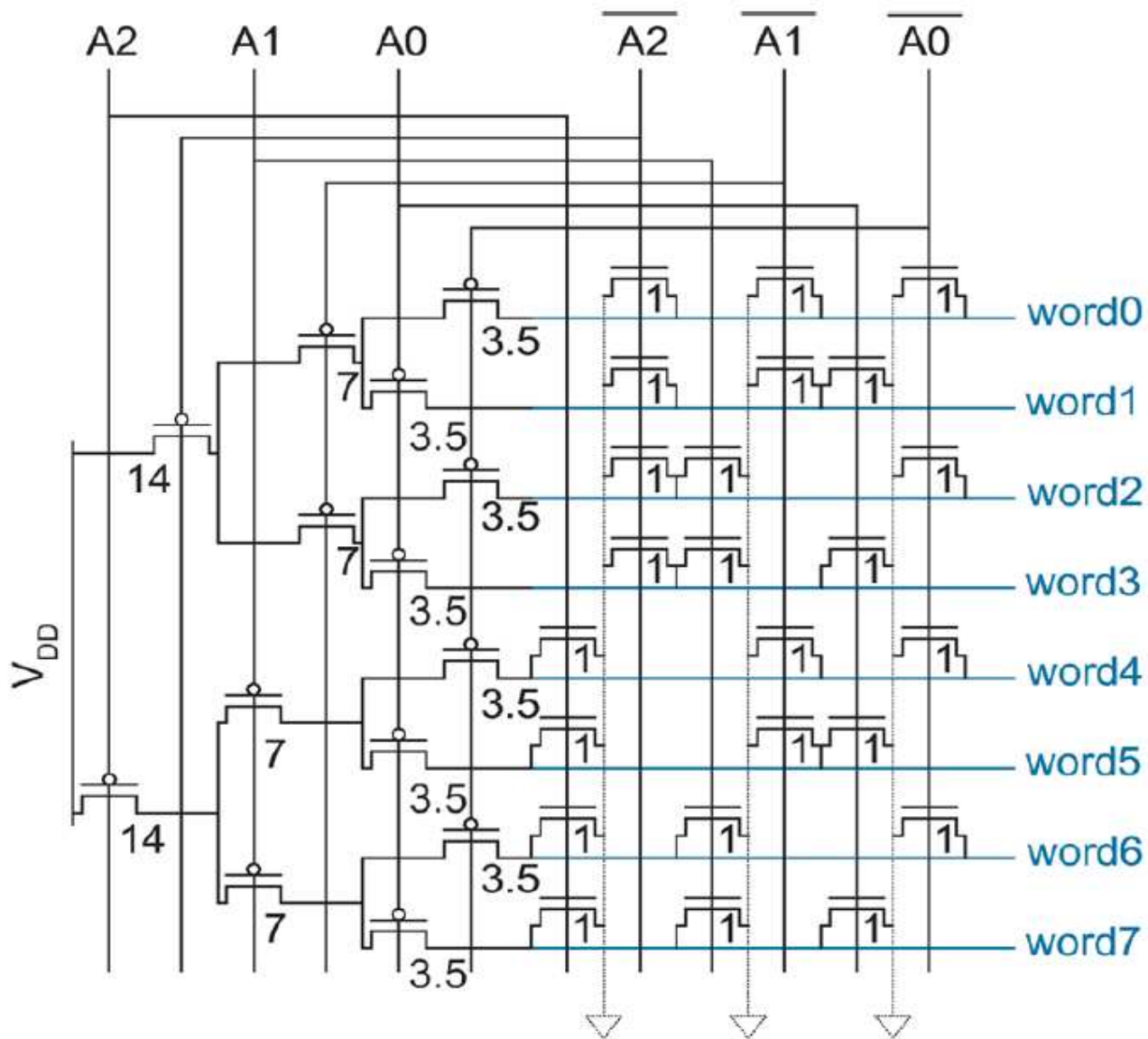


FIG 11.14 Lyon-Schediwy decoder


Column Circuitry

- Some circuitry is required for each column
 - Bitline conditioning
 - Sense amplifiers
 - Column multiplexing
- Each column must have write drivers and read sensing circuits


Column Multiplexing

- Recall that array may be folded for good aspect ratio
- Ex: 2k word x 16 folded into 256 rows x 128 columns
 - Must select 16 output bits from the 128 columns
 - Requires 16 8:1 column multiplexers

Typical Column Access

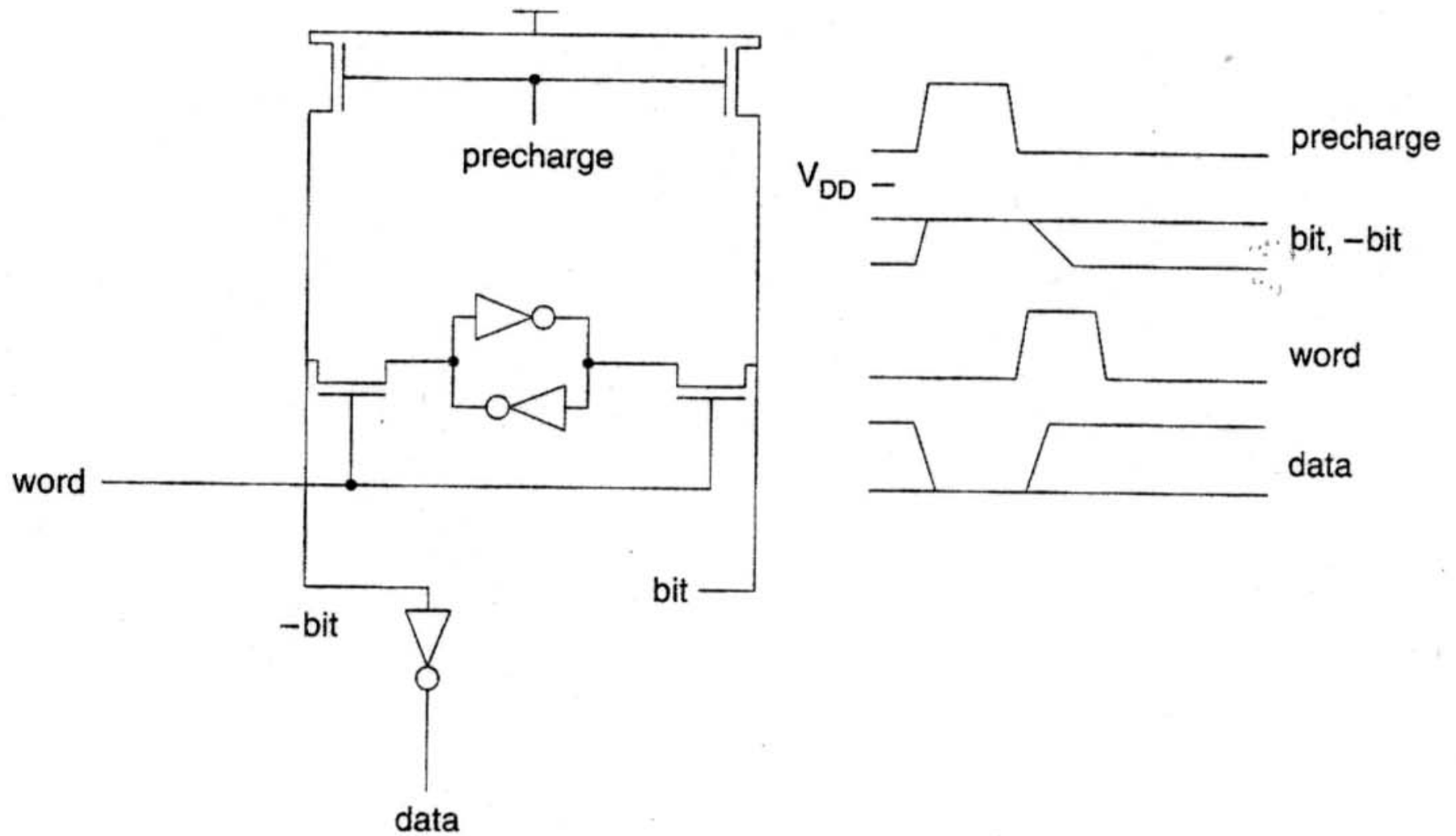


Pass Transistor Based Column Decoder

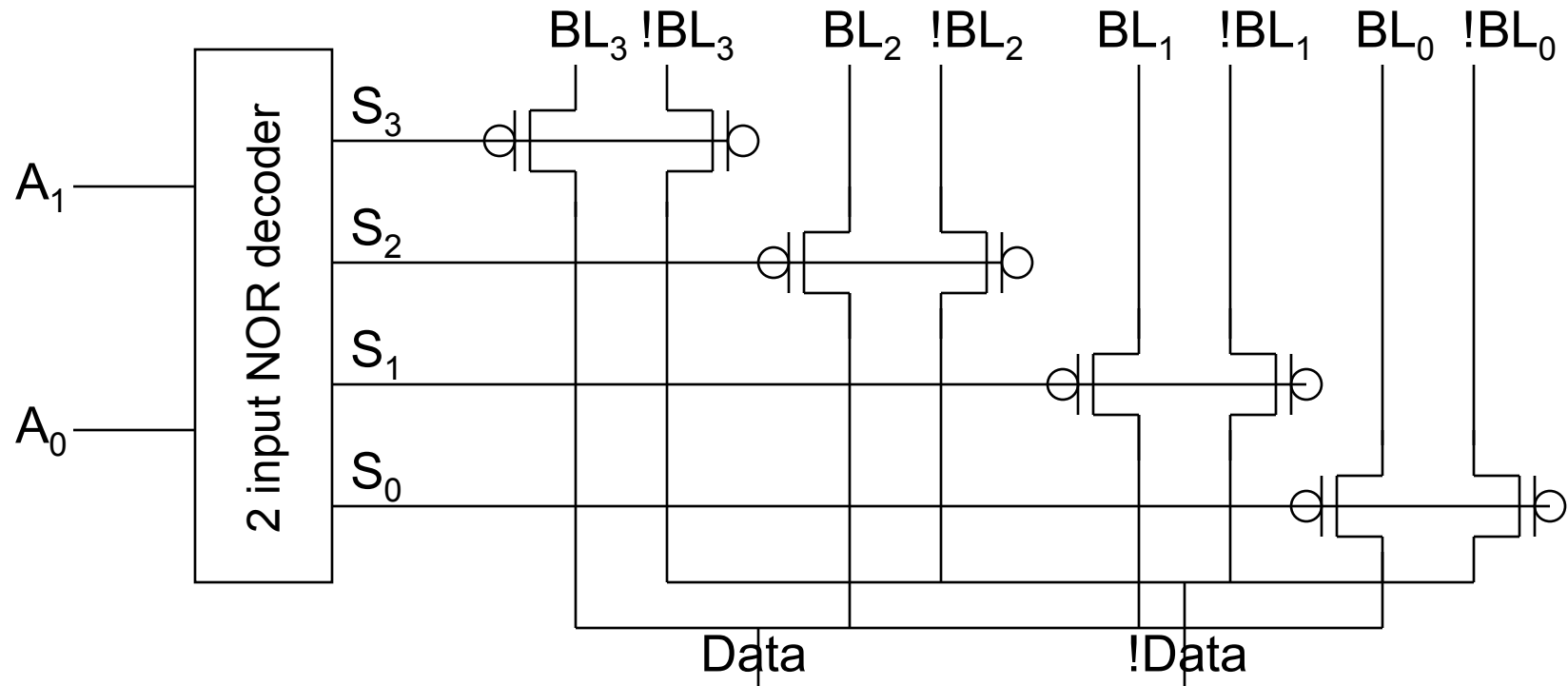


- Advantage: speed since there is only one extra transistor in the signal path
- Disadvantage: large transistor count

Tree Decoder Mux

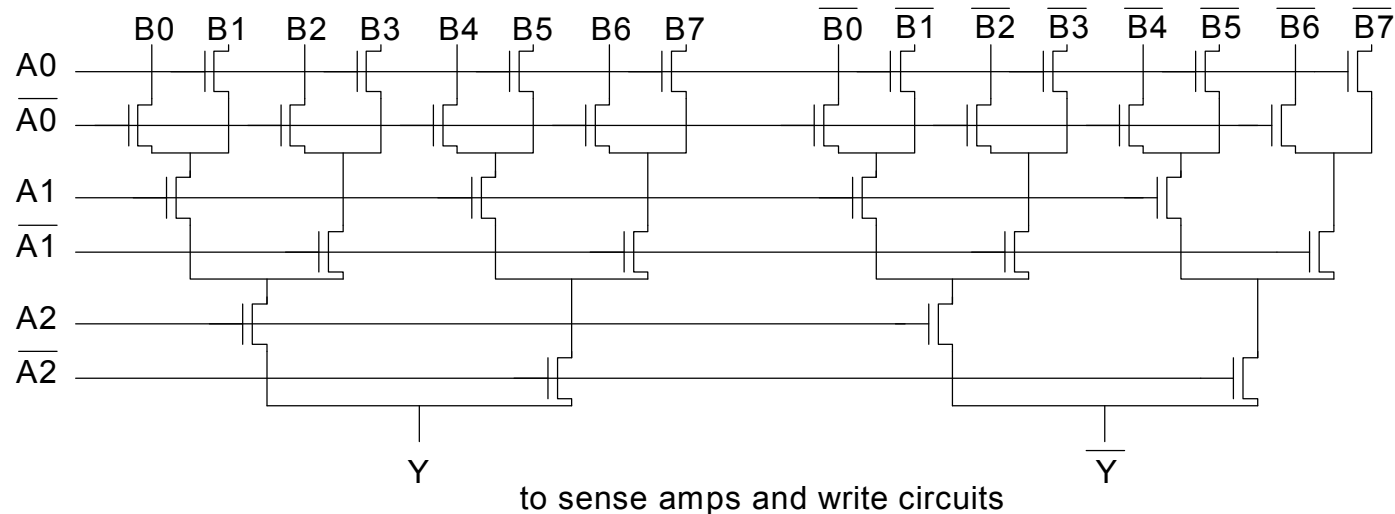- Column MUX can use pass transistors
 - Use nMOS only, precharge outputs
- One design is to use k series transistors for $2^k:1$ mux
 - No external decoder logic needed





Ex: 2-way Muxed SRAM

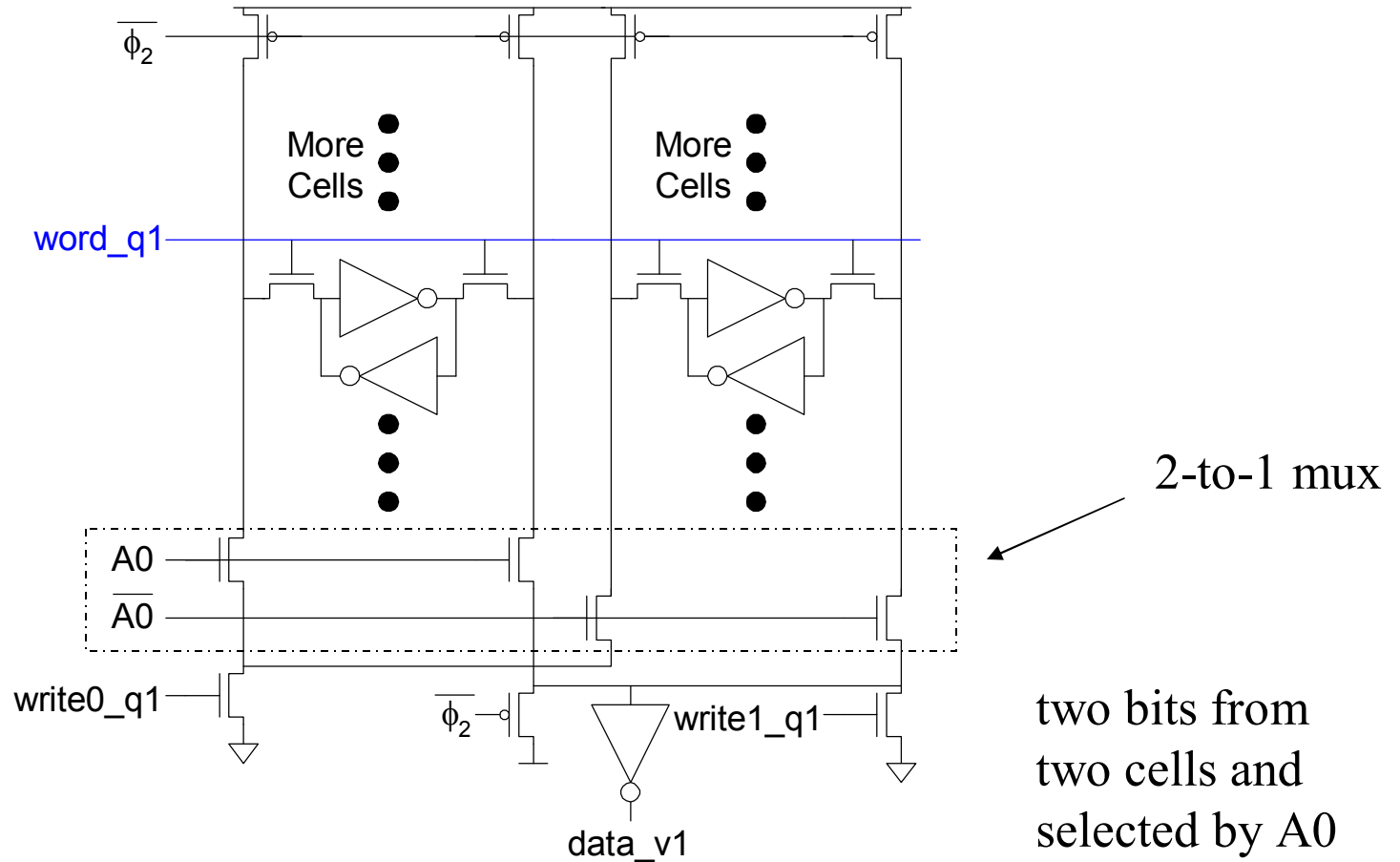

Bitline Conditioning

- Precharge bitlines high before reads

  


- Equalize bitlines to minimize voltage difference when using sense amplifiers

Sense Amplifiers

- Bitlines have many cells attached
 - Ex: 32-kbit SRAM has 256 rows x 128 cols
 - 128 cells on each bitline
- $t_{pd} \propto (C/I) \Delta V$
 - Even with shared diffusion contacts, 64C of diffusion capacitance (big C)
 - Discharged slowly through small transistors (small I)
- *Sense amplifiers* are triggered on small voltage swing (reduce ΔV)


Differential Pair Amp

 - Differential pair requires no clock
- But always dissipates static power




Clocked Sense Amp

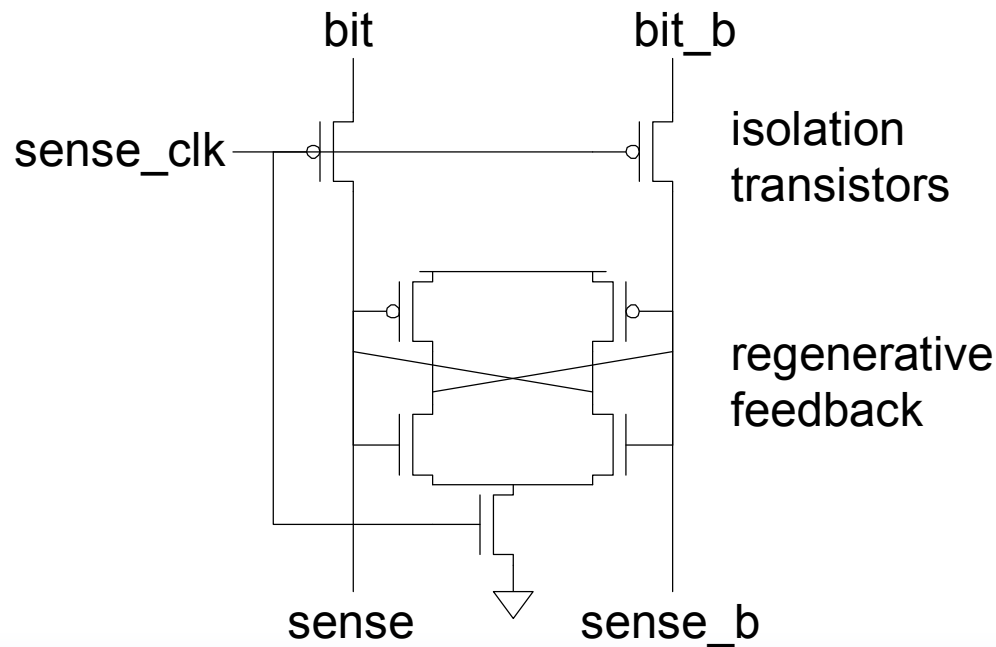
- ❑ Clocked sense amp saves power
- ❑ Requires sense_clk after enough bitline swing
- ❑ Isolation transistors cut off large bitline capacitance



Sense Amp Waveforms

 

Write Driver Circuits

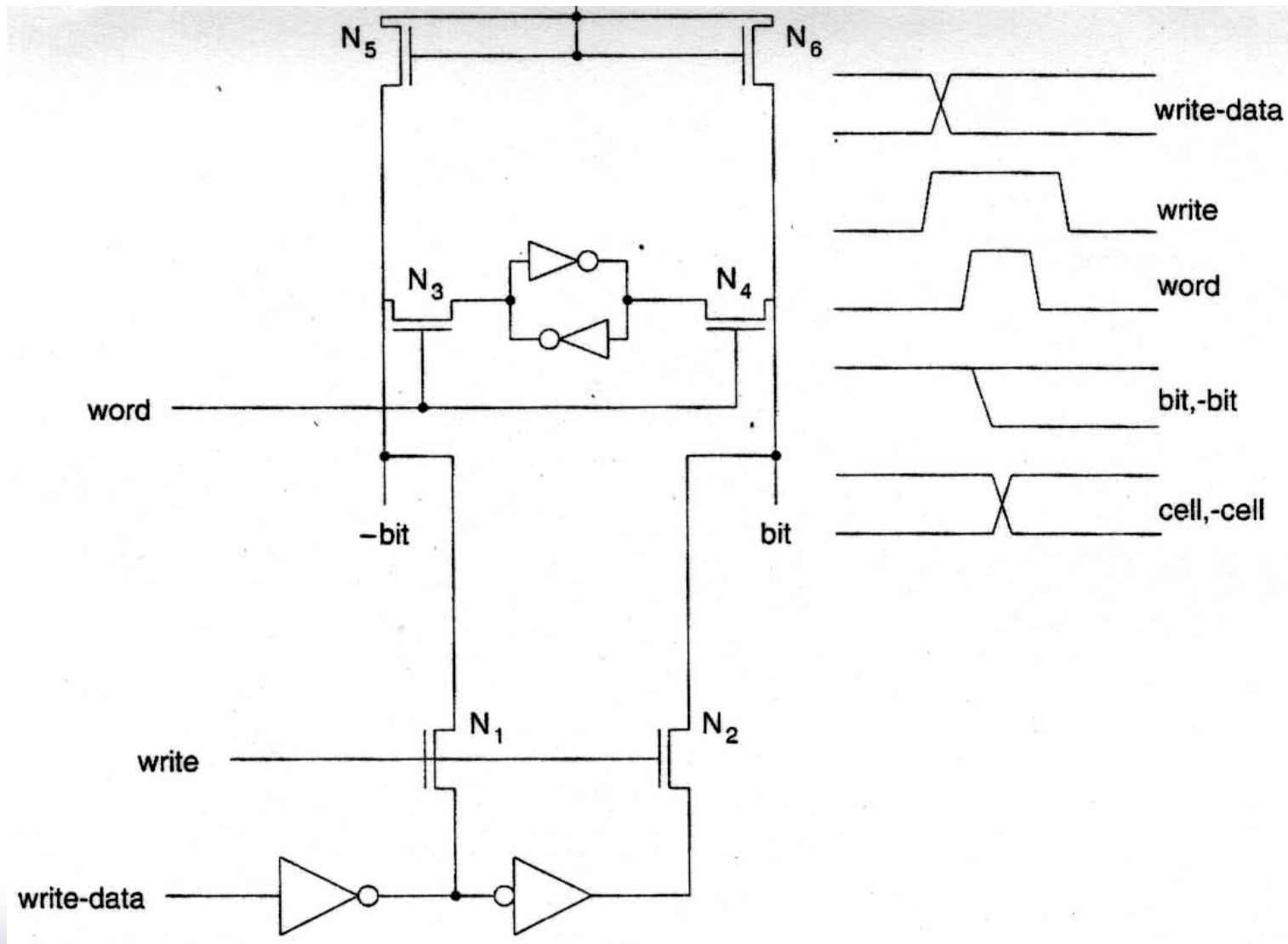


Dual-Ported SRAM

□ Simple dual-ported SRAM

- Two independent single-ended reads
- Or one differential write

wordA reads bit_b (complementary)

wordB reads bit (true)

 

□ Do two reads and one write by time multiplexing

STMicroelectronics • Read Using ph1, write during ph2


Memory

Multiple Ports

- ❑ We have considered single-ported SRAM
 - One read or one write on each cycle
- ❑ *Multiported* SRAM are needed for register files
- ❑ Examples:
 - Multicycle MIPS must read two sources or write a result on some cycles
 - Pipelined MIPS must read two sources and write a third result each cycle
 - Superscalar MIPS must read and write many sources and results each cycle

Multi-Ported SRAM

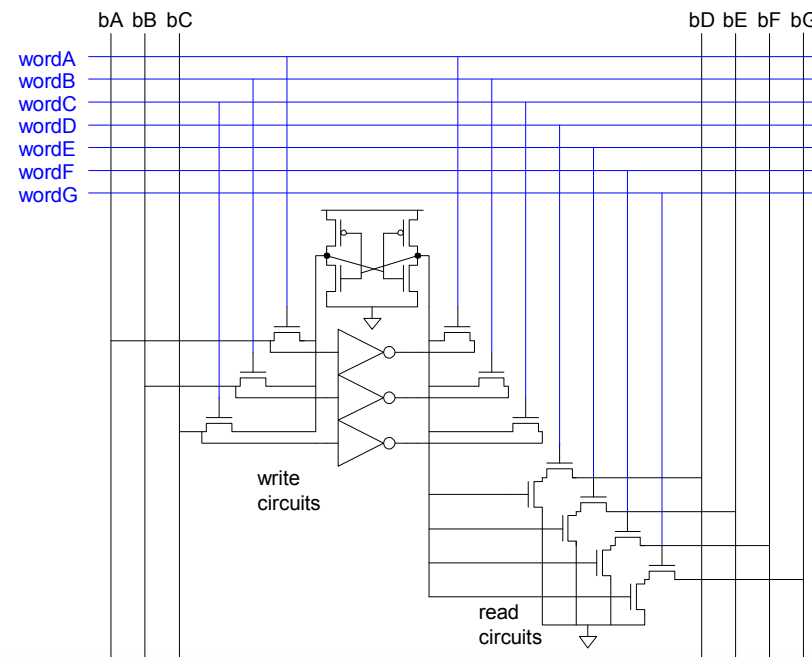- ❑ Adding more access transistors hurts read stability
- ❑ Multiported SRAM isolates reads from state node
- ❑ Single-ended design minimizes number of bitlines



Logical effort of RAMs


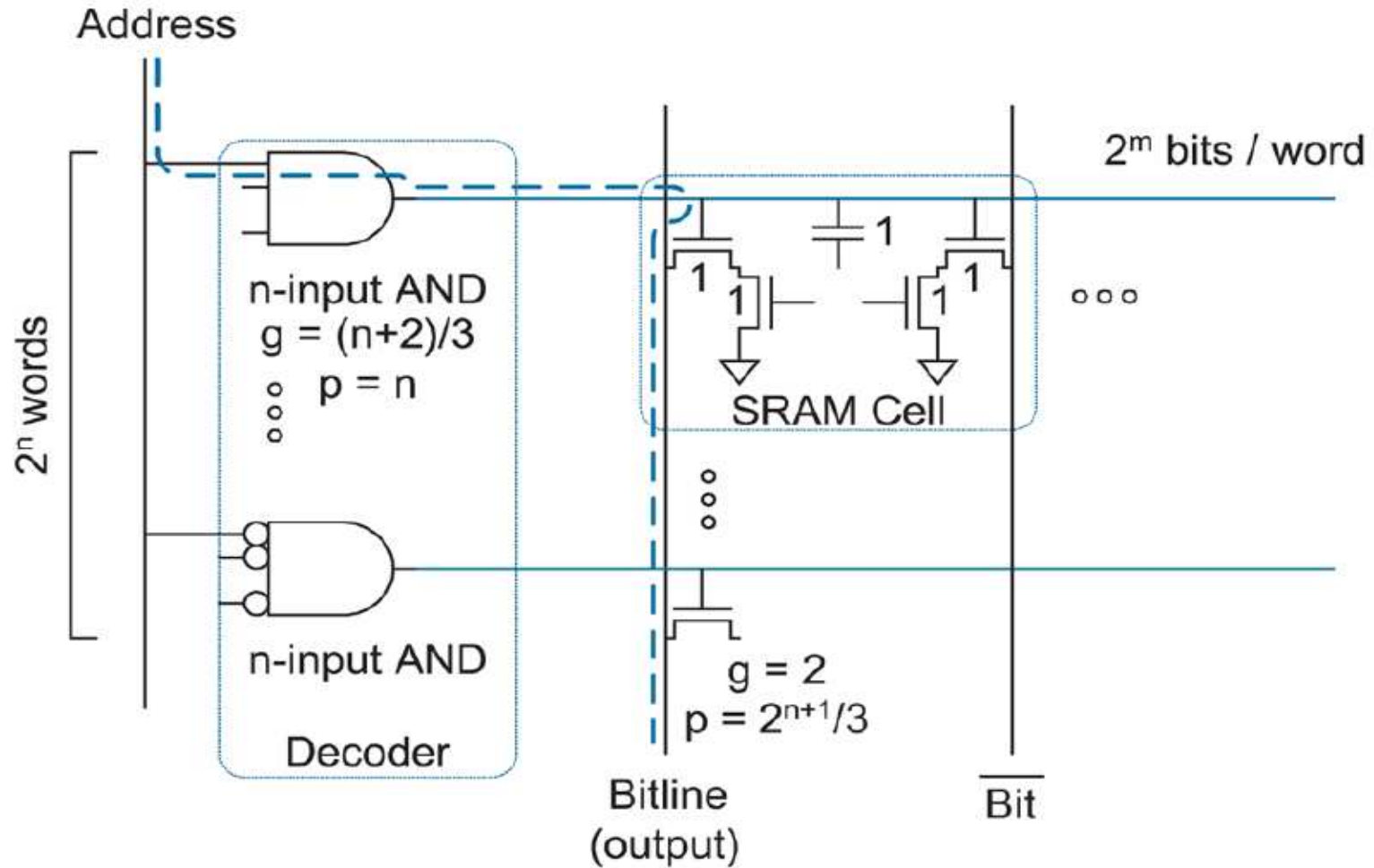



FIG 11.25 Critical path for read of small SRAM

Timing is non trivial design problem !!

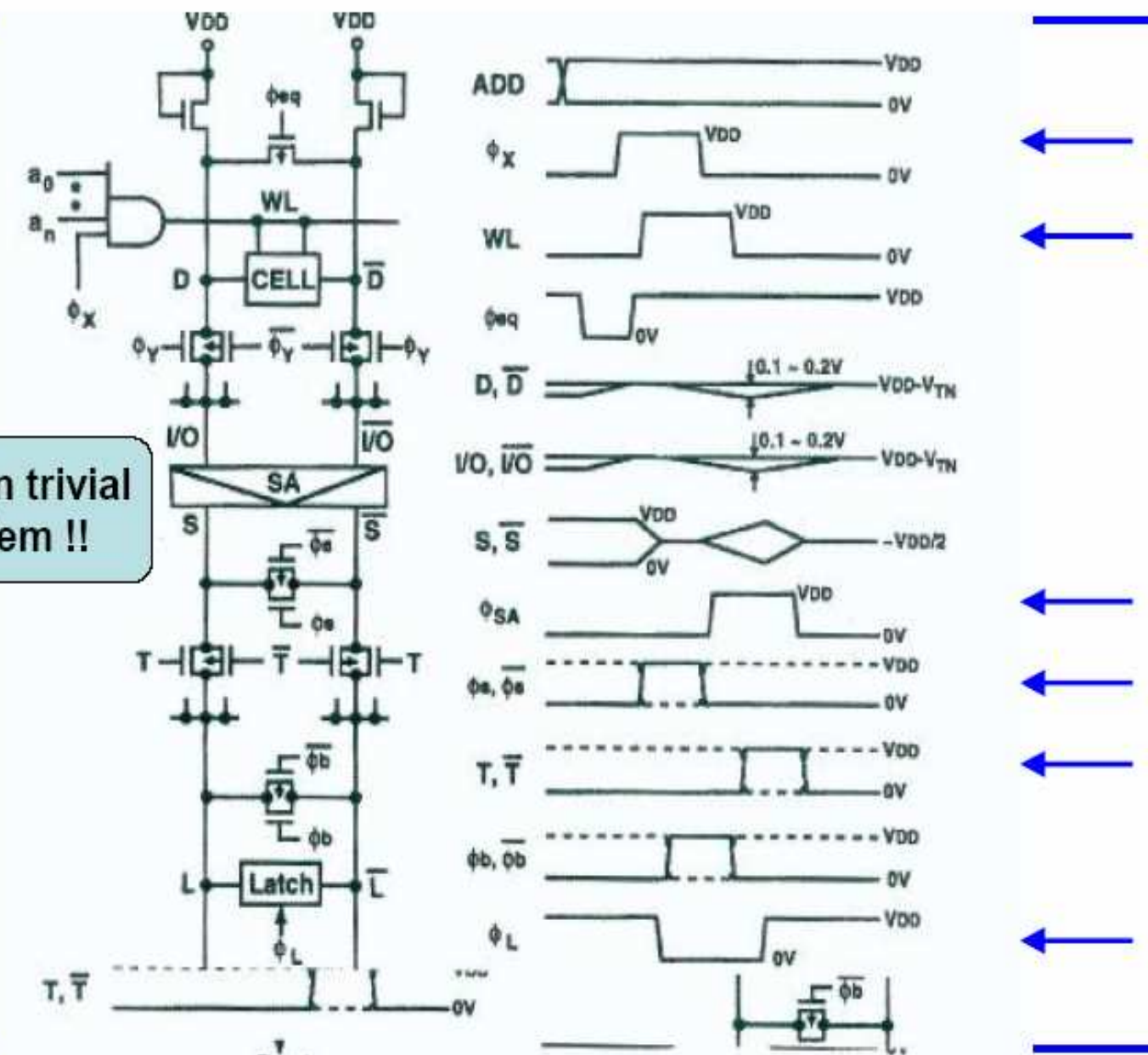

Twisted Bitlines

 - Sense amplifiers also amplify noise
 - Coupling noise is severe in modern processes
 - Try to couple equally onto bit and bit_b
 - Done by *twisting* bitlines




Alternative SRAM Cells

- ❑ Low Voltage/High Leakage/Process Variations crowd the operating margins of conventional SRAM
- ❑ Alternative Sense Amplifiers, column and row arrangements, adaptive timing, smaller hierarchy, redundant and spare rows/columns have all been addressed in the literature with some success.
- ❑ Some problems come from the cell design itself—modifying the cell can break conflicting demands for optimization

10T

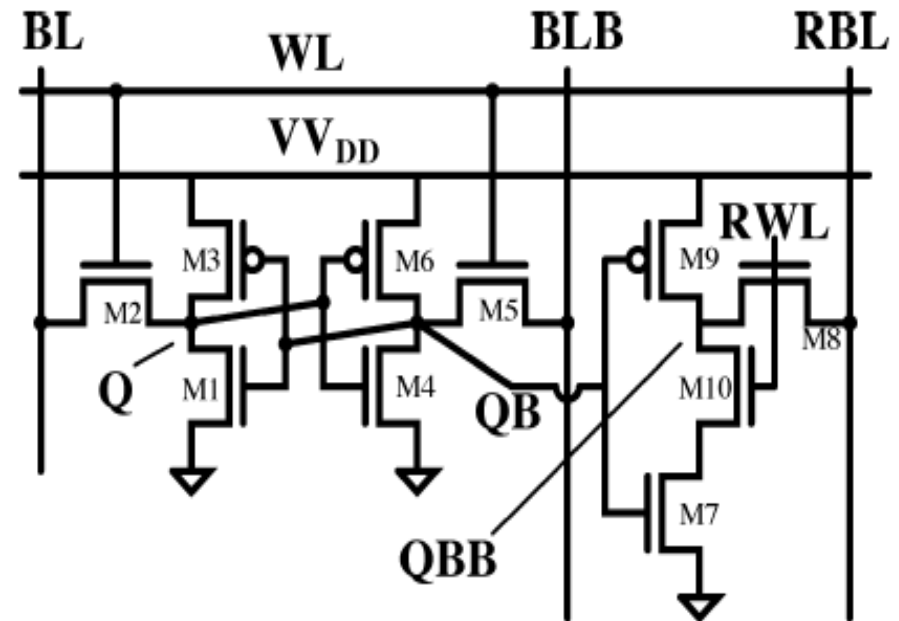- Features
 - BL Leakage reduction
- Approaches
 - Separated Read port
 - Stacked effect by M10
- Performance
 - 400mV@475kHz, 3.28uW
 - 320mV W/O Read error@27°C
 - 380mV W/O Write error@27°C
 - $V_{min}=300mV@1\%$ bit errors
 - 256 bits/BL




A 256-kb 65-nm Sub-threshold SRAM Design for Ultra-Low-Voltage Operation

STMicro/Intel/UCSD/THNU **B. Calhoun & A. Chandrakasan, JSSC, 2007**
Memory

10T

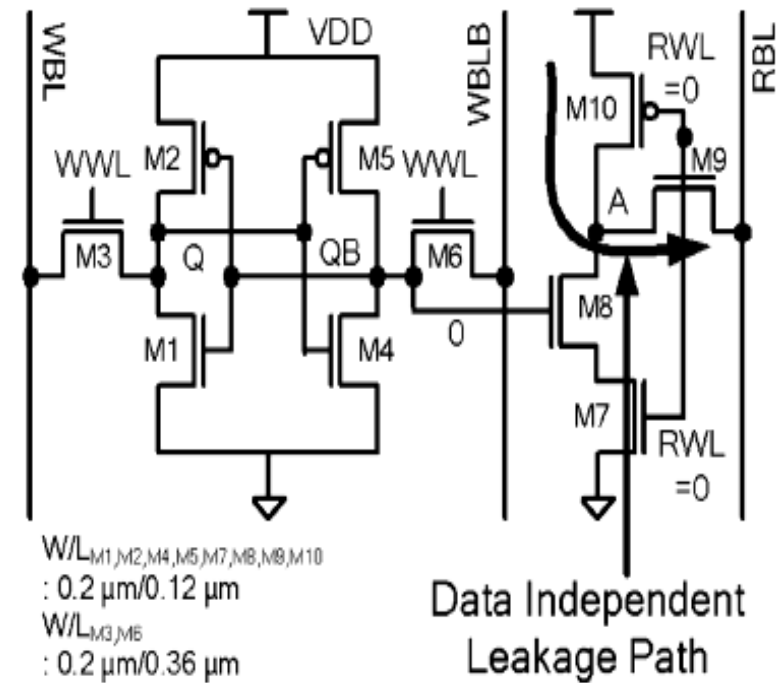- Features
 - BL leakage reduction of data
- Approaches
 - Virtual GND Replica
 - Reverse Short Channel Effect
 - BL Writeback
- Performance
 - 0.2V@100kHz, 2uW
 - 1024 bits/BL
 - 130nm process technology



A High-Density Subthreshold SRAM with Data-Independent Bitline Leakage and

Virtual Ground Replica Scheme

Chris Kim, ISSCC 2007

10T

□ Features


- ST cell array can work @160mV
- 2.1x larger than 6T cell

□ Approaches

- Schmitt Trigger based cell
- Good stability @ LowVDD
- Good scalability

□ Performance

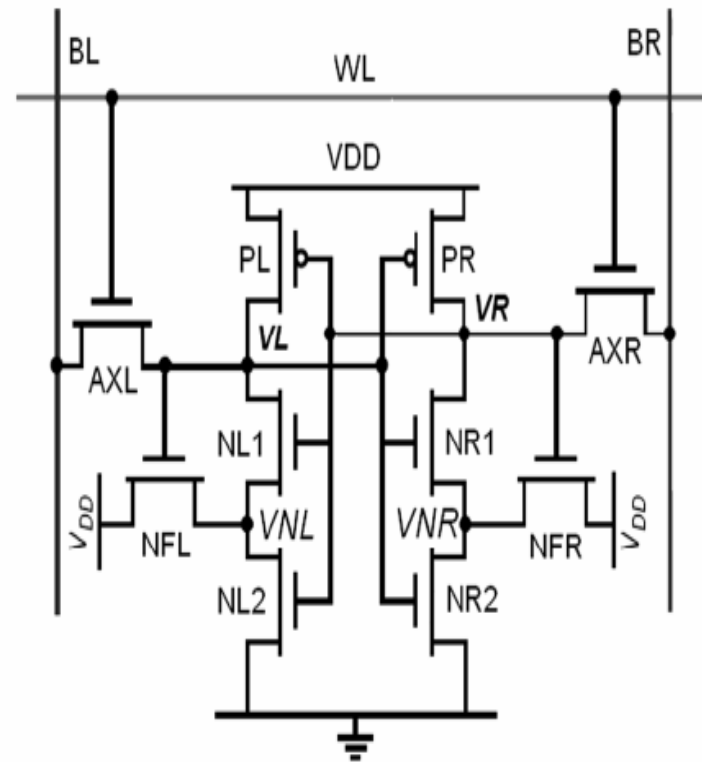- Read SNM \uparrow 1.56x @VDD=0.4V
- More power saving
- Leakage power \downarrow 18%
- Dynamic power \downarrow 50%
- Hold SNM @150mV is 2.3x of 6T
- 130nm process



A 160mV Robust Schmitt Trigger Based Subthreshold SRAM

K. Roy, JSSC, 2007

9T

□ Features

- Modifying from 10Tcell
- 17% more area than 6T cell
- 16.5% less area than 10T cell

□ Approaches


- More leakage saving than 8T cell
- Separated read port

□ Performance

- 128 bits/BL @350mV ,100MHz
- Hold SNM=117mV @300mV
- Stand-by power: 6uW
- 65nm process

A 100MHz to 1GHz, 0.35V to 1.5V Supply 256x64 SRAM Block using Symmetrized 9T SRAM cell with controlled Read

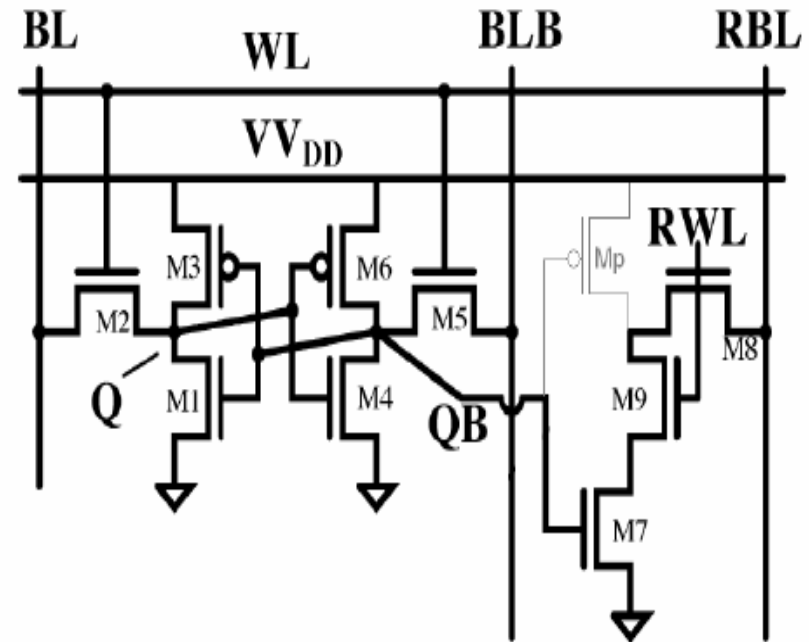S. A. Verkila,et al, Conference on VLSI Design, 2008



9T

□ Features

- Read stability enhancement
- Leakage power reduction

□ Approaches

- Separated read port
- Min. sizing of N3, N4 and negative


Vg7, and larger Node3 durir stand-by mode for leakage reduction

□ Performance

- 2x R-SNM cf. 6T
- 22.9% leakage power reduction
- 65 nm PTM


High Read Stability and Low Leakage Cache Memory Cell

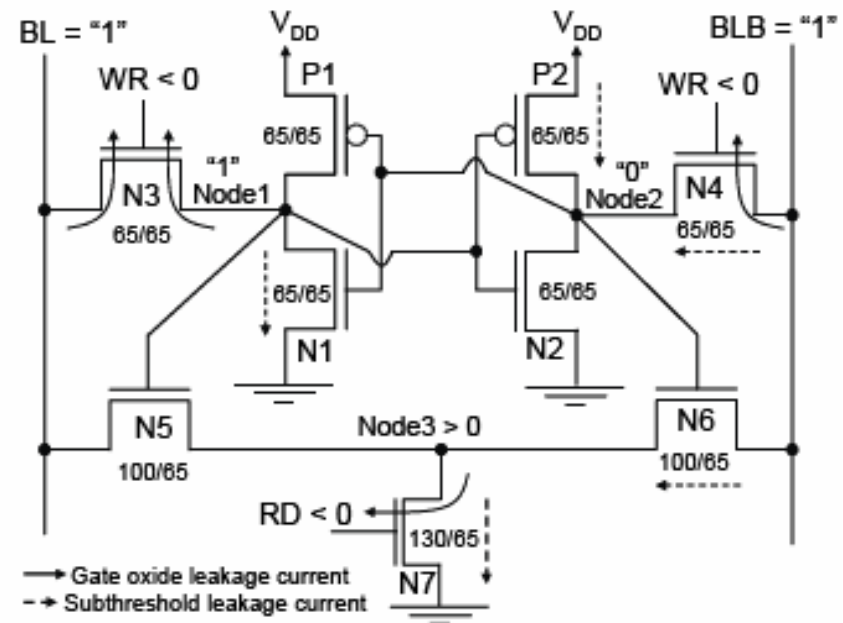Z. Liu and V. Kursun, IEEE Conference, 2007



8T

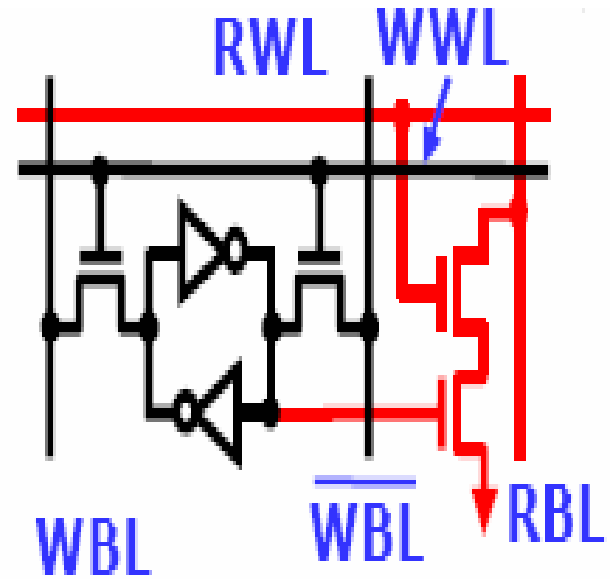- Features
 - No read disturb
 - About 30% area penalty
- Approaches
 - Separate Read & Write WL
 - Separated read port
- Performance
 - Larger SNM than 6T
 - Better scalability than 6T



Stable SRM Cell Design for the 32nm Node and Beyond

Leland Chang et. al,
Symp. on VLSI 2005
Memory

8T

□ Features


- No read disturb
- Low VDD(350mV)
- Low subthreshold(Sub. Vt) leakage

□ Approaches

- Separate Read & Write WL
- Separated read port
- Foot-drivers reduce the sub.Vt leakage

□ Performance

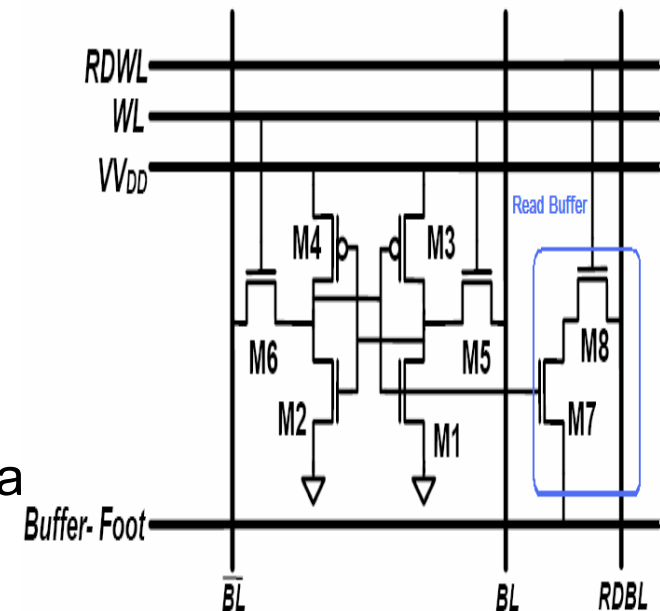- 65nm process ,128 cells/row
- Operating @ 25KHz
- 2.2uW leakage power



A 256kb 65nm 8T Subhreshold SRAM Employing Sense-Amplifier

Redundancy

STMicro/Intel/UCSD/THUN. Verma ,and A. P. Chandrakasan, JSSC,2008

7T

□ Features


- 23% smaller than Conv. 6T bitcell
- Low VDD(440mV)
- Not suit for low speed demanc

□ Approaches

- Seperate Read &Write WL
- Seperate Read &Write BL
- Data protection nMOS:N5

□ Performance

- 20ns access time@0.5V
- 90nm process

 

A Read-Static-Noise-Margin-Free SRAM Cell for Low-VDD and

STMicro/Intel/UCSD/THNU High-Speed Applications NEC, JS&C, 2006

7T

□ Features


- 90% power saving

□ Approaches

- BL swing: $V_{DD}/6$

□ Performance

 - 0.35um proces
- *Leakage* not controlled well



90% Write Power-Saving SRAM Using Sense-Amplifying Memory Cell

T. Sakurai et. al., JSSC, 2004

7T

□ Features


- Low write power
- SNM is effected by “Read pattern”
(Read 0-N2,P2,N4 & Read 1-N1,P1,N3,N5)
- 17.5% larger than 6T

□ Approaches

- Reducing write power by cut off the (feedback) connection to BL

□ Performance

- 0.18um proces
- 49% write power saving

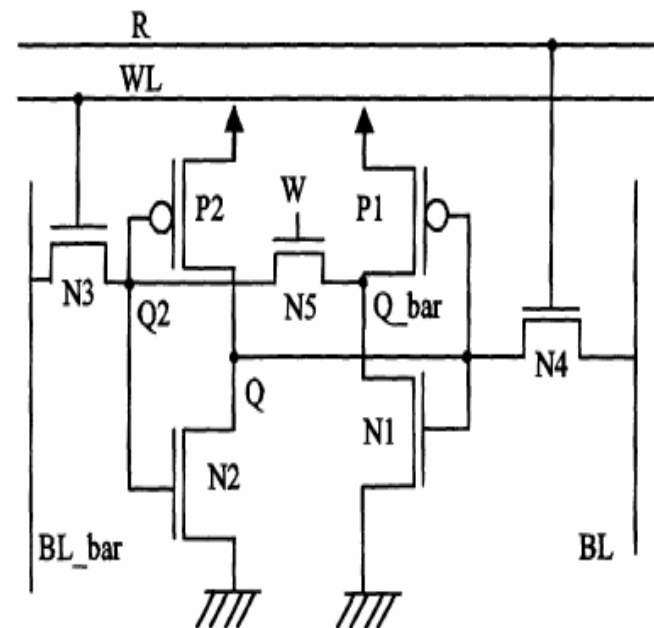


Novel 7T SRAM Cell For Low Power Cache
Design

R. Aly, M. Faisal and A. Bayoumi

IEEE SoC Conf. 2005

6T

 - Features
 - Single-ended
 - Low VDD
- Approaches
 - Adjustable header/footer (virVDD, virGND)
- Performance
 - VDD range: 1.2V~193mV
 - Vmin=170mV with 2% redundancy




A Sub-200mV 6T SRAM in 0.13 μ m CMOS

ISSCC, 2007
Memory

5T

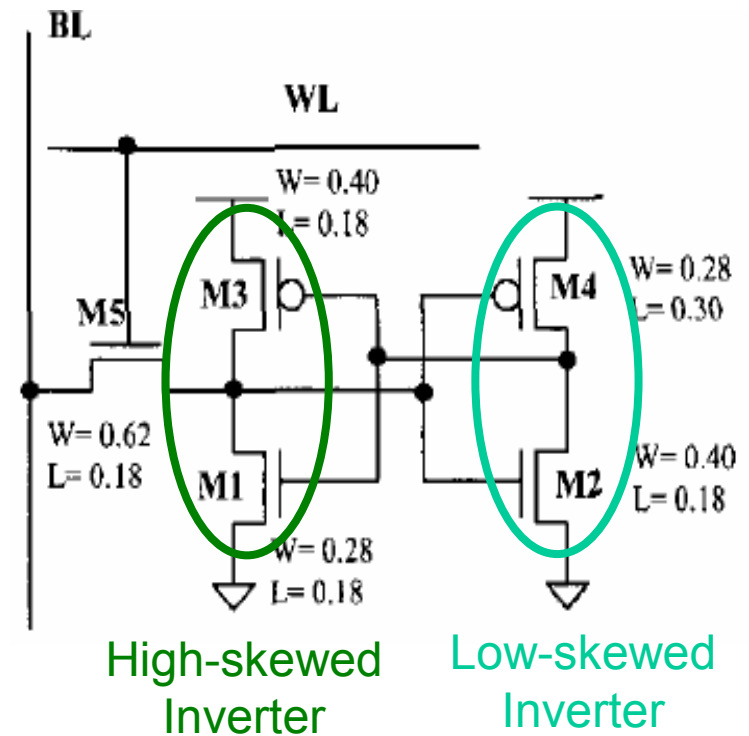- Features
 - Single-ended
 - Single BL, Single WL
 - Area 23% smaller than 6T
- Approaches
 - BL precharge to $V_{pc}=600mV$
 - Asymmetric cell sizing
 - Differential SA is used for Read
- Performance
 - 75% BL leakage reduction cf. 6T
 - SNM is *50% lower* than the 6T's
 - 0.18um process



A High Density, Low Leakage, 5T SRAM for Embedded Caches

Example Electrical Design: UCSD




32nm prototype

- Butterfly (read stability)
- N-curves (read and write stability)
- I_{read} (read stability and access time)
- VDD_{HOLD} (data retention)
- I_{leakage} (power and data retention)
- SPICE Model:
 - 32nm HKMG (high-K/metal-gate) from PTM
- Reference Design
 - Scaled bitcell from TSMC 90nm bitcell

	TSMC 90nm		32nm scaled from TSMC 90nm (REFERENCE)		32nm proposed (for 30x12, 25x12)	
	L (nm)	W (nm)	L (nm)	W (nm)	L (nm)	W (nm)
Pull-up	100	100	32	32	32	44
Pull-down	100	175	32	56	32	88
Pass-Gate	115	120	37	38	32	44


Butterfly and N-Curves

  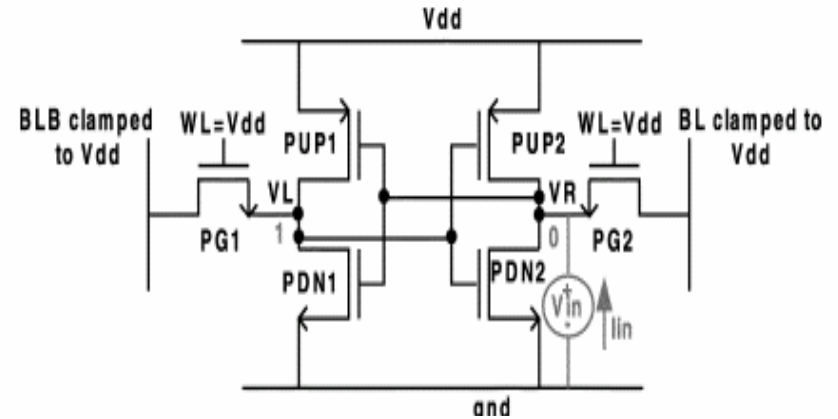- Measure method
 - Increase VR and measure VL
 - Increase VL and measure VR
 - Make voltage transfer curve in VR and VL axes → Butterfly
 - Measure I_{in} → N-curve









I_{read} , I_{leakage} and VDD_{HOLD}

- I_{read}
 - Measure bitline current when WL switches to high
- I_{LEAKAGE}
 - Measure VDD (or VSS) current when WL=0
- VDD_{HOLD}
 - Decreasing VDD voltage, while WL=0
 - Measure minimum VDD voltage when $|V(\text{nl}) - V(\text{nr})| = \text{'sensing margin'}$
(100mV is assumed)

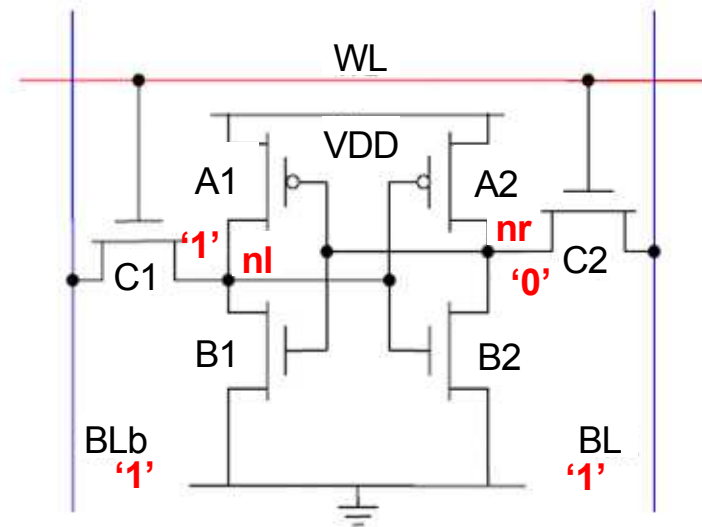

	REFERENCE	32nm proposed (for 30x12 and 25x12)
I_{read}	41.2 μA	66.7 μA
I_{leakage}	85.4 nA	142.7 nA
VDD_{HOLD}	110 mV	118 mV

Corner Simulation: Butterfly and N-Curve

    
 
 


(SS, 125degC, 1.0V)


(NN, 25degC, 1.0V)

(FF, -40degC, 1.0V)

 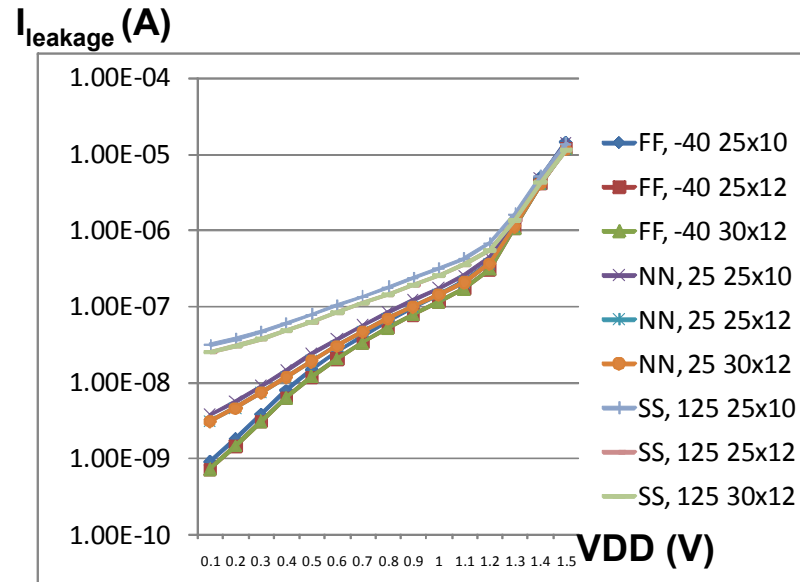 
Corner Simulation: I_{read} , I_{leakage} and VDD_{HOLD}




Processor Memory Bandwidth/Pins

 



GPU Bandwidth/Core (local and PCIe)

 

Speed Doubles With Each Generation

 

Why 3D DRAM?

  

Projected improvement to DRAM of 3-D Interconnections

BANDWIDTH
800%



POWER CONSUMPTION
50%

SIZE REDUCTION
35%

