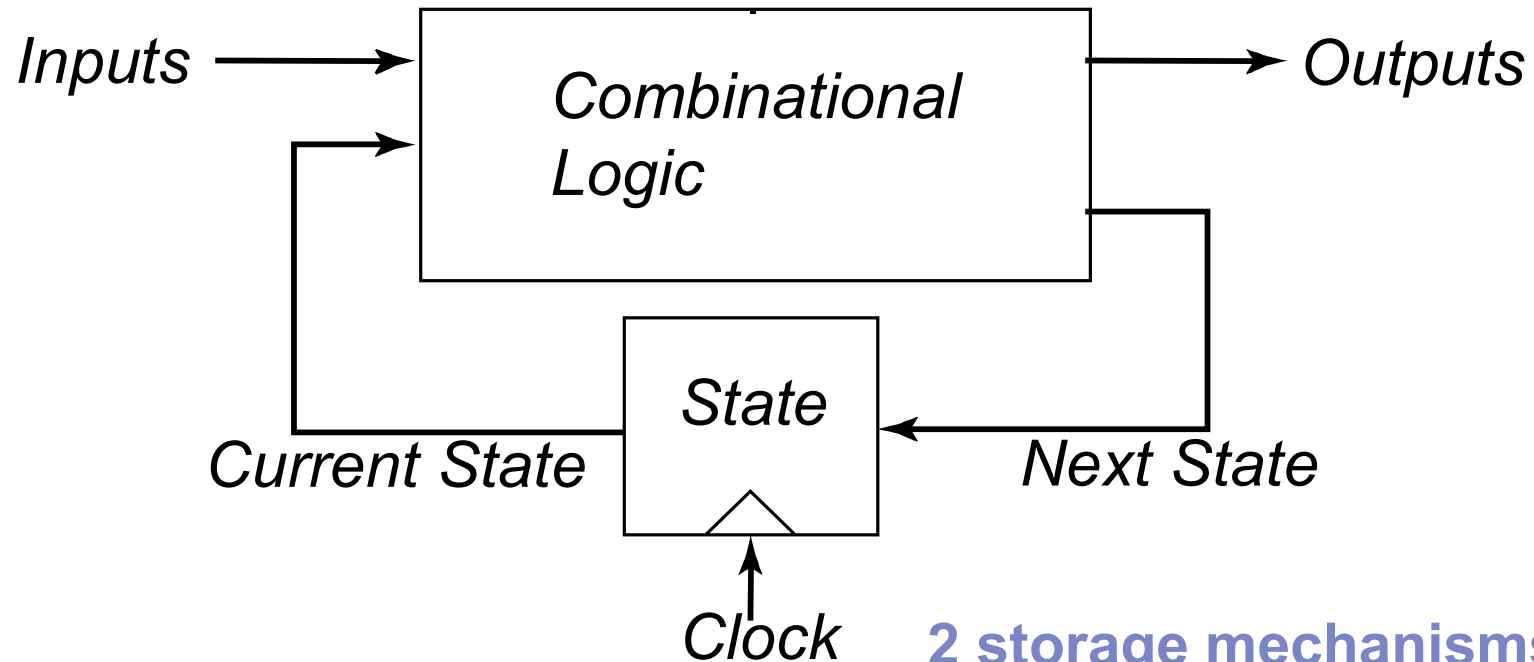




# Designing Sequential Logic Circuits

Jan M. Rabaey  
Anantha Chandrakasan  
Borivoje Nikolic

# Sequential Logic



- 2 storage mechanisms:**
- positive feedback
  - charge-based





# *Naming Conventions*

- In the text:
  - a latch is level sensitive
  - a register is edge-triggered
- Many different naming conventions:
  - flip-flops (level or edge?)
  - Transparency?
  - Dual edge/level
    
# Latch versus Register

- Latch- stores if clock is low  
transparent if clock is high


- Register- stores if clock rises, never transparent (mostly)




 
# Latch-Based Design

- N latch is transparent when  $\phi = 0$


- P latch is transparent when  $\phi = 1$



# Timing Definitions

 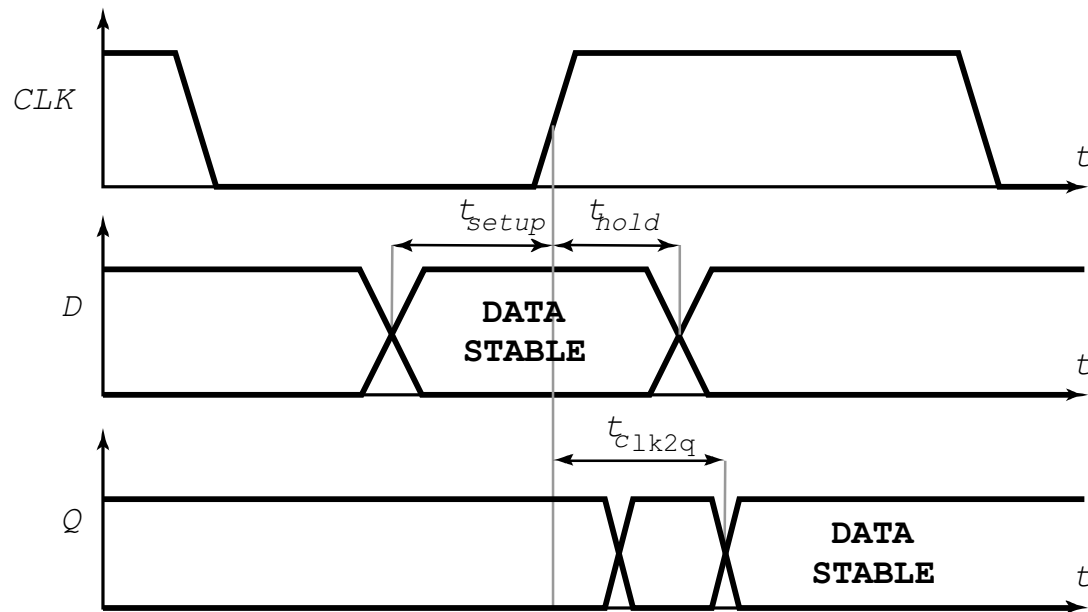

# Maximum Clock Frequency

 


## Timing Constraints:

$$t_{clk2q} + t_{p(comb)} + t_{setup} = T$$
$$t_{cdreg} + t_{cdlogic} > t_{hold}$$

First Constraint ensures clock is slow enough that Registers sample correct value

Second Constraint ensures that there is no path after the clock changes to alter the previously stored data


# Positive Feedback: Bi-Stability

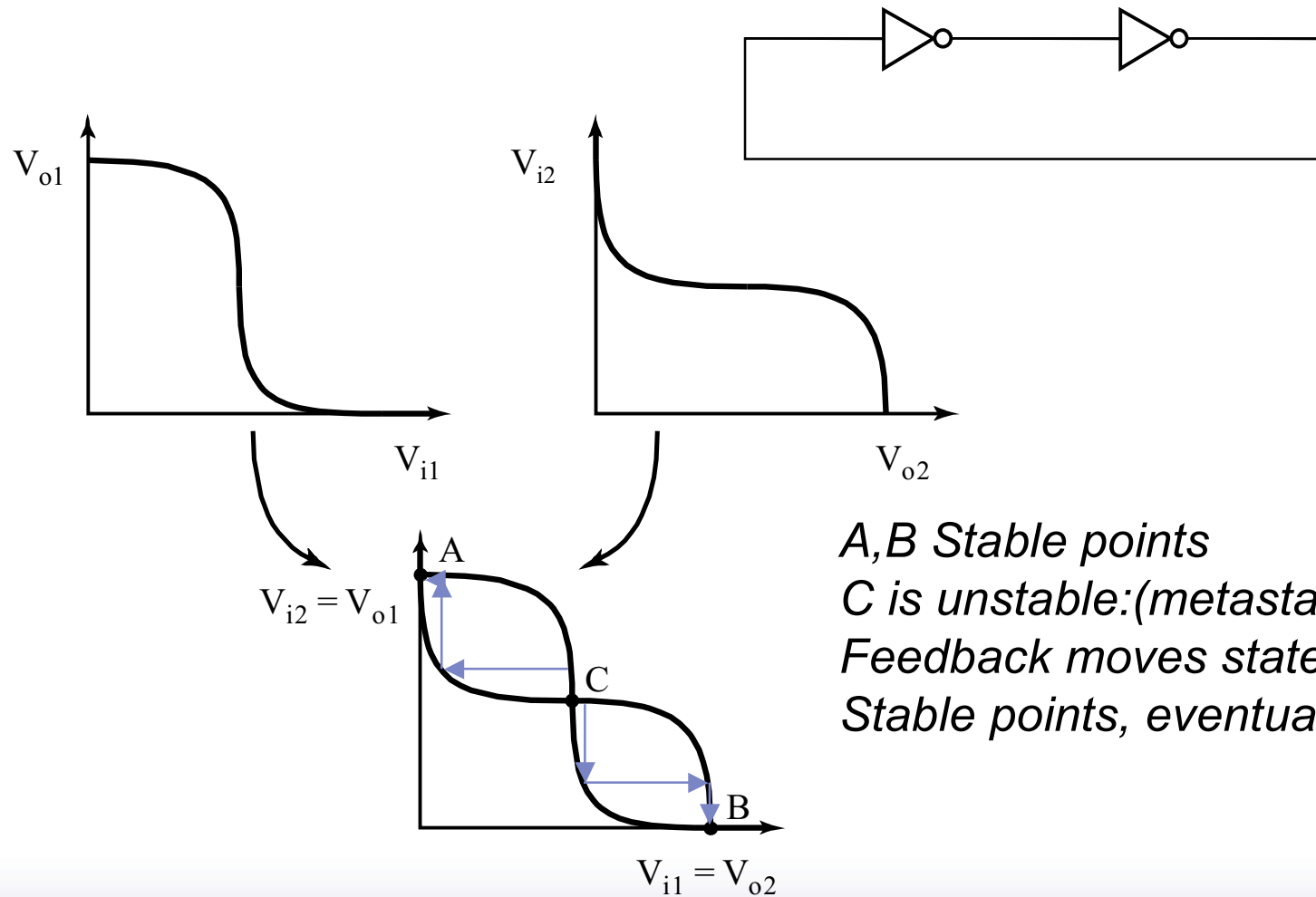


*A, B Stable points  
C is unstable: (metastable)  
Feedback moves state to  
Stable points, eventually*
 
# Writing a Static Latch

Use the clock to distinguish between the transparent and opaque states




Converting into a MUX

 

Forcing the state  
(can implement as NMOS-only)

 
# Mux-Based Latches

Negative latch  
(transparent when CLK= 0)




$$Q = \overline{Clk} \cdot Q + Clk \cdot In$$

 Positive latch  
(transparent when CLK= 1)




$$Q = Clk \cdot Q + \overline{Clk} \cdot In$$

# Master-Slave Register

 


Two opposite latches trigger on edge  
Also called master-slave latch pair

# Clk-Q Delay

 


*Clock to Q delays are  
Different for rising and falling  
Transitions  
Use Worst Case – not Avg!*

# Setup Time (MS register)

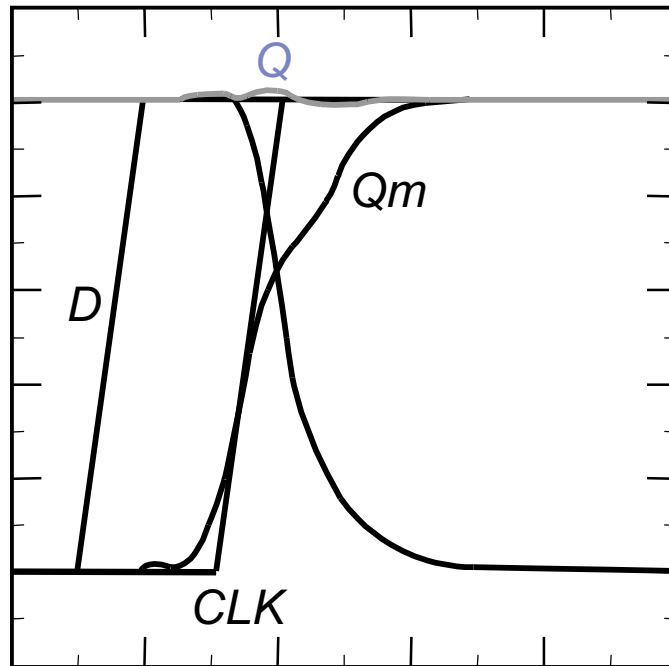


Setup = 0.21nS  
Passed D

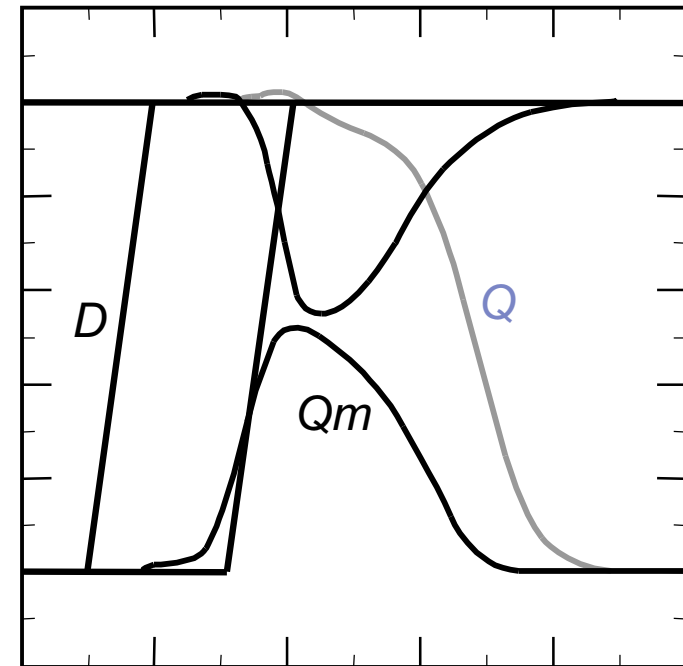


Setup = 0.20nS  
Failed to pass D
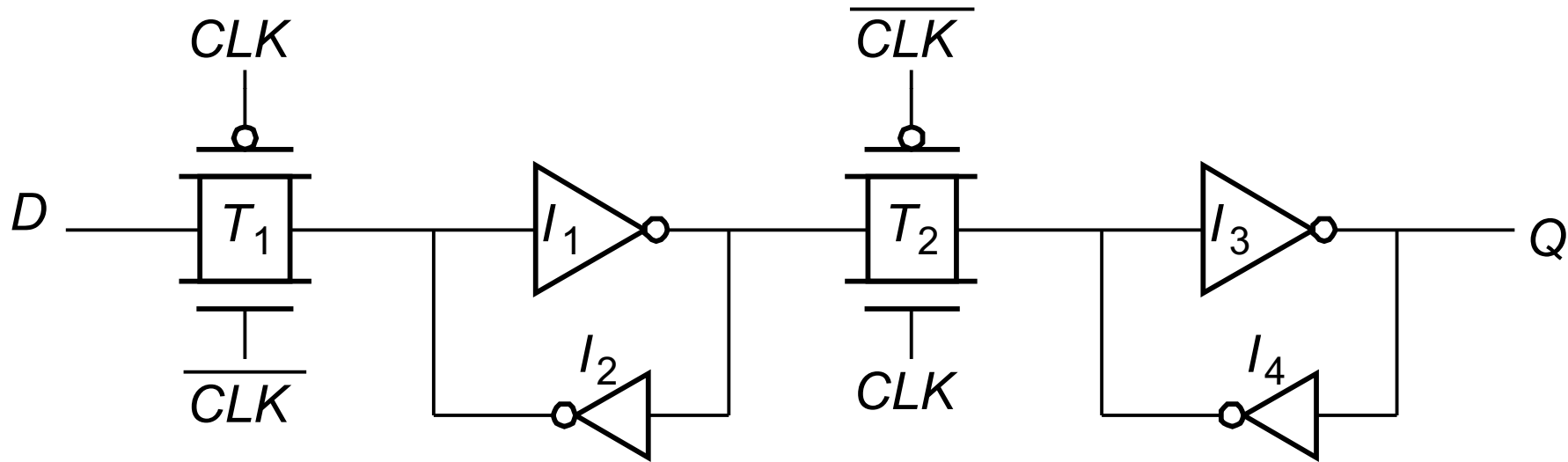
# *(Pseudo Static) Master-Slave Register*




- *Reduced load on Clock*
- *Possible Backward flow of data*
  - *Reduce strength of  $I_2$  and  $I_4$*

# Avoiding Clock Overlap

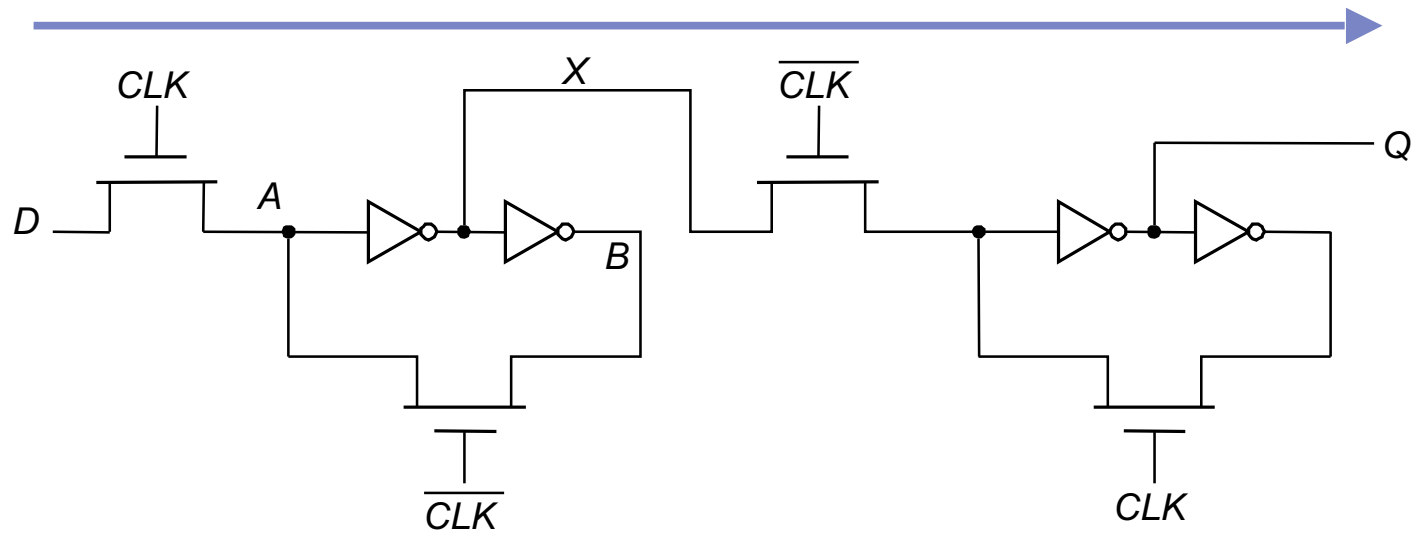



(a) Schematic diagram

 

(b) Overlapping clock pairs

# Cross-Coupled Pairs



NOR-based set-reset

  

$S$	$R$	$Q$	$Q'$
0	0	$Q$	$Q'$
1	0	1	0
0	1	0	1
1	1	-	-


# Cross-Coupled NAND

Cross-coupled NANDs

  


This is not used in datapaths any more,  
but is a basic register memory cell

# Sizing Issues

 

 
Output voltage dependence  
on transistor width



Transient response




# Making a Dynamic Latch Pseudo-Static

 

 
# Setup/Hold Time Illustrations

Circuit before clock arrival (Setup-1 case)




# Setup/Hold Time Illustrations
 
## Circuit before clock arrival (Setup-1 case)



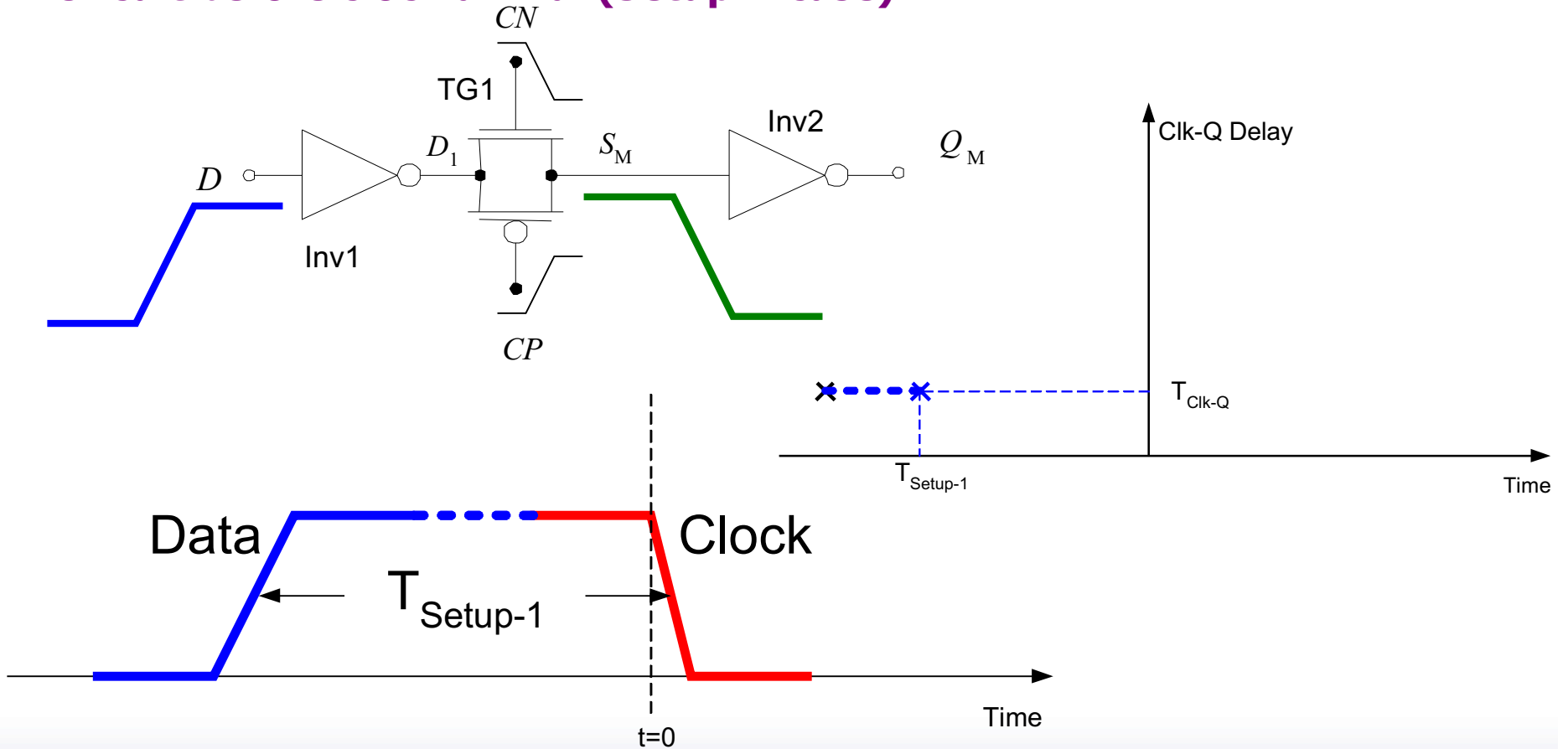
# Setup/Hold Time Illustrations

Circuit before clock arrival (Setup-1 case)



 
# Setup/Hold Time Illustrations

Circuit before clock arrival (Setup-1 case)



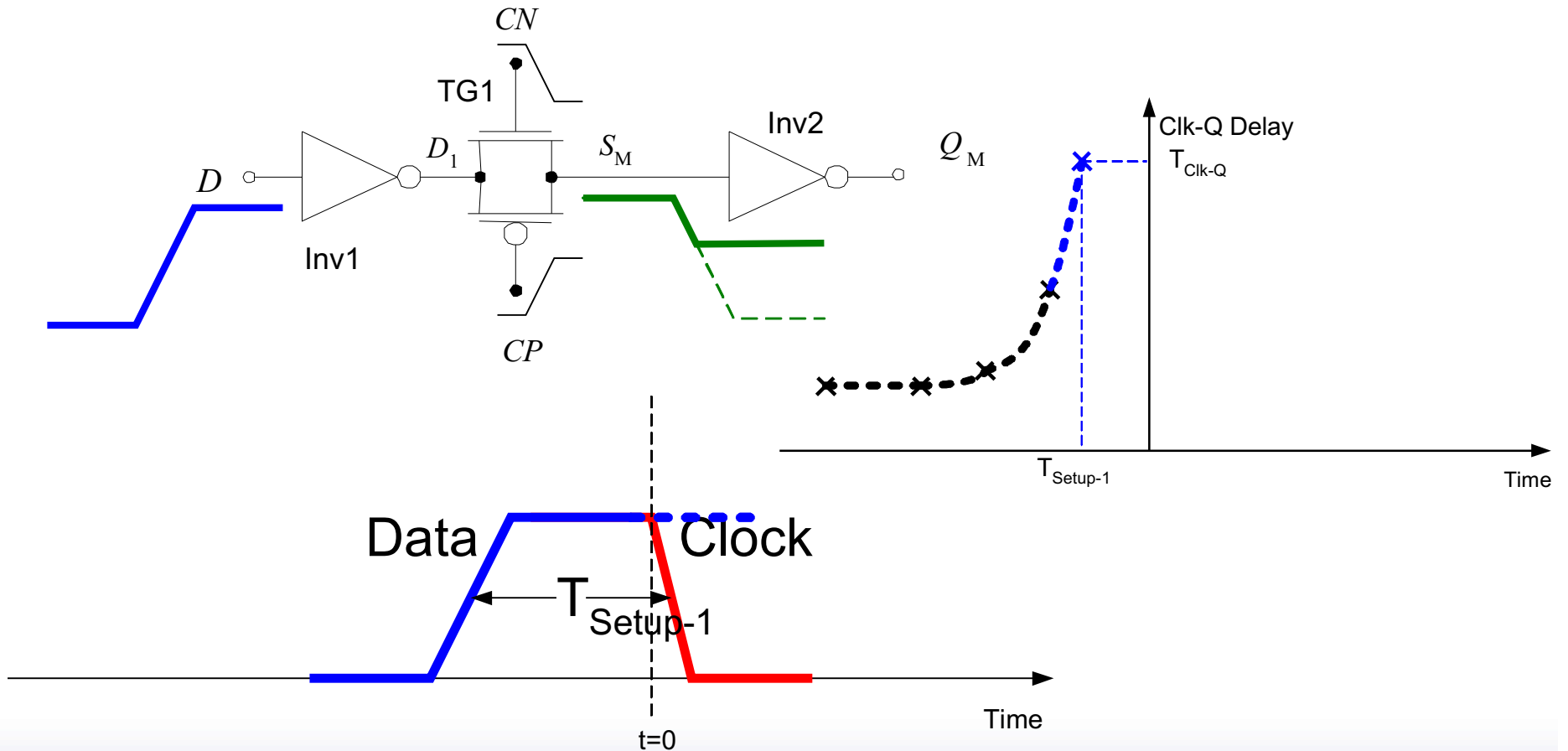
# Setup/Hold Time Illustrations

Circuit before clock arrival (Setup-1 case)




# Setup/Hold Time Illustrations

## Hold-1 case

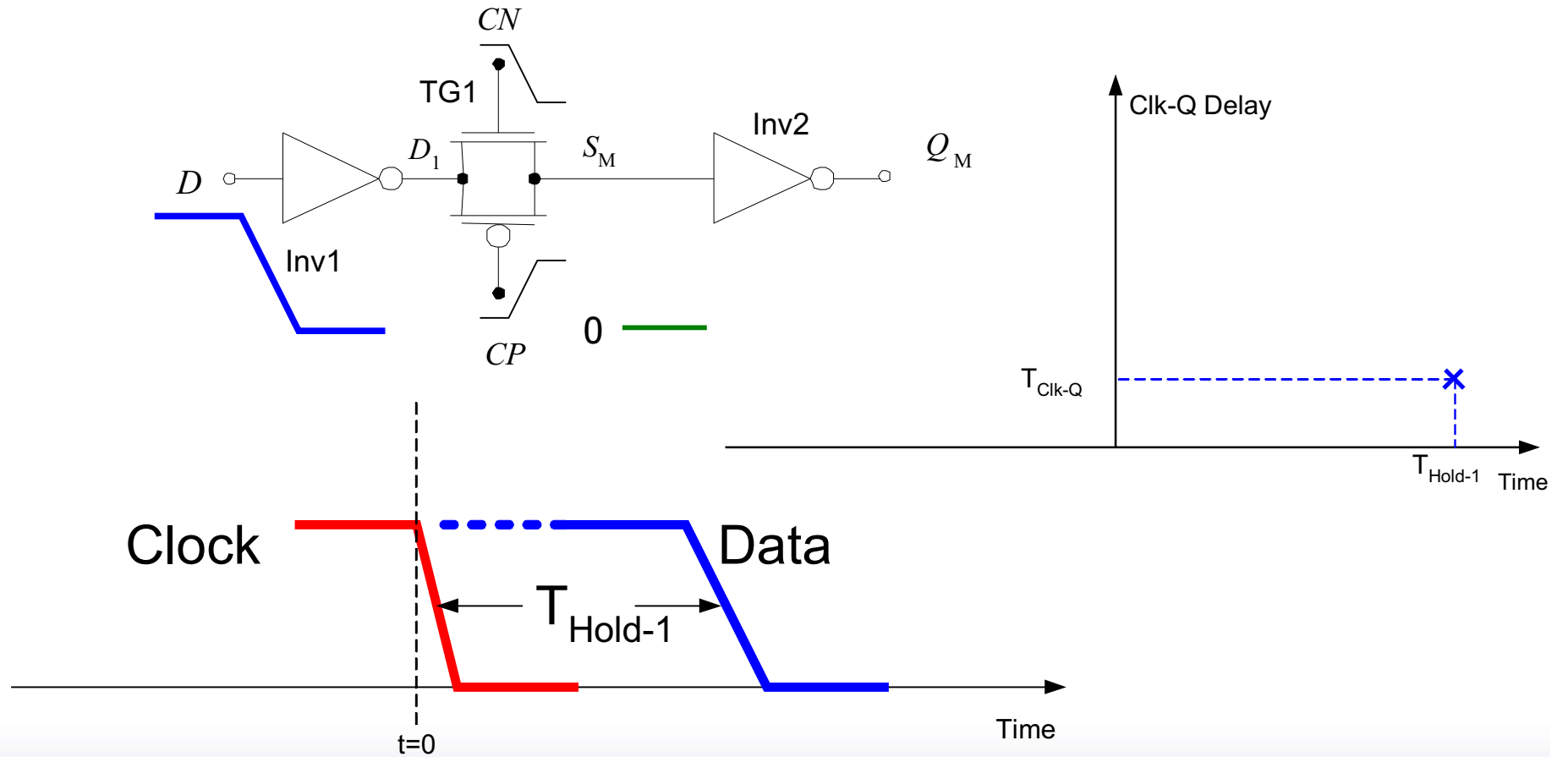


# Setup/Hold Time Illustrations

## Hold-1 case

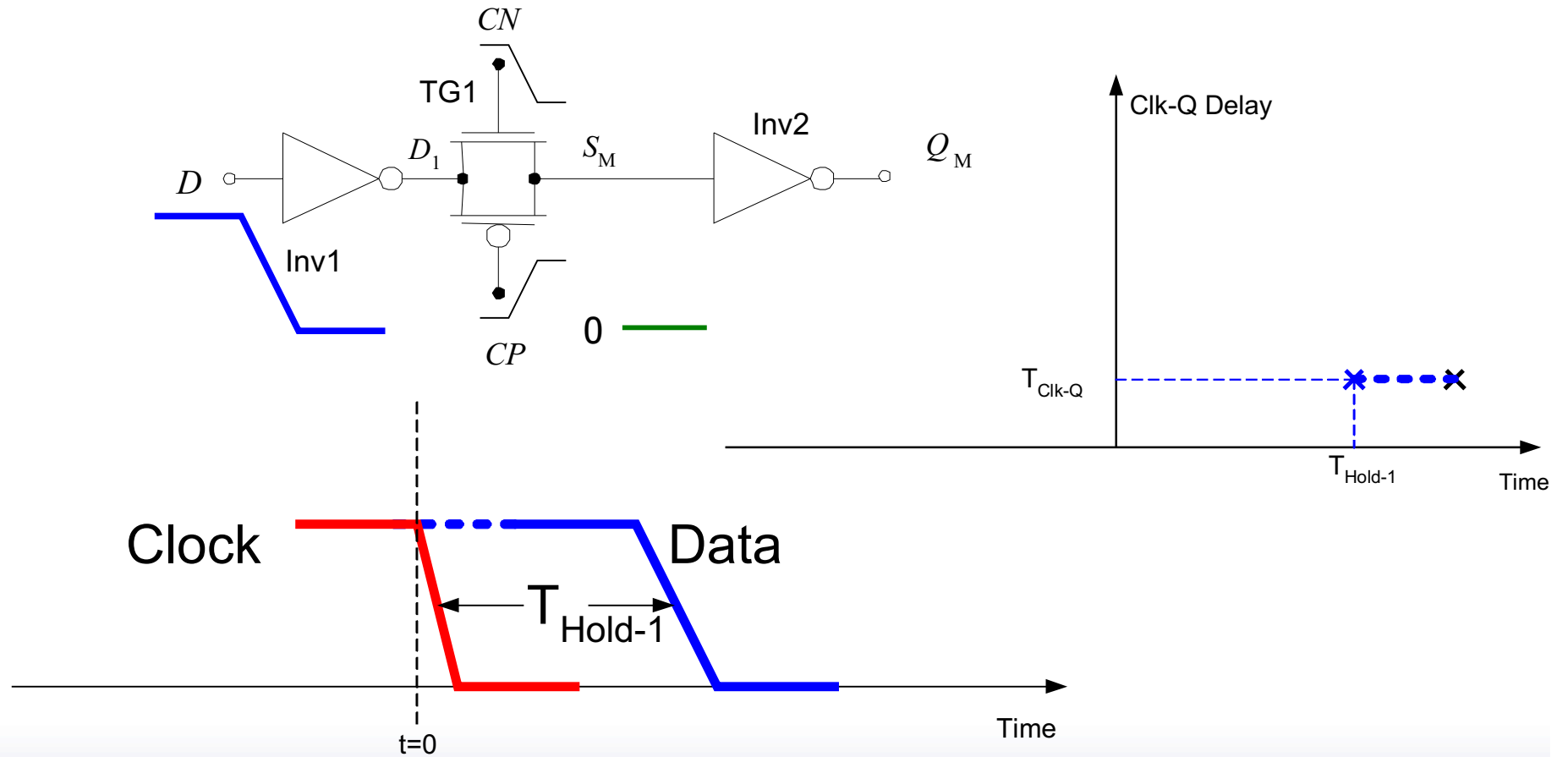


# Setup/Hold Time Illustrations

## Hold-1 case

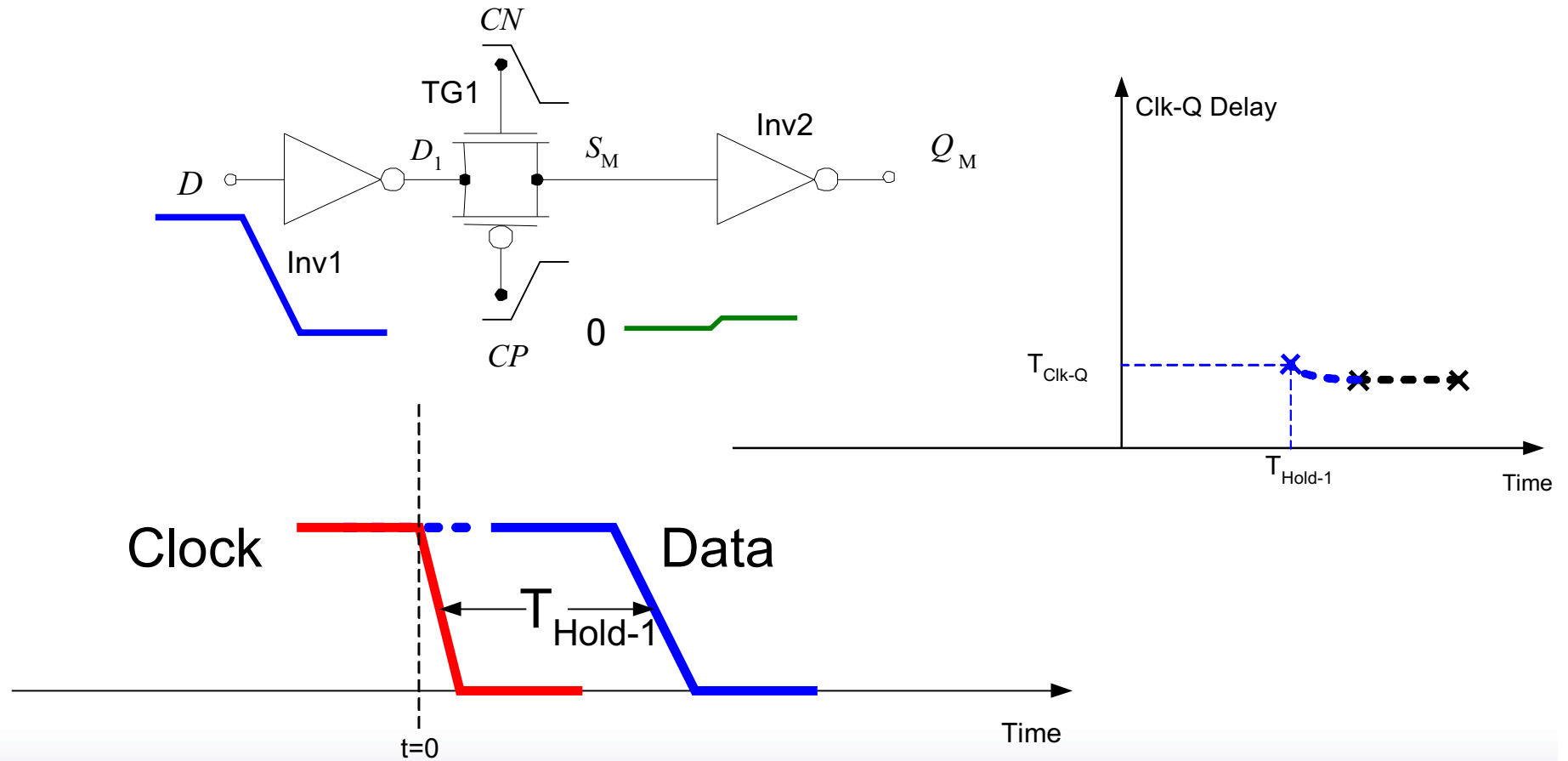


# Setup/Hold Time Illustrations

## Hold-1 case

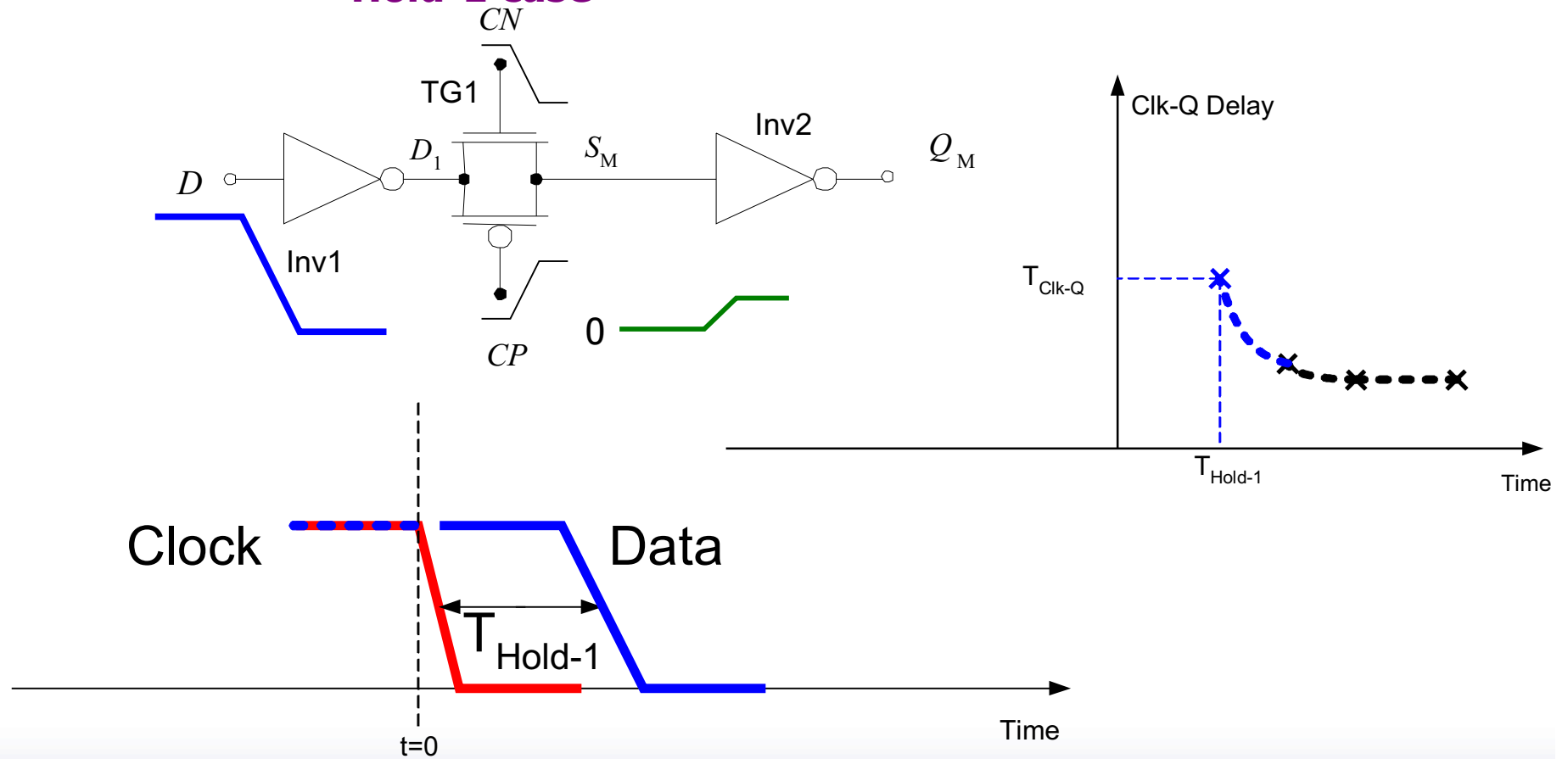


# Setup/Hold Time Illustrations

## Hold-1 case

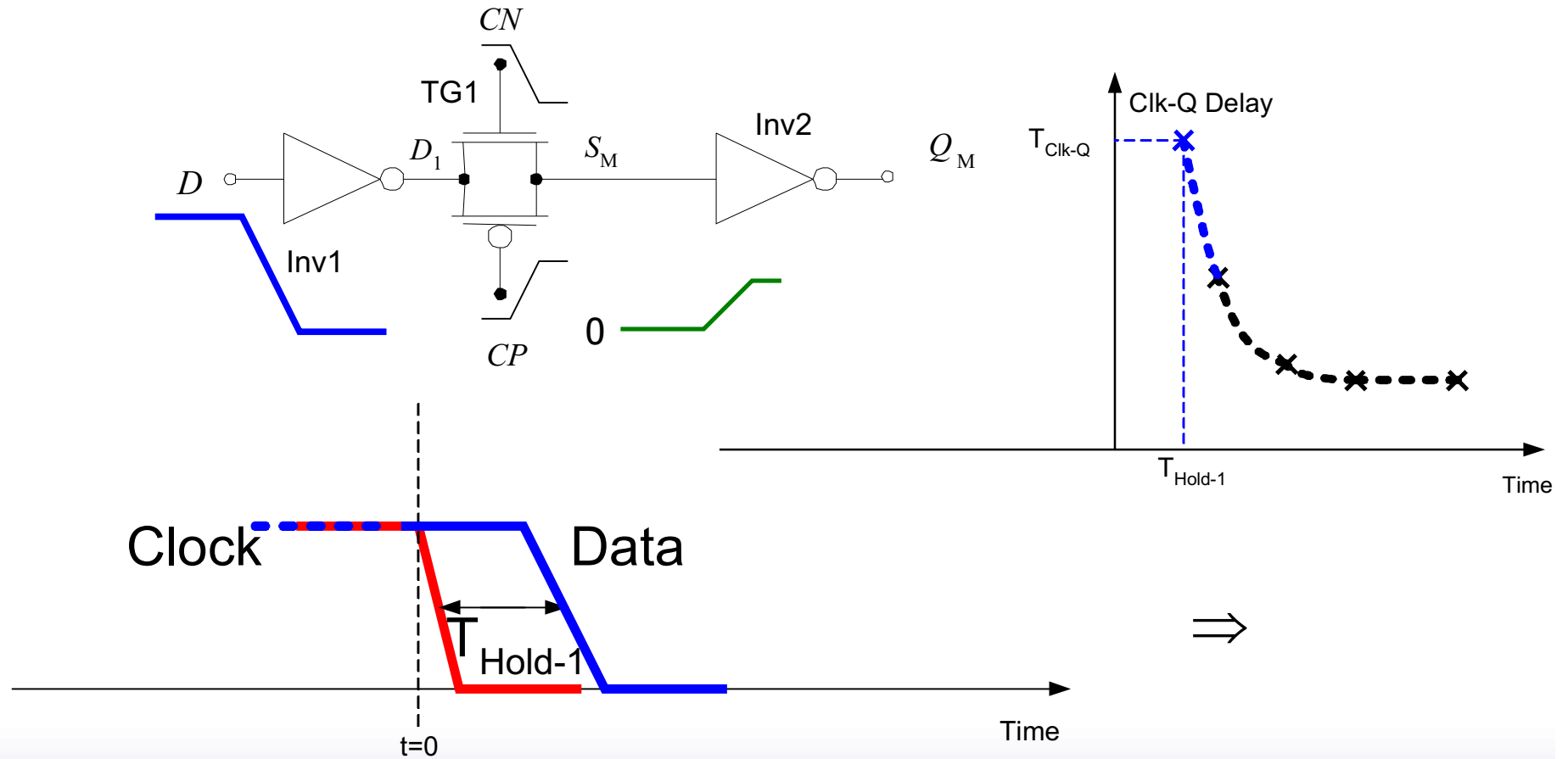

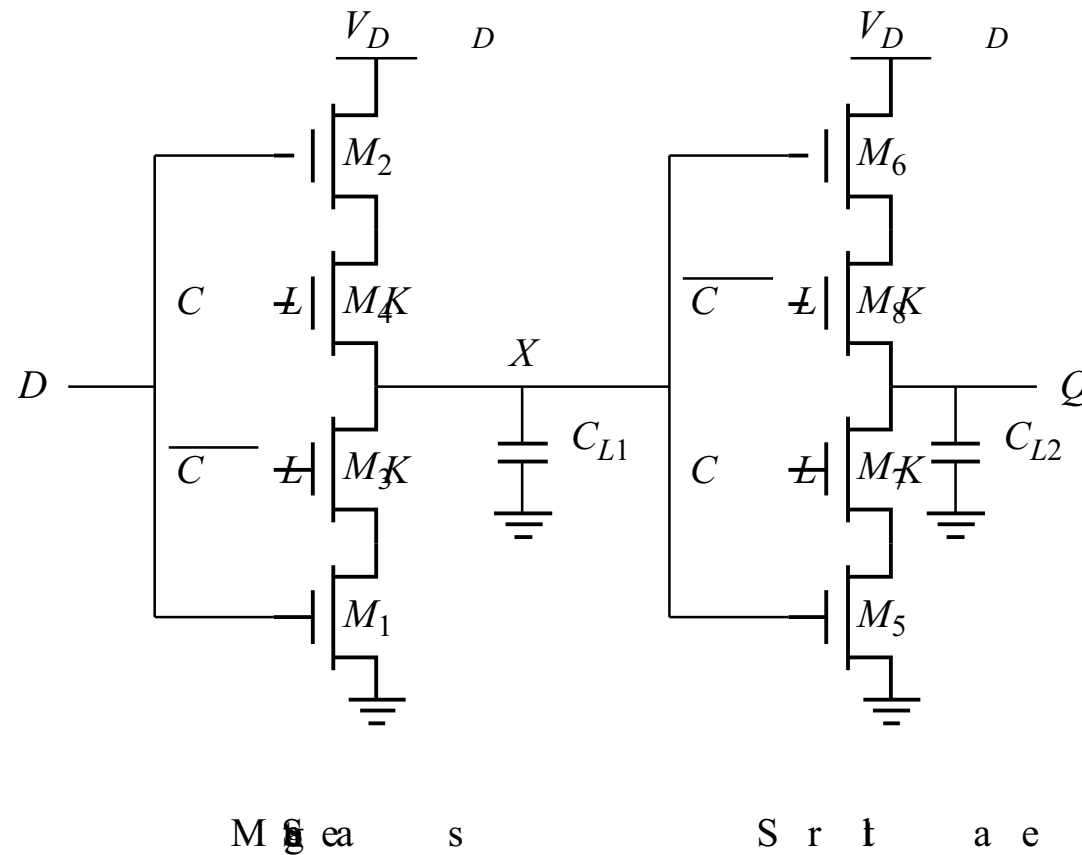
# Other Latches/Registers: C<sup>2</sup>MOS




“Keepers” can be added to make circuit pseudo-static


# *Inensitive to Clock-Overlap*

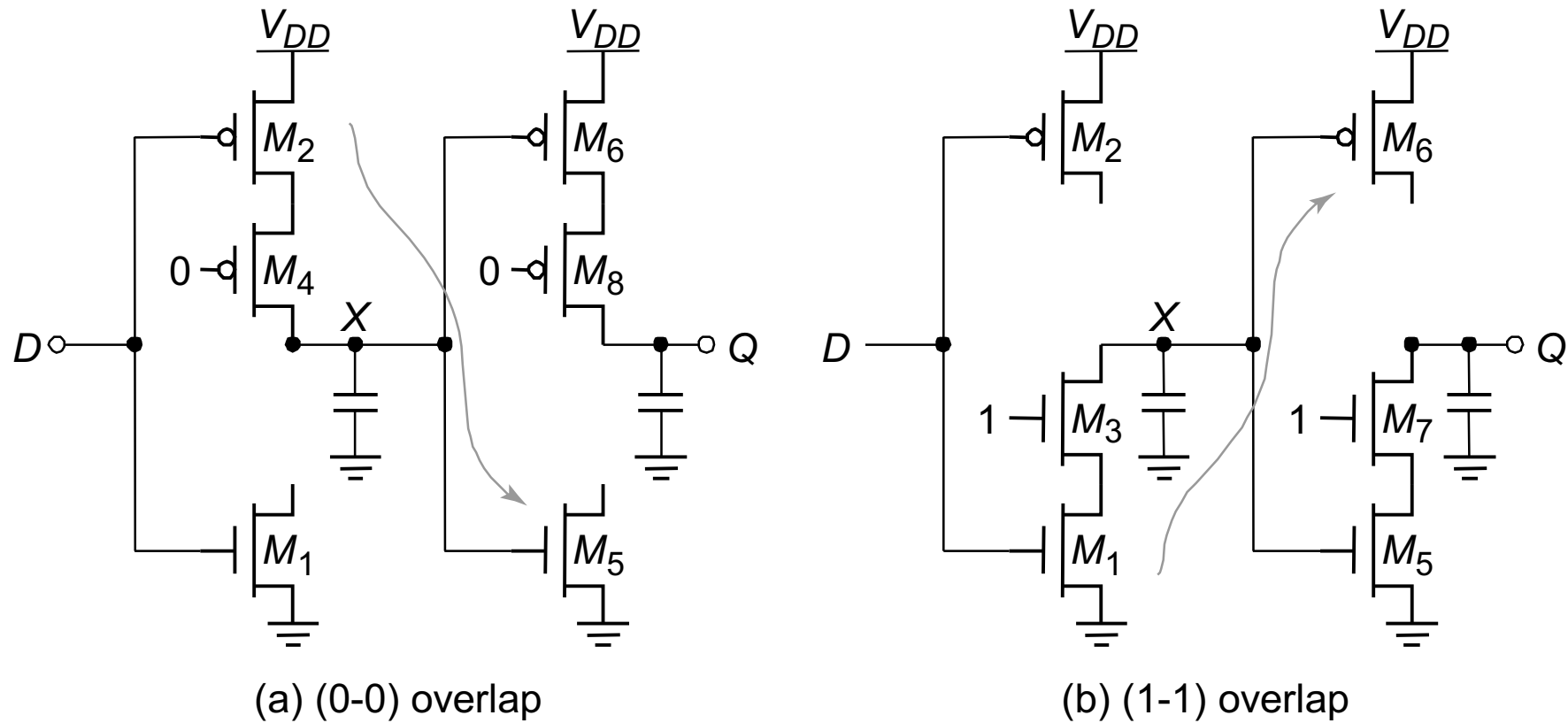

# Pipelining

 


Reference

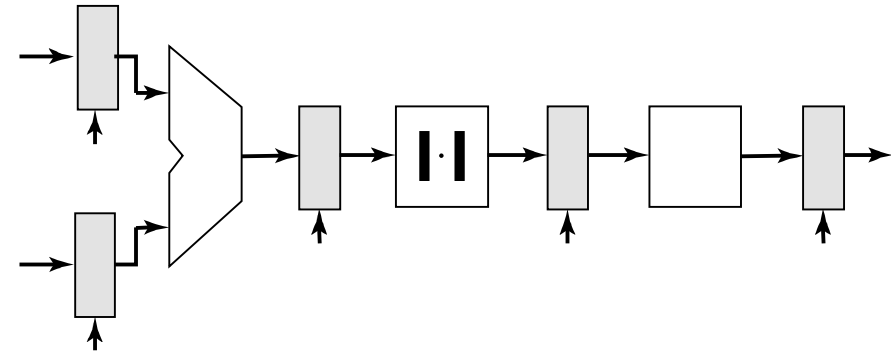

Pipelined


Clock Period	Adder	Absolute Value	Logarithm
1	$a_1 + b_1$		
2	$a_2 + b_2$	$ a_1 + b_1 $	
3	$a_3 + b_3$	$ a_2 + b_2 $	$\log(a_1 + b_1)$
4	$a_4 + b_4$	$ a_3 + b_3 $	$\log(a_2 + b_2)$
5	$a_5 + b_5$	$ a_4 + b_4 $	$\log(a_3 + b_3)$

# Other Latches/Registers: TSPC

 

Positive latch

(transparent when CLK= 1)

 

Negative latch


(transparent when CLK= 0)

# Pulse-Triggered Latches


## An Alternative Approach

Ways to design an edge-triggered sequential cell:



Master-Slave  
Latches

 


Pulse-Triggered  
Latch

 


# Latch-Based Pipeline

  

 
# Non-Bistable Sequential Circuits— Schmitt Trigger



 - VTC with hysteresis
- Restores signal slopes




# Noise Suppression: Schmitt Trigger

 




# Schmitt Trigger Simulated VTC

 


 Voltage-transfer characteristics with hysteresis.




The effect of varying the ratio of the PMOS device  $M_4$ . The width is  $k \cdot 0.5 \mu\text{m}$ .


# CMOS Schmitt Trigger (2)

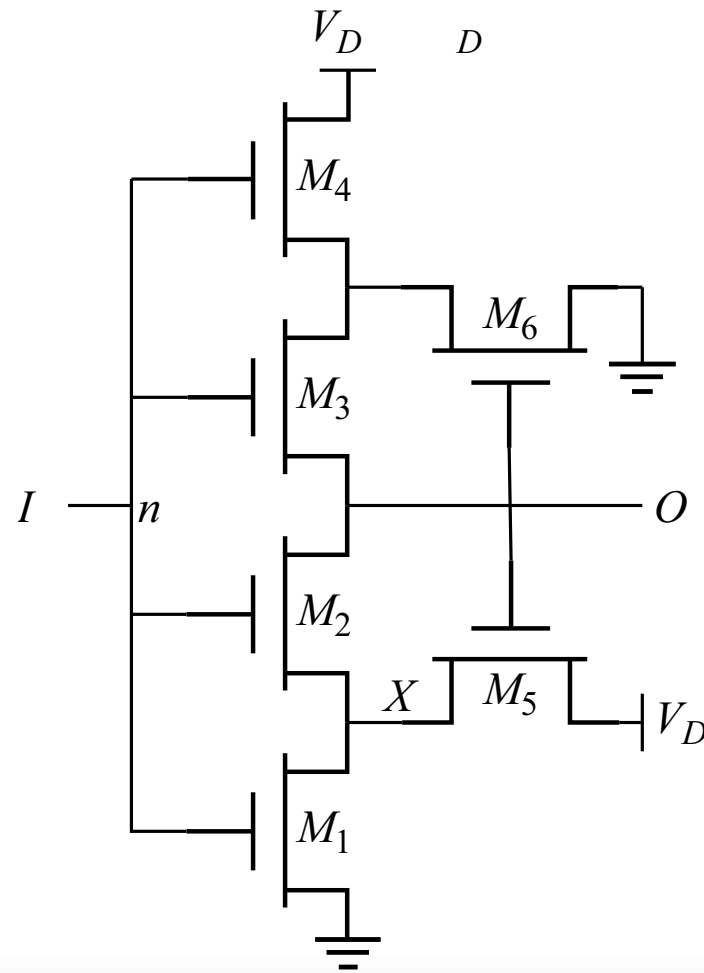


# Multivibrator Circuits

 

 **Bistable Multivibrator**  
flip-flop, Schmitt Trigger




**Monostable Multivibrator**  
one-shot

 


**Astable Multivibrator**  
oscillator


# Transition-Triggered Monostable

 

# Monostable Trigger (RC-based)


 


(a) Trigger circuit.

 


(b) Waveforms.

# Astable Multivibrators (Oscillators)

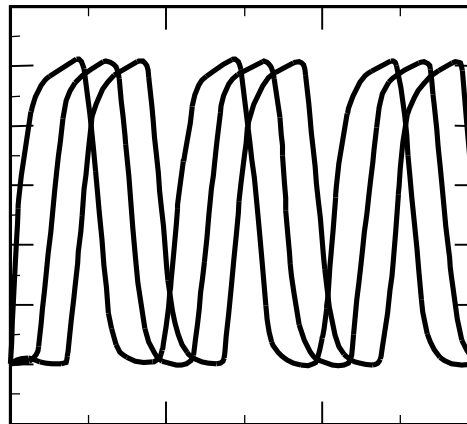 



simulated response of 5-stage oscillator

# Relaxation Oscillator

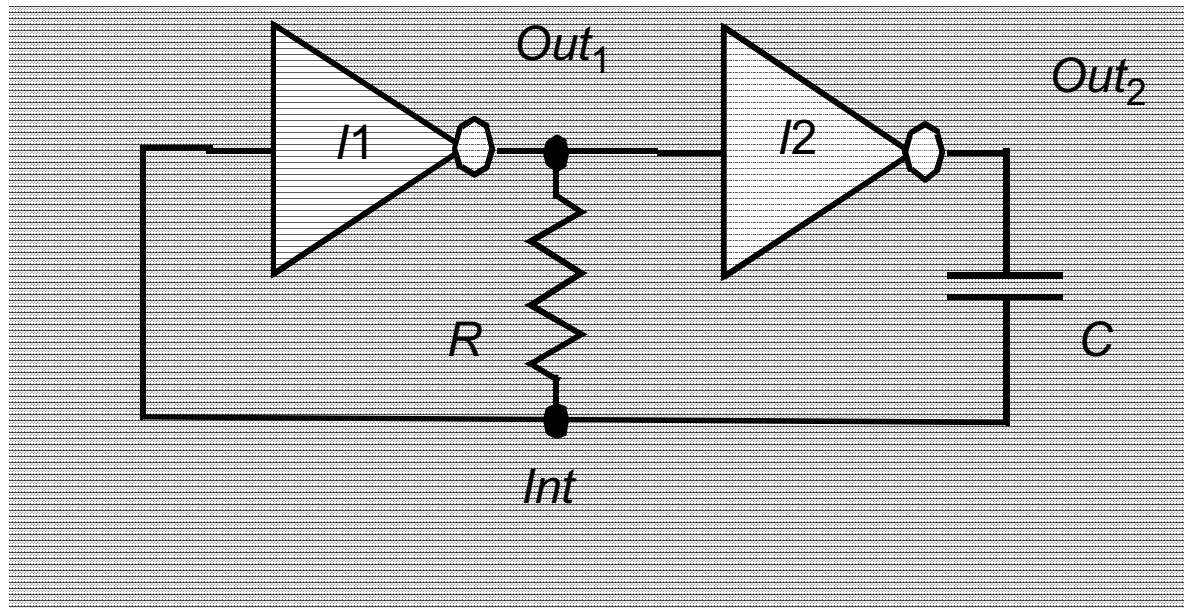


$$T = 2 (\log 3) RC$$

# Voltage Controller Oscillator (VCO)

 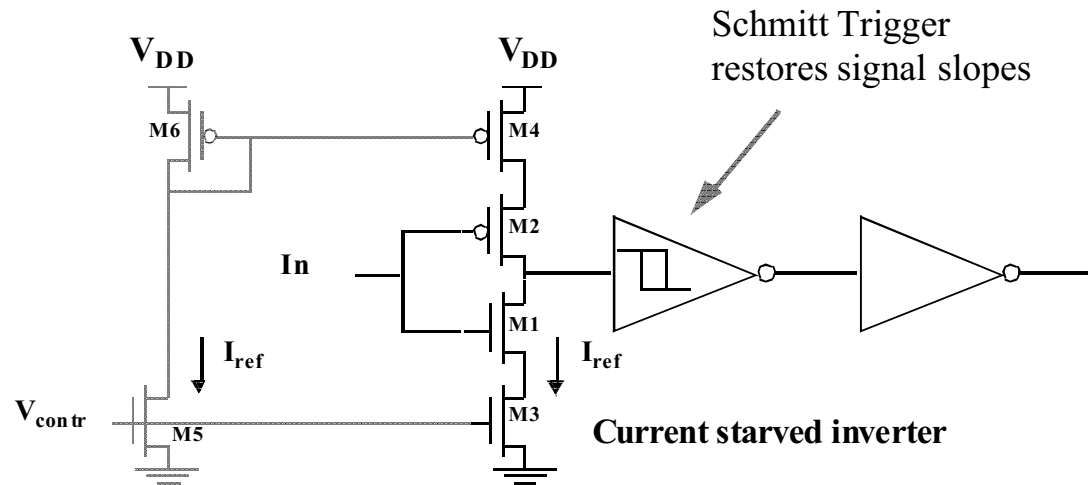


propagation delay as a function of control voltage


# Differential Delay Element and VCO

 

delay cell

 

two stage VCO

 

simulated waveforms of 2-stage VCO

# Homework 4

1. A common way to characterize registers is to measure the timing aperture which is the total window in which transitions on data are not correctly output. This is done by making two clocks which are close, but not the same so that the relative phase drifts slowly with each cycle. Construct a pseudo-static register, a C2MOS register, and a TSPC register in SUE with the assumption that the input is driven by a unit inverter (2/1, min width nmos), the clock is driven by a 2x inverter. Optimize your designs to minimize the timing aperture (setup+hold) and clock to Q assuming the output load is 2 inverters. Simulate your designs in SPICE and turn in both the designs (annotated schematics and spice results – plz. don't waste paper!)