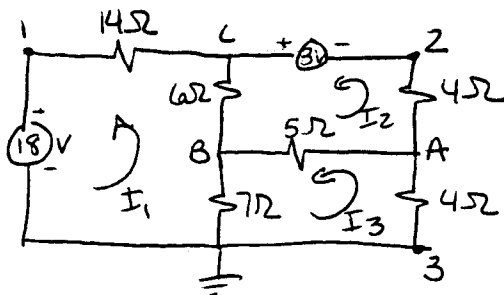


1. find ~~V_A~~ V_A, V_B, V_C



Constraints

$$V_1 = 18V$$

$$V_3 = 0V$$

Mesh

$$0 = -7\Omega(I_1 - I_3) - 6\Omega(I_1 - I_2) - 14\Omega I_1 - 18$$

$$0 = -4\Omega I_3 - 5\Omega(I_3 - I_2) - 7\Omega(I_3 - I_1)$$

$$0 = 4\Omega I_2 + 3V - 6\Omega(I_2 - I_1) - 5\Omega(I_2 - I_3)$$

$$-27I_1 + 6I_2 + 7I_3 = 18$$

$$7I_1 + 5I_2 - 16I_3 = 0$$

$$6I_1 - 15I_2 + 5I_3 = -3$$

$$I_1 = -.85 A$$

$$I_2 = -.297 A$$

$$I_3 = -.466 A$$


$$V_C = 18V + 14\Omega(.85) = 29.9V = V_C = 29.9V$$

$$V_A = 4\Omega(.466) = 1.864V = V_A$$

$$V_B = 7\Omega(.85 - .466) = 2.7V = V_B$$

2. Find the voltage and phase at V_A


Voltage due to 2V 10Hz source

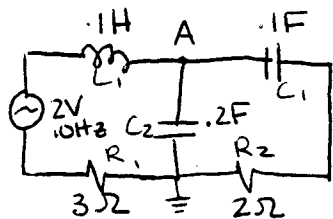

$$\omega = 10 \text{ Hz}$$

Combine C_1 & R_2 in ~~parallel~~ series
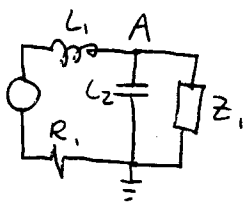
$$Z_{C_1 R_2} = 2 \Omega + \frac{1}{j\omega(1)} = Z_1$$



Combine L_2 & Z_1 in parallel

$$\frac{1}{Z_2} = j\omega(2) + \frac{1}{Z_1 + j\omega(1)}$$

$$Z_2 = 4.97 + j2.65 \quad .00312 - .0792j$$

$$V_A = \frac{1}{\sqrt{2}} Z_2 e^{i2\pi 10t} \left[\frac{Z_2}{Z_2 + R_1 + L_1} \right]$$

$$= \frac{1}{\sqrt{2}} Z_2 e^{i2\pi 10t} \left[\frac{.00312 - .0792j}{.00312 - .0792j + 3 + (20\pi)(1.1)j} \right]$$


$$= \frac{1}{\sqrt{2}} Z_2 e^{i2\pi 10t} (-.01015 - .00541j)$$

$$= \frac{1}{\sqrt{2}} Z_2 e^{i2\pi 10t} (.0115 e^{-2.65j})$$

$$V_A = .023 \sin(20\pi t - 2.65)$$

2 (cont)

Voltage due to 3V 15Hz source

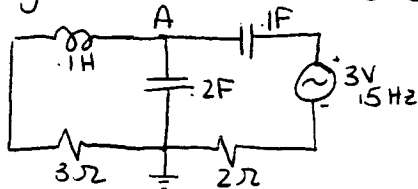

Combine .1H in series with 3Ω

$$Z_1 = (1)(2\pi 15)j + 3 = 9.42j + 3$$

Combine Z_1 in parallel w/ .2F

$$\frac{1}{Z_2} = j(30\pi \times .2) + \frac{1}{3 + 9.42j}$$

$$Z_2 = 1/87.3 \times 10^{-6} - .0533j$$

$$V_A = \text{Im} \left[\text{Re} \left[3e^{j30\pi t} \left(\frac{Z_2}{Z_2 + 2 + j(30\pi)j} \right) \right] \right]$$

$$= \text{Re} \left[3e^{j30\pi t} (.00216 - .0265j) \right]$$

$$= \text{Re} \left[3e^{j30\pi t} .0266e^{-1.49j} \right]$$

$$V_A = .0797 \frac{\cos}{\sin} (30\pi t - 1.49)$$

Superposition

$$V_{A_{\text{tot}}} = .0797 \frac{\sin}{\cos} (30\pi t - 1.49) + .023 \frac{\sin}{\cos} (20\pi t - 2.65)$$

3. find a general solution to

$$\begin{bmatrix} 2 & -3 \\ 4 & 6 \end{bmatrix} \begin{bmatrix} y_1 \\ y_2 \end{bmatrix} = \begin{bmatrix} y_1' \\ y_2' \end{bmatrix}$$

a. find the eigenvalues

$$\begin{vmatrix} 2-\lambda & -3 \\ 4 & 6-\lambda \end{vmatrix} = 0 = (2-\lambda)(6-\lambda) + 12$$

$$= 12 - 8\lambda + \lambda^2 + 12$$

$$= 24 - 8\lambda + \lambda^2$$

eigenvalues are $\lambda = 4 + 2\sqrt{2}i$; $4 - 2\sqrt{2}i$

find eigenvectors

$$\lambda = 4 + 2\sqrt{2}i$$

$$\begin{bmatrix} 2 - (4 + 2\sqrt{2}i) & -3 \\ 4 & 6 - (4 + 2\sqrt{2}i) \end{bmatrix} \rightarrow \begin{bmatrix} -2 - 2\sqrt{2}i & -3 \\ 4 & 2 - 2\sqrt{2}i \end{bmatrix}$$

$$\rightarrow \begin{bmatrix} 1 & \frac{1}{2} - \frac{\sqrt{2}}{2}i \\ 0 & 0 \end{bmatrix}$$

\therefore the eigenvector is

$$\begin{bmatrix} \frac{1}{2} - \frac{\sqrt{2}}{2}i \\ -1 \end{bmatrix}$$

$$\lambda = 4 - 2\sqrt{2}i$$

$$\begin{bmatrix} 2 - (4 - 2\sqrt{2}i) & -3 \\ 4 & 6 - (4 - 2\sqrt{2}i) \end{bmatrix} \rightarrow \begin{bmatrix} -2 + 2\sqrt{2}i & -3 \\ 4 & 2 + 2\sqrt{2}i \end{bmatrix}$$

$$\rightarrow \begin{bmatrix} 1 & \frac{1}{2} + \frac{\sqrt{2}}{2}i \\ 0 & 0 \end{bmatrix}$$

\therefore the eigenvector is

$$\begin{bmatrix} \frac{1}{2} + \frac{\sqrt{2}}{2}i \\ -1 \end{bmatrix}$$

$$\begin{pmatrix} y_1 \\ y_2 \end{pmatrix} = C_1 \begin{pmatrix} \frac{1}{2} - \frac{\sqrt{2}}{2}i \\ -1 \end{pmatrix} e^{(4+2\sqrt{2}i)t} + C_2 \begin{pmatrix} \frac{1}{2} + \frac{\sqrt{2}}{2}i \\ -1 \end{pmatrix} e^{(4-2\sqrt{2}i)t}$$