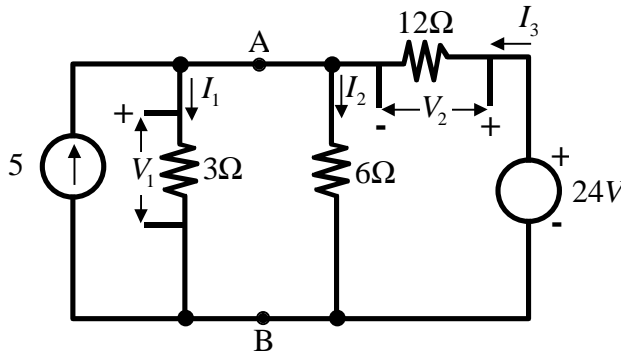


Kirchoff's Laws Direct:

$$\text{KCL, KVL, Ohm's Law} \Rightarrow V = IR \Rightarrow VG = I \\ G = R^{-1}$$

$$\text{Ohm's Law: } V_1 = 3 \cdot I_1 = 6 \cdot I_2 \\ V_2 = 12 \cdot I_3$$

(always get 1 equation/Resistor)



KCL:

$$\left. \begin{aligned} \text{A: } -5 + I_1 + I_2 - I_3 &= 0 \\ \text{B: } 5 - I_1 - I_2 + I_3 &= 0 \end{aligned} \right\} \text{ eq. are dependent}$$

(in general, get $n-1$ indep. for nodes)

$$\text{KVL: } -V_1 + 24 - V_2 = 0 \quad \text{write 1 loop equation for each loop with a voltage not in the current set of equations.}$$

\Rightarrow Eliminate either V_1 or I using Ohm's Law


$$\text{eq: A: } -5 + \frac{V_1}{3} + \frac{V_1}{6} - \frac{V_2}{12} = 0 \\ \Rightarrow \begin{bmatrix} \frac{1}{3} + \frac{1}{6} & -\frac{1}{12} \\ -1 & -1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 5 \\ 24 \end{bmatrix}$$

$$\text{KVL: } -V_1 + 24 - V_2 = 0$$

Cramer's Rule: $[A] \cdot \bar{X} = \bar{B}$

$$X_i = \frac{\text{Det}[A^{0..i-1} | B | A^{i+1..N}]}{\text{Det}[A]}$$

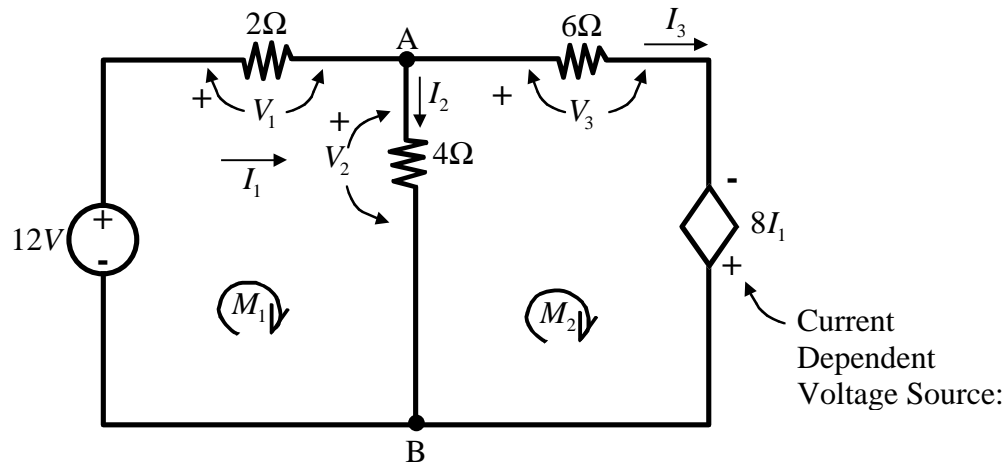We can always write in terms of only V , or I variables using ohm's law:




KCL: $A: -I_1 + I_2 + I_3 = 0$

KVL: $M_1: -12 + 2I_1 + 4I_2 = 0$

$M_2: -4I_2 + 6I_3 - 8I_1 = 0$

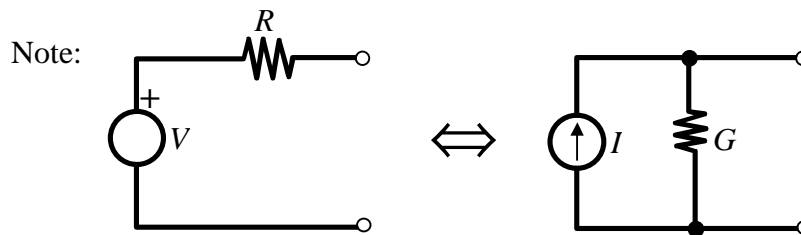
$$\begin{bmatrix} -1 & 1 & 1 \\ 2 & 4 & 0 \\ -8 & -4 & 6 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 12 \\ 0 \end{bmatrix}$$



if $V = IR$
 $R = G^{-1}$

Rules for nodes:

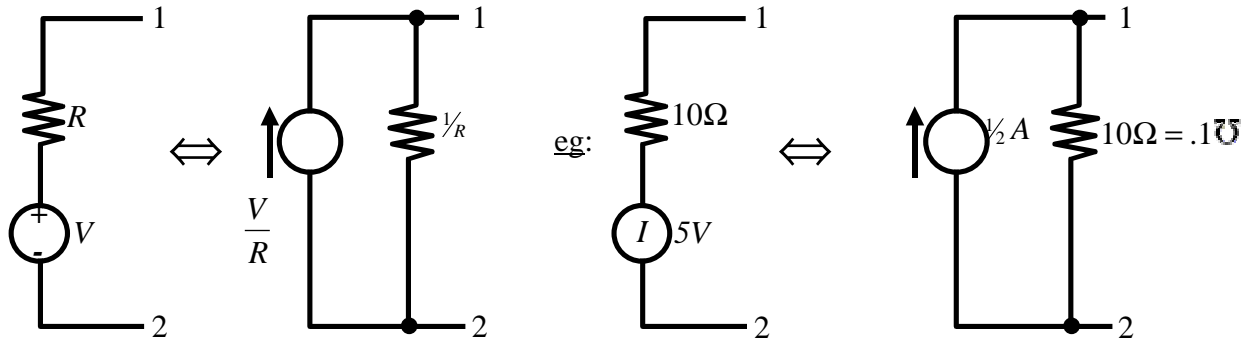- 1) Convert all voltage to current sources



- 1) Determine a reference node and identify unknown relative voltages


- 2) Use KCL at each unknown node:

$$\begin{aligned} \text{at node A: } & G_{AA}V_A - G_{AB}V_B - \dots - G_{AN}V_N = I_A \\ \text{B: } & -G_{AB}V_A + G_{BB}V_B - \dots - G_{BN}V_N = I_B \\ \text{N: } & -G_{AN}V_A + G_{BN}V_B - \dots - G_{NN}V_N = I_N \end{aligned}$$

where: $G_{ii} = \Sigma$ all conductances connected to node i
 $G_{ji} = \Sigma$ all conductances between node i and node j
 $I_i = \Sigma$ all current sources connected to node i

\Rightarrow Define N equations in N unknowns

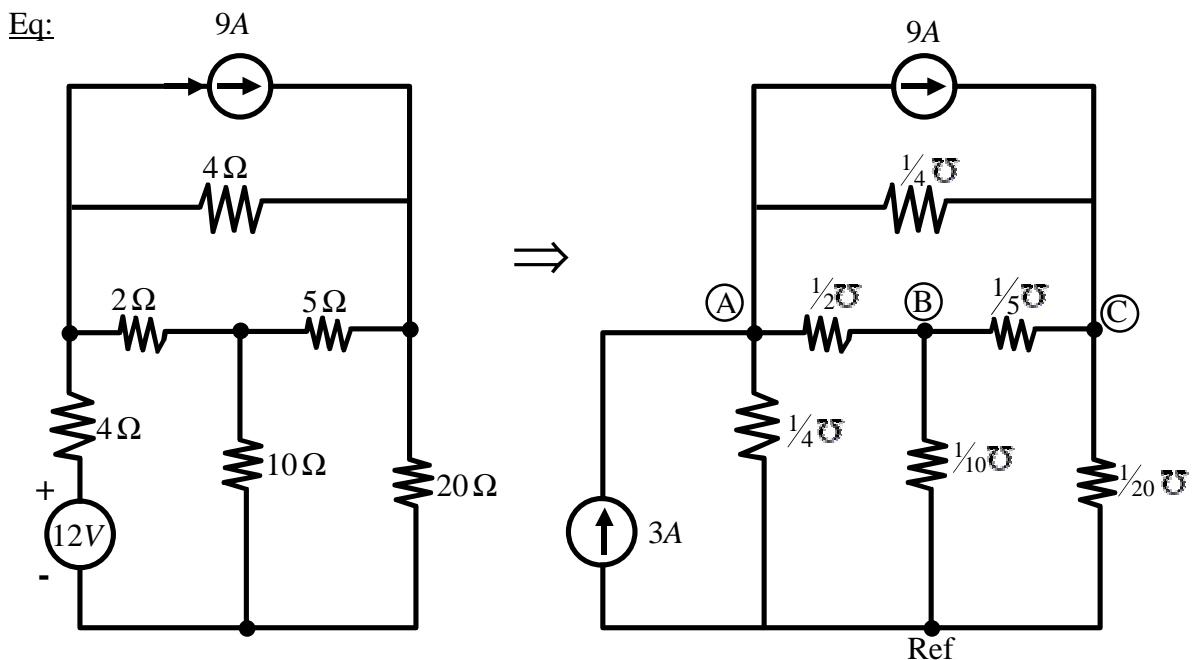all other voltages and currents by Ohm's Law from V and S .



$$\text{A: } (0.25 + .5 + .25)V_A - 0.5V_B - 0.25V_C = 3 - 9 \text{ (A)}$$

$$\text{B: } -0.5V_A + (0.5 + 0.1 + 0.2)V_B - .02V_C = 0$$


$$\text{C: } -0.25V_A - 0.2V_B + (0.2 + 0.25 + 0.05)V_C = 9$$

$$\Rightarrow \begin{bmatrix} 1.0 & -0.5 & -2.5 \\ -0.5 & .8 & -0.2 \\ -0.25 & -0.2 & .5 \end{bmatrix} \begin{bmatrix} V_A \\ V_B \\ V_C \end{bmatrix} = \begin{bmatrix} -6 \\ 0 \\ 9 \end{bmatrix}$$

$$\Rightarrow V_A = 4V \quad V_B = 8.33V \quad V_C = 23.3V$$

One can also solve for N independent currents in N meshes

Consider:

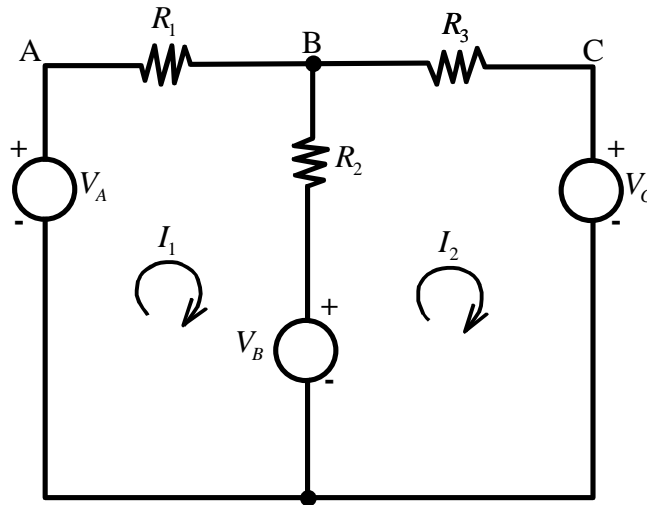

We know that KVL \Rightarrow
voltages around a loop = 0.

Current I_1 flows in a simple mesh.

$$I_1: I_1 \cdot R_1 + I_1 \cdot R_2 - I_2 \cdot R_2 + V_B - V_A = 0$$

$$I_2: I_2 \cdot R_3 + I_2 \cdot R_2 - I_1 \cdot R_2 + V_C - V_B = 0$$

We can as usual re-arrange to a form that can be written by inspection:

$$\begin{aligned} 1: (R_1 + R_2)I_1 - R_2I_2 &= V_A - V_B \\ 2: -R_2I_1 + (R_2 + R_3)I_2 &= V_B - V_C \end{aligned} \Rightarrow \begin{bmatrix} R_1 + R_2 & -R_2 \\ -R_2 & R_2 + R_3 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} V_A - V_B \\ V_B - V_C \end{bmatrix}$$

* Note that KCL is always solved implicitly since at each node we have a sum of currents in meshes: each mesh enters and leaves with the same current.

In general:

- 1) Connect each current source with parallel res. to voltage source with series R .
- 2) Select a current variable and mesh for each simple loop (usually we traverse each loop in same direction, ie, clockwise).
- 3) Use KVL for each loop in terms of the mesh current variable.

iff no dependent sources:


$$\begin{aligned} 1: & \quad R_{11}I_1 - R_{12}I_2 - \dots - R_{1N}I_N = V_1 \\ 2: & \quad -R_{12}I_1 - R_{22}I_2 - \dots - R_{2N}I_N = V_2 \\ N: & \quad -R_{1N}I_1 - R_{2N}I_2 - \dots - R_{NN}I_N = V_N \end{aligned}$$

R_{ii} = sum of all resistance in mesh I

R_{ij} = sum of all common resistance to meshes I, J

V_i = sum of voltage rises in mesh I , in direction of current I_i

Eq: A Wheatstone Bridge

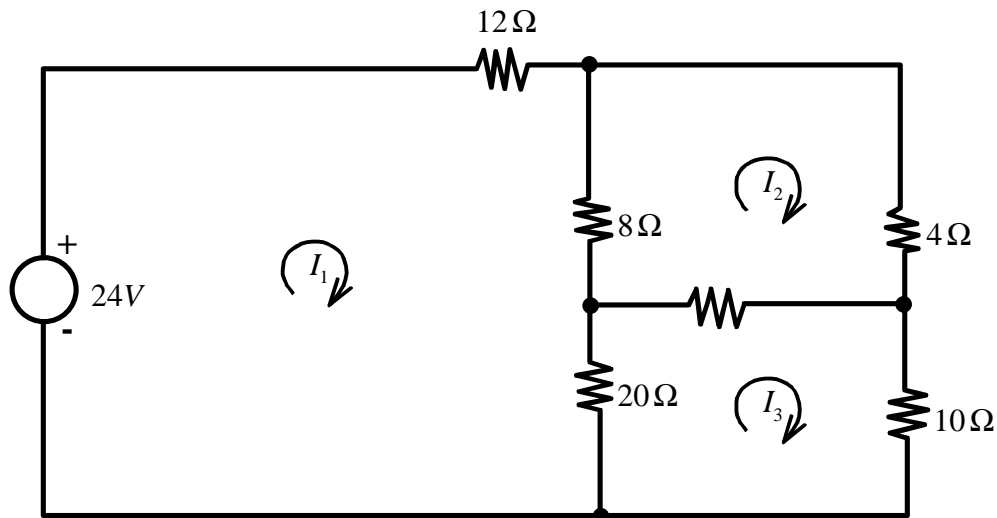

$$\begin{aligned} \Rightarrow & \quad (12 + 8 + 20)I_1 - 8I_2 - 20I_3 = 24 \\ & \quad -8I_1 + (8 + 4 + 6)I_2 - 6I_3 = 0 \\ & \quad -20I_1 - 6I_2 + (20 + 6 + 10)I_3 = 0 \end{aligned}$$

$$\begin{bmatrix} 40 & -8 & -20 \\ -8 & +18 & -6 \\ -20 & -6 & +36 \end{bmatrix} \cdot \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 24 \\ 0 \\ 0 \end{bmatrix}$$

How to solve this system?

⇒ Gaussian Elimination to Triangular form:

$$\begin{array}{l} 1: \\ 2: \\ 3: \end{array} \begin{bmatrix} 20 & -4 & -10 \\ -4 & 9 & -3 \\ -10 & -3 & 18 \end{bmatrix} = \begin{bmatrix} 12 \\ 0 \\ 0 \end{bmatrix} \quad (\text{divide both sides by 2})$$

$$3 \cdot \frac{5}{9} = \left[\frac{-80}{9} \quad \frac{-5}{3} \quad +10 \right] [0]$$

$$\begin{array}{l} 1' \\ 2 \\ 3 \end{array} \begin{bmatrix} \frac{130}{9} & \frac{-17}{3} & 0 \\ -4 & 9 & -3 \\ -10 & -3 & 18 \end{bmatrix} = \begin{bmatrix} 12 \\ 0 \\ 0 \end{bmatrix}$$

$$3 \cdot \frac{1}{6} = \left[\frac{-10}{6} \quad \frac{1}{2} \quad 3 \right] = [0]$$

$$\begin{array}{l} 1' \\ 2' \\ 3 \end{array} \begin{bmatrix} \frac{130}{9} & \frac{-17}{3} & 0 \\ \frac{-17}{5} & \frac{17}{2} & 0 \\ -10 & -3 & 18 \end{bmatrix} = \begin{bmatrix} 12 \\ 0 \\ 0 \end{bmatrix}$$

$$2' \cdot \frac{2}{17} \cdot \frac{17}{3} = 2' \cdot \frac{2}{3} = \left[\frac{-34}{9} \quad \frac{17}{3} \quad 0 \right]$$

$$\begin{array}{l} 1' \\ 2'' \\ 3 \end{array} \begin{bmatrix} \frac{96}{9} & 0 & 0 \\ \frac{-17}{3} & \frac{17}{2} & 0 \\ -10 & -3 & 18 \end{bmatrix} = \begin{bmatrix} 12 \\ 0 \\ 0 \end{bmatrix}$$

$$\Rightarrow \frac{96}{9} \cdot I_1 = 12V \quad I_1 = \frac{5}{4}A$$


$$\text{Then } 2' = \frac{+17}{3} \cdot \frac{5}{4} = \frac{17}{2} \cdot I_2 \Rightarrow I_2 = \frac{3}{4}A$$

$$3' \Rightarrow +10 \cdot \frac{5}{4} + 3 \cdot \frac{3}{4} = 18 \cdot I_3 \quad \Rightarrow I_3 = \frac{3}{4}A$$

Dependent Voltage & Current Sources:

We model the activity of many active components by use of a “programmable” voltage or current source whose strength is a function of the voltage or currents elsewhere in the circuit:

Eq:

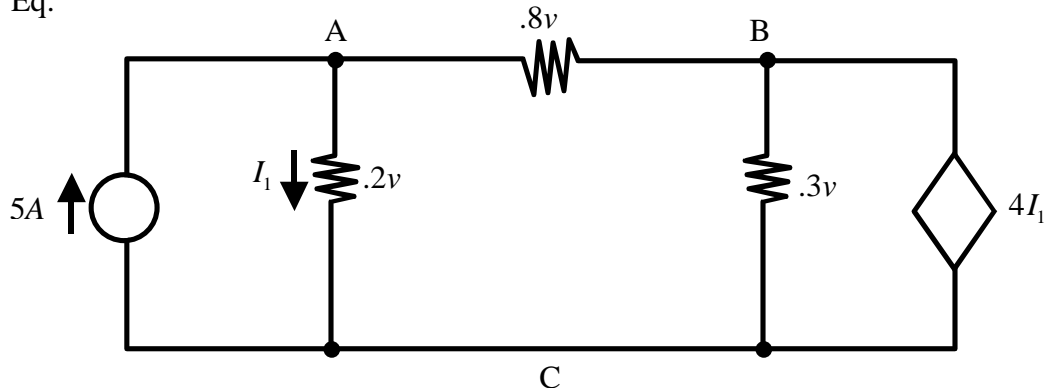

if we choose B as the reference node \Rightarrow

$$\text{A: } (.8 + .2)V_A - .2V_C = 5$$


$$\text{C: } -(.2)V_A + (.2 + .3)V_C = -5 + 4I_1$$

$$\text{now } I = 0.2 \cdot (V_A - V_C)$$

$$\Rightarrow \begin{bmatrix} 1 & -.2 \\ -1 & 1.3 \end{bmatrix} \begin{bmatrix} V_A \\ V_C \end{bmatrix} = \begin{bmatrix} 5 \\ -5 \end{bmatrix}$$

Superposition for Circuits

Consider:

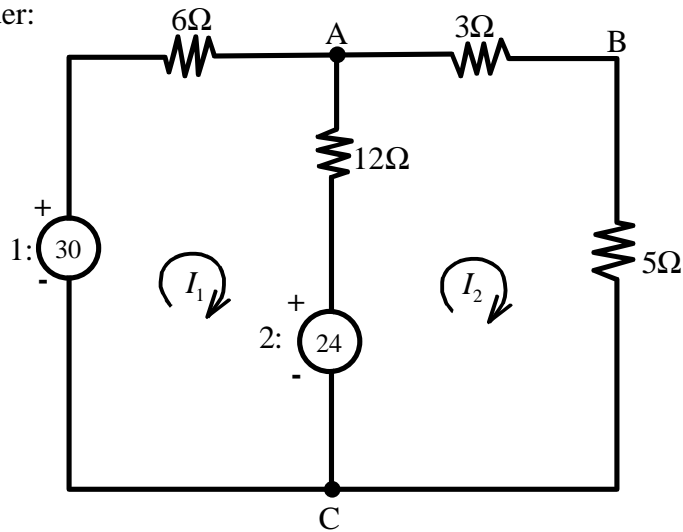


We could solve this by either node or mesh analysis, but there may be a simpler approach:

If we suppress source #1 (i.e. make a short circuit) we can find I'_1, I'_2 . Similarly, I_1, I_2 could be written without source #2.

Total currents and voltages superpose \Rightarrow suppress one at a time and then superpose the results:

Suppress 1:

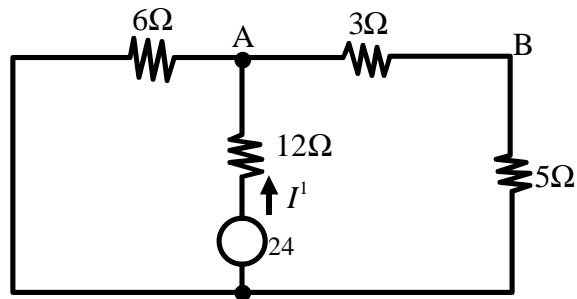


$$\Rightarrow 24V = (12 + 6 \parallel (3 + 5)) \cdot I'$$

$$\text{So } I' = \frac{7}{108} \cdot 24 = \frac{14}{9} A \Rightarrow V'_A = \frac{56}{3} + 24 \text{ volt}$$

$$I'_1 = \frac{-128}{18} \quad I'_2 = \frac{128}{18}$$

Now: Suppress I_2 , run I_1

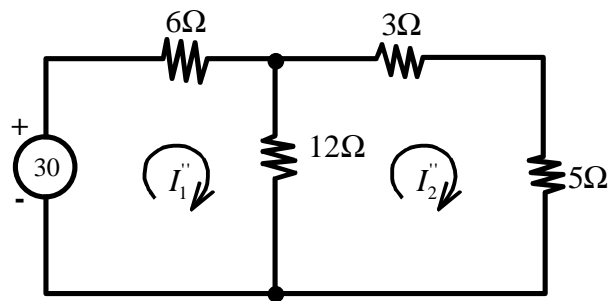


$$30V = (6 + 12 \parallel (8)) \cdot I_1''$$

Exponential Excitation of circuits: Admittance & Impedance

Idea: Exponential function is easy to analyze \Rightarrow
 simple to add/multiply/integrates, etc.
 Also is a common case for circuit excitation

Consider:

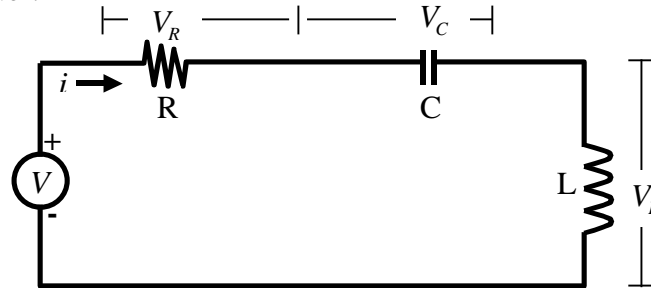

where $V = Ae^{st}$ for complex s , A , real t .

We know all currents are same in circuit, $V_R + V_C + V_L = V$ KVL

$$V_R = i(t) \cdot R \quad V_C = \frac{1}{C} \cdot \int i(t) dt \quad V_L = L \frac{di(t)}{dt}$$

or

$$i_R(t) = \frac{V_R(t)}{R} \quad i_C(t) = C \frac{dV_C(t)}{dt} \quad i_L(t) = \frac{1}{L} \int V_C(t) dt$$

for our circuit $V(t) = Ae^{st} \Rightarrow V_R(t) = A' e^{st}$, $V_C(t) = A'' e^{st} \dots$

where: $Ae^{st} = (A' + A'' + A''')e^{st}$ KVL

we have $i_R(t) = \frac{A'}{R} e^{st}$ $i_C(t) = C \cdot A'' \cdot s e^{st}$ $i_L = \frac{A'''}{sL} e^{st}$


Note: for this kind of excitation, $i_L(t) = C \cdot A'' \cdot s e^{st}$
 $= sC \cdot V_C(t)$

$$i_L(t) = \frac{1}{sL} V_L(t)$$


$$i_R(t) = \frac{1}{R} V_R(t)$$

So: sC has same units/behavior as $\frac{1}{R}$: conductance.

Eg. 2:

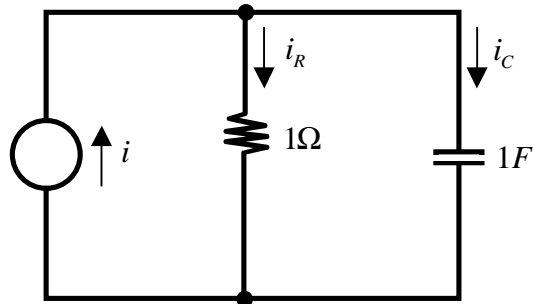

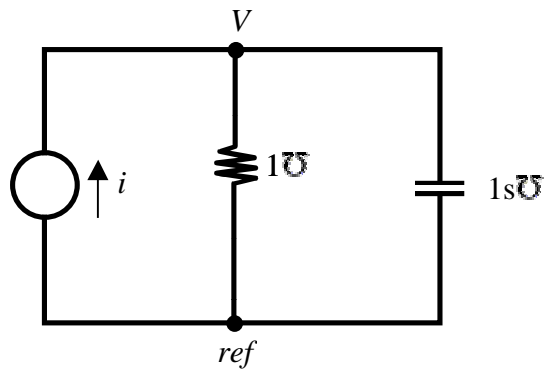Parallel \Rightarrow admittances \Rightarrow



$$1 = \frac{V}{1} + sV$$

$$\Rightarrow V = \frac{I}{1+s}$$

for $i(t) = 10e^{-2t}$ $s = -2, A = 10$

$$V = \frac{10}{1-2} = -10e^{st} = -10e^{-2t} \text{ volts}$$

Sinewave (Sinusoidal) excitation:

We know: $e^{io} = \cos o + i \sin o$

$$\Rightarrow \cos o = \frac{e^{io} + e^{-io}}{2} \quad \sin o = \frac{e^{io} - e^{-io}}{2i}$$

We wish to study circuits with excitation: $v(t) = V \cos(\omega t + \phi)$

$$= \frac{V}{2} (e^{i\omega t + i\phi} + e^{-i\omega t - i\phi}) = v_1 e^{i\omega t} + v_2 e^{-i\omega t}$$

$$v_1 = \frac{V}{2} e^{i\phi} \quad v_2 = \frac{V}{2} e^{-i\phi}$$

note V is complex.

		R	C	L
We define:	<u>Admittance</u>	$\frac{1}{R}$	sC	$\frac{1}{sL}$
	<u>Impedance</u>	R	$\frac{1}{sC}$	sL

for $s = i\omega$	(sinusoid case)	$\frac{1}{R}$	$i\omega C$	$\frac{1}{i\omega L}$
		R	$\frac{1}{i\omega C}$	$i\omega L$

Admittances compose like conductances, Impedances compose like resistances.

$$\text{So for our circuit: } v(t) = R \cdot i(t) + L \cdot \frac{di(t)}{dt} + \frac{1}{C} \int i(t) dt$$

$$\text{for } i(t) = I e^{st}$$

$$\Rightarrow v(t) = (R \cdot I + L \cdot I \cdot s + \frac{I}{sC}) e^{st}$$

$$\text{or } I = \frac{V}{R + Ls + \frac{1}{sC}} = \frac{V}{z(s)}$$

we write impedances as $Z(s)$, admittance as $Y(s)$

$$\text{so } i(t) = I e^{st} = \frac{V}{R + Ls + \frac{1}{sC}} \cdot e^{st}$$


$$\text{eg: if } V = 10 \cdot e^{-2t} \quad (10V @ t = 0 \rightarrow \text{decreasing})$$

$$R = 1\Omega \quad L = \frac{1}{2}H \quad C = \frac{1}{2}F$$

$$i(t) = \frac{10}{1 + \frac{s}{2} + \frac{2}{s}} e^{st} = -10e^{-2t} \text{ (Amps)}$$

Basic Trick: Extend the circuit techniques for node and mesh analysis to also handle Impedance and Admittances

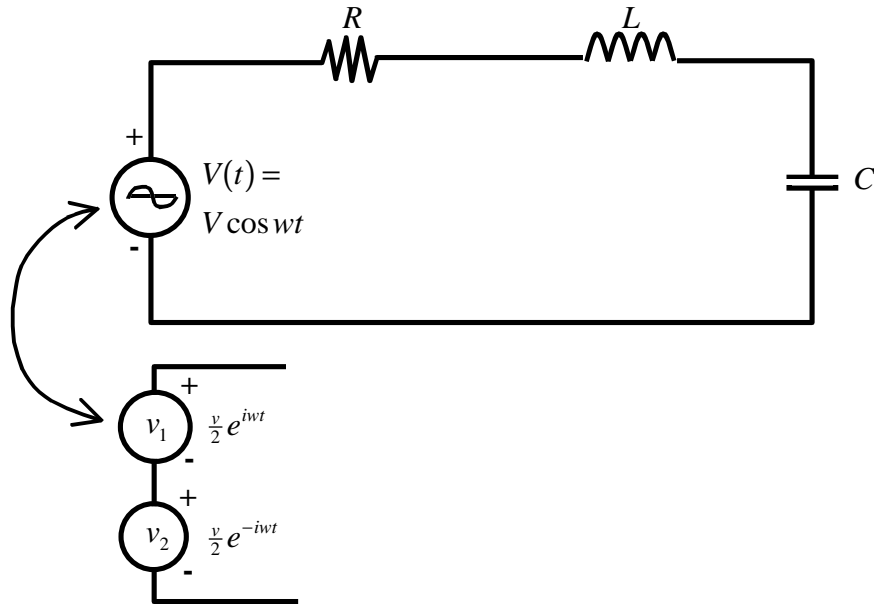\Rightarrow generalize circuits which can be analyzed.



note: we can apply superposition to solve this:

suppress v_1 or v_2 and solve for other.

$$I_1 = \frac{\frac{V}{2}}{R + i\omega L + \frac{1}{i\omega C}} \quad I_2 = \frac{\frac{V}{2}}{R - i\omega L + \frac{1}{-i\omega C}}$$

if we write I_1, I_2 in exponential complex form:

$$I_1 = I_1 e^{i\sigma_1} \quad I_2 = I_2 e^{i\sigma_2}$$

$$\text{we get: } I_1 = I_2 = \frac{\frac{V}{2}}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}} \quad \sigma_1 = -\tan^{-1}\left(\frac{\omega L - \frac{1}{\omega C}}{R}\right) = -\sigma_2$$

$$i_1(t) = I_1 e^{i\sigma_1} e^{i\omega t} \dots$$

$$i_1(t) = i_1 + i_2 = I_1 \left(e^{i(\omega t + \sigma_1)} + e^{-i(\omega t - \sigma_1)} \right)$$

$$= \frac{V}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}} \cdot \cos(\omega t + \sigma_1)$$

I, V are called Phasors