

Homework #4


Due: Wed. at beginning of class.

Reading: Handout

Ref: Ma 5a Text, ECE 2a text

1. The following differential equation has one solution that is a polynomial in x , -- find the polynomial solution: $(2x - 3x^3)y'' + 4y' + 6xy = 0$

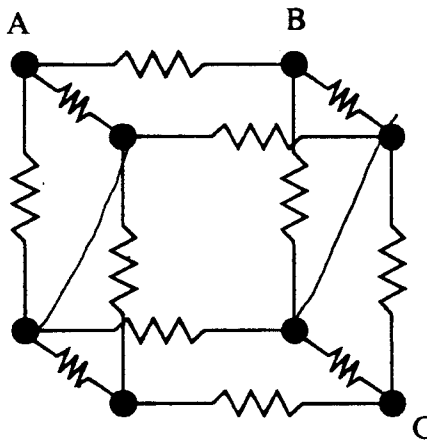2. Consider the following resistor network:



Given that all resistors are 1Ω , find the resistances between nodes:

- A to B
- A to C
- B to C

(Hint: use symmetry to find nodes that must be at a common potential.)

3. Suppose a $2A$ current source is placed so that a positive current flows into node A and out of node C, and that a $3A$ source is placed so that a positive current flows into node A and out of node B. What voltage will appear between points B and C? (Hint: use superposition!)

1. Find a polynomial solution to

$$(2x-3x^3)y''+4y'+6xy=0$$

Assume y is of the form $y = Ax^2 + Bx + C$

$$y' = 2Ax + B$$

$$y'' = 2A$$

plug back into ~~original~~ equation

$$2A(2x-3x^3) + 4(2Ax+B) + 6x(Ax^2+Bx+C) = 0$$

$$x^3(-6A+6A) + x^2(6B) + x(4A+8A+6C) + 4B = 0$$

$$4B = 0$$

$$12A + 6C = 0$$

$$6B = 0$$


$$\therefore B = 0$$

$$12A = -6C$$

$$C = -2A$$


$$\boxed{\therefore y = Ax^2 - 2A}$$

2. Resistor Cube

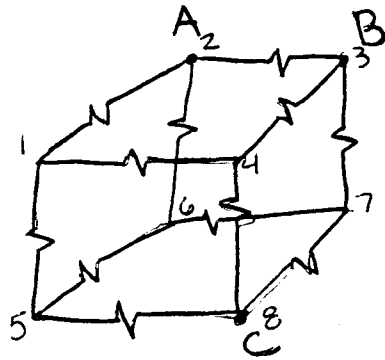

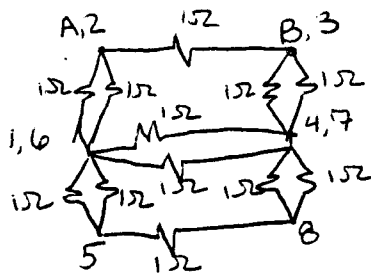
a) Find the resistance from A → B

from symmetry it is known that nodes 1 & 6 are at the same potential and can be shorted together as can nodes 4 and 7




combine all the resistors in parallel
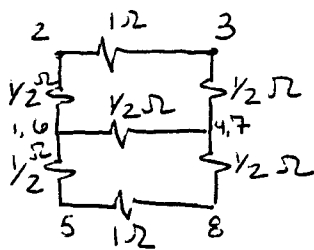
$$1\Omega // 1\Omega = \frac{1}{2}\Omega$$



combine the bottom 3 in series

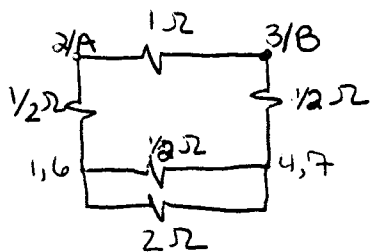


$$\frac{1}{2}\Omega + 1\Omega + \frac{1}{2}\Omega = 2\Omega$$

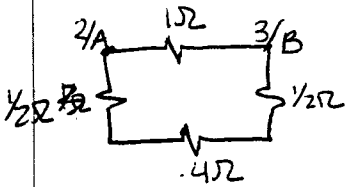2. a) (cont)


combine the resistors in parallel

$$\frac{1}{2}\Omega // 2\Omega = .4\Omega$$



combine the last series resistors

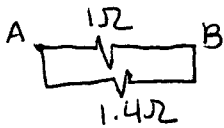
$$\frac{1}{2}\Omega + \frac{1}{2}\Omega + .4\Omega = 1.4\Omega$$



$$R_{AB} = 1\Omega // 1.4\Omega = \frac{7}{12}\Omega = .583\Omega = R_{AB}$$

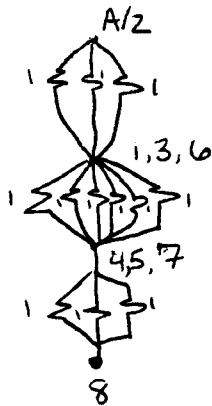b) from A → C


from symmetry it can be observed nodes 4, 5 + 7 are at the same potential as are 1, 3 + 6



combine the parallel resistors

$$1\Omega // 1\Omega // 1\Omega = \frac{1}{3}\Omega$$
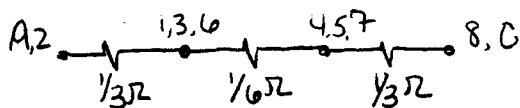
$$1\Omega // 1\Omega // 1\Omega // 1\Omega // 1\Omega // 1\Omega = \frac{1}{6}\Omega$$




$$R_{AC} = \frac{1}{3}\Omega + \frac{1}{6}\Omega + \frac{1}{3}\Omega = \frac{5}{6}\Omega = R_{AC}$$

2 cont.

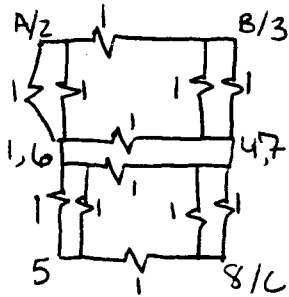
c) ~~R_{AB}~~ R_{BC}

from symmetry one can see 1+6 and 4+7 are at the same potential




combine parallel resistors


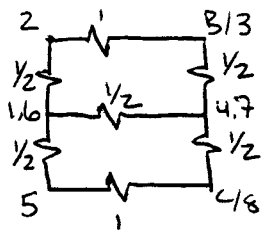
$$1\Omega // 1\Omega = \frac{1}{2}\Omega$$



combine series resistors

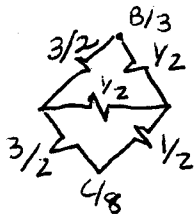

Using the Δ -Y transformation

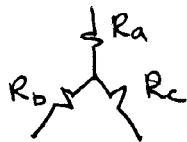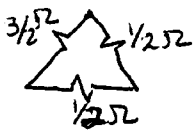


$$R_a = \frac{(3/2)(1/2)}{\frac{1}{2} + \frac{1}{2} + \frac{3}{2}} = \frac{3/4}{5/2} = \frac{3}{10}\Omega$$


$$R_b = \frac{(3/2)(1/2)}{\frac{1}{2} + \frac{1}{2} + \frac{3}{2}} = \frac{3}{10}\Omega$$

$$R_c = \frac{(1/2)(1/2)}{\frac{3}{2} + \frac{1}{2} + \frac{1}{2}} = \frac{1/4}{5/2} = \frac{1}{10}\Omega$$

2 c) cont

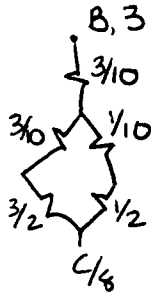


combine the series resistors

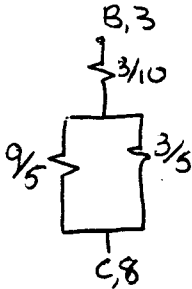

combine the parallel resistors
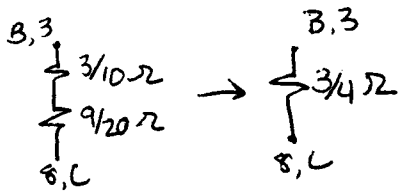
$$\frac{9}{5} \Omega \parallel \frac{3}{5} \Omega = \frac{9}{20}$$



$$R_{BC} = \frac{3}{4} \Omega$$

Set up nodal equations

$$\textcircled{2} \quad 3A = \left(\frac{V_B - V_A}{1\Omega} \right) + \left(\frac{V_6 - V_A}{\frac{1}{2}\Omega} \right)$$

$$\textcircled{3} \quad 3A = \left(\frac{V_4 - V_B}{\frac{1}{2}\Omega} \right) + \left(\frac{V_A - V_B}{1\Omega} \right)$$

$$\textcircled{8} \quad 0 = \left(\frac{V_6 - V_C}{\frac{3}{2}\Omega} \right) + \left(\frac{V_4 - V_C}{\frac{1}{2}\Omega} \right)$$

$$\textcircled{6} \quad 0 = \left(\frac{V_A - V_6}{\frac{1}{2}\Omega} \right) + \left(\frac{V_4 - V_6}{\frac{1}{2}\Omega} \right) + \left(\frac{V_8 - V_6}{\frac{2}{3}\Omega} \right)$$

$$\textcircled{4} \quad 0 = \left(\frac{V_B - V_4}{\frac{1}{2}\Omega} \right) + \left(\frac{V_6 - V_4}{\frac{1}{2}\Omega} \right) + \left(\frac{V_8 - V_4}{\frac{1}{2}\Omega} \right)$$

Set $V_8 = 0 = V_C$

$$\frac{-V_6}{\frac{3}{2}\Omega} = \frac{V_4}{\frac{1}{2}\Omega} \quad -V_6 = 3V_4$$

$$-3A = V_A(-1-2) + V_8 + 2V_6$$

$$3A = V_A \quad -3V_B - \frac{2}{3}V_6$$

$$0 = 2V_A$$

$$0 + V_6(-4 - \frac{2}{3} + \frac{2}{3})$$

$$V_B = -\frac{6}{11} V = -.545 V$$

$$V_{BC} = 1V + -.545V = \boxed{.454V} = V_{BC}$$