

ECE 124a/256c




# Power Distribution and Noise

---

Forrest Brewer
 
# Chip Power Requirements

- Large Scale Chip Power Phenomenal
  - Pentium 4 @ 0.13um has 85A Peak Package Current
  - @ 1.5V requires  $.15/85 = 1.8\text{m}\Omega$  total power network resistance
  - On-chip peak current risetime is  $<100\text{pS}$ !
- $I_{DD}$  changes on many time scales (DC to GHz)





# Power Distribution Problem

---

- Maintain stable voltage with low noise
  - Noise reduces reliability and lowers performance
- Average Power
  - Electromigration (grain activation)
- Peak Current
  - IR drop in Vdd and Gnd Bounce
- Provide current return paths for signals
  - Transmission line signalling noise reduction
  - Simultaneous output switching
- Consume minimal routing area and wire resources
  - still need *levels* of metalization




# Power Coupled Noise

---


- Droop due to IR drop, Ldi/dt noise and Supply Inductance
- Modulates behavior of Gates
  - Signalling Failure
  - Reduction of Noise Budget (Can you afford dynamic logic)
  - Reduction of System Performance
  - Increase in Power Dissipation
  - Reduction of device reliability
    - Hot Electrons
    - Oxide Damage
    - Electromigration

## Noise to Jitter Conversion

 

- Power noise can move the switching threshold of Gate
- Each repeater adds to the net jitter and skew at destination
 
# Noise to Jitter Conversion: Fundamentals




- Uncertainty of threshold reference ( $A$  from power supply noise) determines jitter
  - The buffer can switch (threshold) anywhere in this region ( $A'$ )
  - The slower the rise time the more opportunity is presented to PWR noise
- Amount of jitter directly proportional to the magnitude of the noise/ripple/GND bounce
  - $B$  (jitter) =  $A$  (noise) \*  $dt/dV$



 
# CMOS Power Loop is not local!

- Current from CMOS transistors comes from supply rails
  - BUT leaves via the output!
  - Load is accepted elsewhere on chip
- Not every output switches each cycle
  - Power loops are a function of state of the circuits!
- Upshot:
  - Cannot statically analyze local power requirements
  - Relatively little correlation between power and ground deviations in area bonded packaging





# Power Distribution Mesh

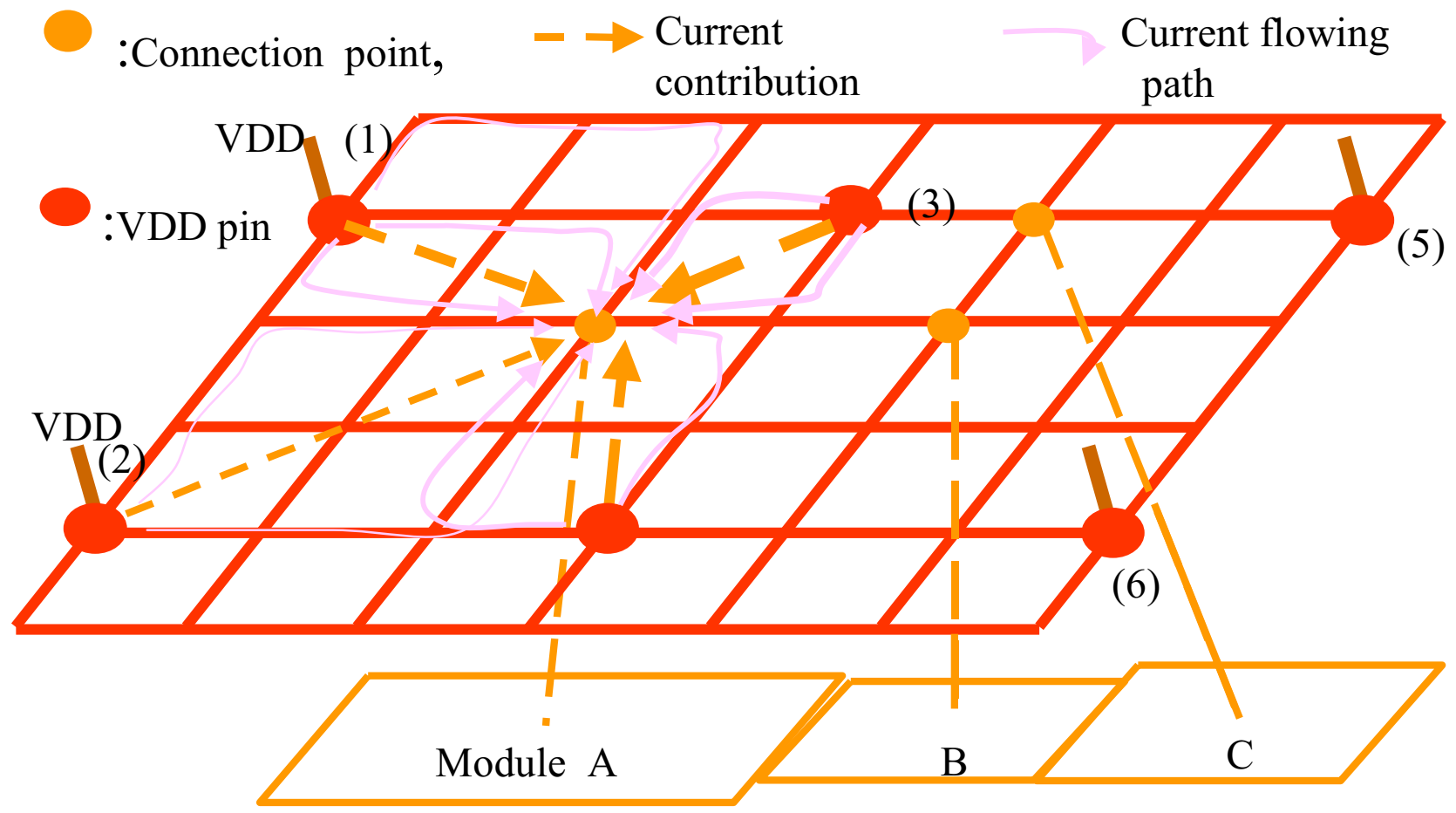


  
# Gate Behavior with Noise

- Effective propagation time can be longer or shorter due to noise
  - Delay is proportional to noise magnitude
  - Noise induced delay can be either positive or negative







# Logic Current Profile

---


- Assume triangle current profile:  $Q = C_{Load}V_{dd}$
- Peak Current  $i_{peak} \approx \frac{2Q}{1.8t_r} = \frac{1.1C_{Load}V_{dd}}{t_r}$
- Average Current  $i_{avg} = \frac{kC_{Load}V_{dd}}{t_{clk}}$
- K denotes the probability of switching (each direction)
  - K=.5 for a clock
  - K=.2 for a heavily used part of microprocessor
  - K=.1 or less for typical asic
  
# 6-> 64 Decoder Current Profile

- Count number of gates switching
- For Power/Ground modeling, count number switching each direction
- Add delays and superpose the current
- Find Peak from  $I_{sat}$  or  $\Delta Q$  given the delay:
  - $I_{peak} = \min(I_{sat}, 1.1\Delta Q/t_r)$



# Current Switching Profile

 



# IR Drop

---


$$V_{drop} = I_{peak} R_{distribution}$$

- IR drop is proportional to local peak current
  - Peak current reduced by parasitic bypass capacitance
  - Geometry to estimate  $R_{dist}$
  - Inductance usually ignored since small compared to IR
    - Capacitive coupling is very large, inductance is the inverse
    - Not true for low resistance busses (e.g. pad frame wiring)

$$V_{drop} = \sum_{path} I_i R_i + L_i \frac{dI_i}{dt}$$

- Local peak strongly affected by synchronization of clocking
  - Intentional skew (DAC '98 Vittal)


# Power Rail IR Drop

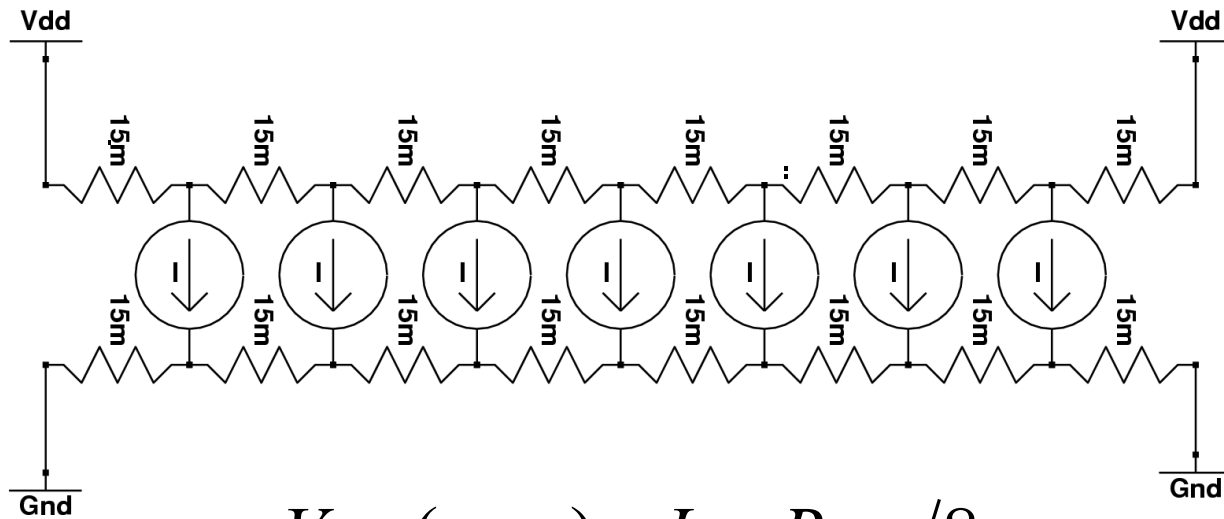

$$V_{drop}(\max) = I_{total} R_{total} / 8$$

- Distributed model of current loads and resistance
  - Supply from both sides, assume uniform load
  - Supply from one side, uniform: 4x as large =  $IR/2$

# Simple Chip Power Model

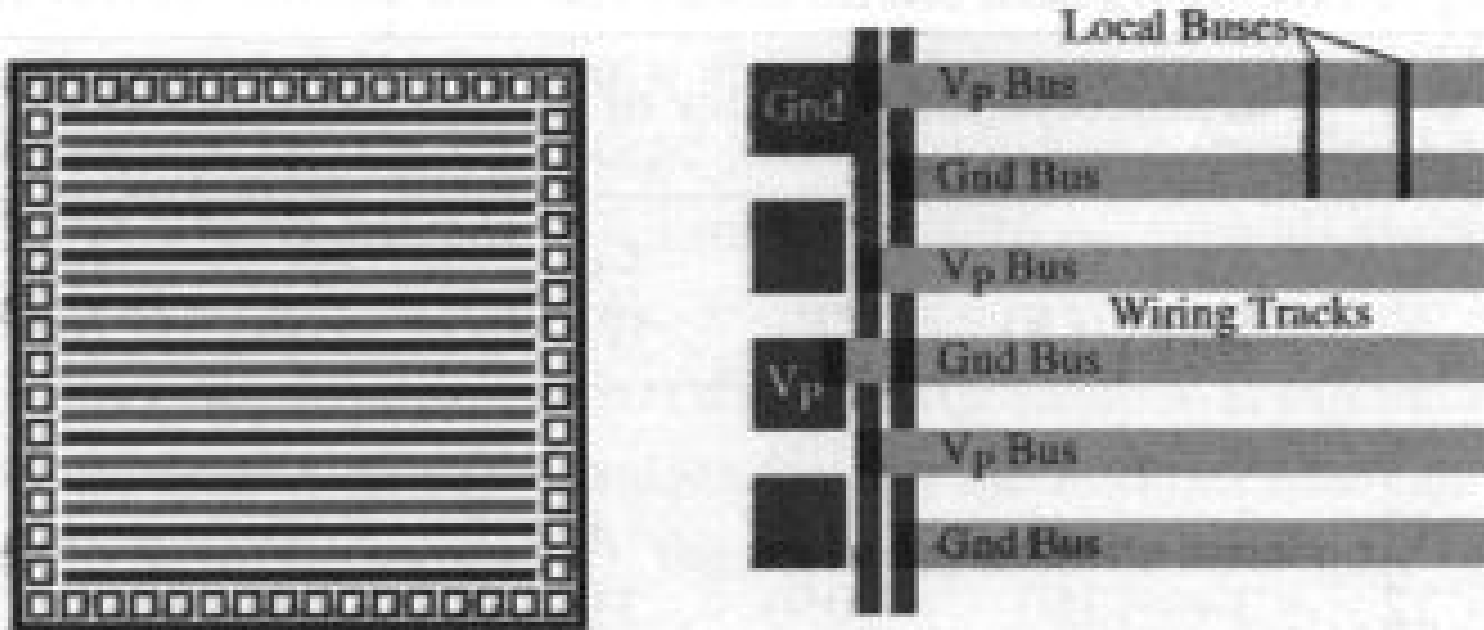

- $1\mu\text{m}$  Copper =  $0.029\Omega/\text{sq.}$ , via =  $1\Omega$ 
  - Wide bus:  $10\text{mm}$  long/ $25\mu\text{m}$  wide is  $400 \cdot 0.029 = 12\Omega$
  - Narrow bus:  $50\mu\text{m}$  long/ $2\mu\text{m}$  wide is  $25 \cdot 0.06 = 1.5\Omega$
- Typical Power Density ( $0.18\mu\text{m}$ )  $20,000$  gates/ $\text{mm}^2$ 
  - $J_{\text{peak}} = 0.54\text{A}/\text{mm}^2$   $J_{\text{avg}} = 100\text{mA}/\text{mm}^2$



## Simple Chip Power Model II

- Assuming uniform demand, each segment needs to supply a total current for the portion of area it covers (segment pitch times chip width)
  - Assume pitch =  $60\mu\text{m}$ , Source area is  $0.06\text{mm} \times 10\text{mm} = 0.6\text{mm}^2$ 
    - Power rail drop is  $IR/8 = 0.54\text{A} \times 0.6\text{mm}^2 \times 12\Omega/8 = 0.49\text{V}$ !, Ground Drop is similar... Note that we have used 86% of the copper on the level...
    - To get a barely acceptable drop, we'd need 2 full layers of metal dedicated to power and ground distribution.
    - In practice, the current peak is filtered by parasitic bypass of the non-switching gates (and designed-in bypass) which lowers the peak current






# Bypass Calculation I

---

- Essential idea: Local capacitor supplies power for peak to provide lower frequency requirement to next stage of power network
- $Q = CV = It$  so:  $C = t \cdot I / V$
- For Impulse of Total charge  $q$ , we have:  $C = q / \Delta V$ 
  - E.G. for  $I = 3A$ ,  $t = 1nS$ ,  $\Delta V = 0.1V \Rightarrow C = 30nF$
  - E.G. for  $q = 120fC$ ,  $\Delta V = 0.1V \Rightarrow C = 1.2pF$

# Parasitic Bypass

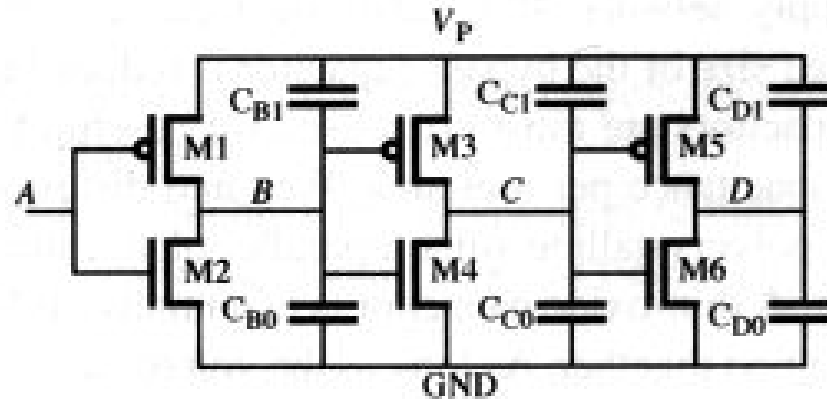

- The majority of gates in a circuit do not switch on a given cycle—
  - Others provide low-resistance (few hundred ohms) path from gates (outputs) to one of the supply rails
  - Roughly 40% of total gate capacitance in given area is connected to each supply rail as bypass
  - (0.18 $\mu$ m) 20,000 gates/mm<sup>2</sup>, typical gate has 8-12 fF => 200pF/mm<sup>2</sup> local bypass or 20nF/1cm<sup>2</sup> die...



# Parasitic Bypass Estimation

- Given the relatively large available bypass– how to estimate?
  - Could Simulate – expensive for large systems
  - Despite dynamic nature of the capacitances, for a subsystem the average capacitance are not strong functions of state
- Good Estimates: (2006 Nassif, Agarwal, Acar) (few percent)
  - For static portions of logic:
  - FET Capacitances basically proportional to width
  - Parasitic Capacitances in stacked FETs divide the voltage swing
  - 0.18um technology, standard cells  $\alpha_n=4\text{fF}/\mu\text{m}$   $\alpha_p=1.2\text{fF}/\mu\text{m}$
  - For each FET  $i$ , with width  $W_i$  included in a stack of Height  $H_i$

$$C = \alpha_n \sum_{i \in N} \frac{W_i}{H_i} + \alpha_p \sum_{i \in P} \frac{W_i}{H_i}$$



## Simple Model (Reprise)

- Parasitic Bypass lowers the required peak current
  - For our model  $C_{\text{load}}/\text{mm}^2 = 20\text{pF}/\text{mm}^2$  ( $I_p=0.56\text{A}/\text{mm}^2$ )
  - We have  $200\text{pF}/\text{mm}^2$  bypass so expect 10% supply deviations =  $0.18\text{V}$  on *both* Vdd and Ground rails + IR drop
  - New IR drop is average current =  $100\text{mA}/\text{mm}^2$  or 5.6x smaller
  - Total drop =  $0.18\text{V} + 0.49/5.6 = 0.27\text{V}$ ... a bit perilous, but survivable
- Note: Doubling supply metal will only reduce noise to  $0.23\text{V}$
- Doubling Capacitance (adding designed-in local bypass) will lower it to  $0.18\text{V}$

Moral– Bypass whenever possible



# Metal Migration

---

- Al ( $2.9\mu\Omega\text{cm}$  M.P. 660 C)
  - $1\text{mA}/\mu\text{m}^2$  at 80C is average current limit for 10 year MTTF
  - Current density decreases rapidly with temperature
- Cu ( $1.7\mu\Omega\text{cm}$  M.P. 1060 C)
  - $10\text{mA}/\mu\text{m}^2$  at 100C or better (depends on fabrication quality)
  - Density decreases with temperature, but much slower over practical Silicon operation temperatures <120C
- Find Average current through wire – check cross section
  - Be wary of Via's!! Typical cross-section 20-40% of minimal wire.




# Off Chip Power Noise

---

Packaging, Board Distribution and Power Supply Issues

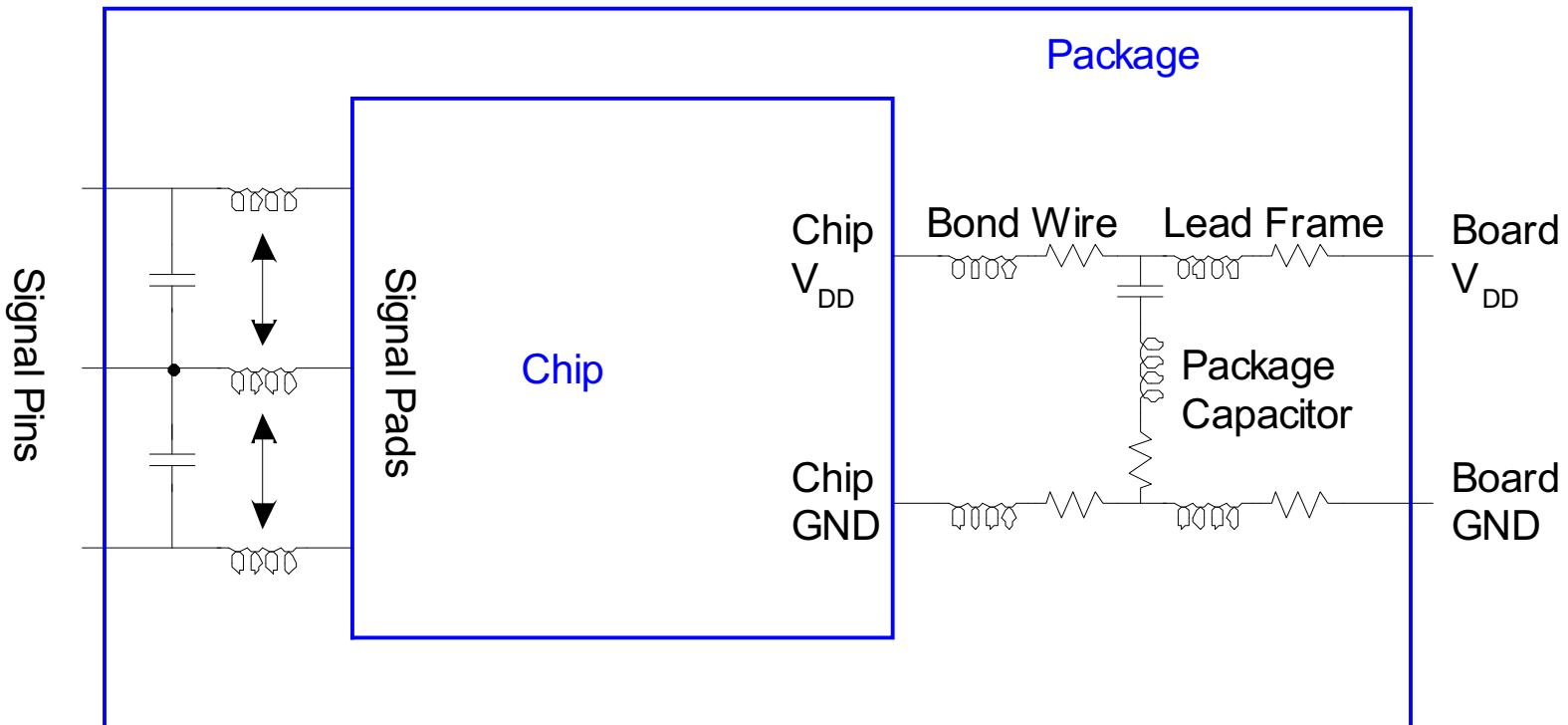
# Package Parasitics

- ❑ Use many  $V_{DD}$ , GND in parallel
  - Inductance,  $di/dt$ , Impedance Control


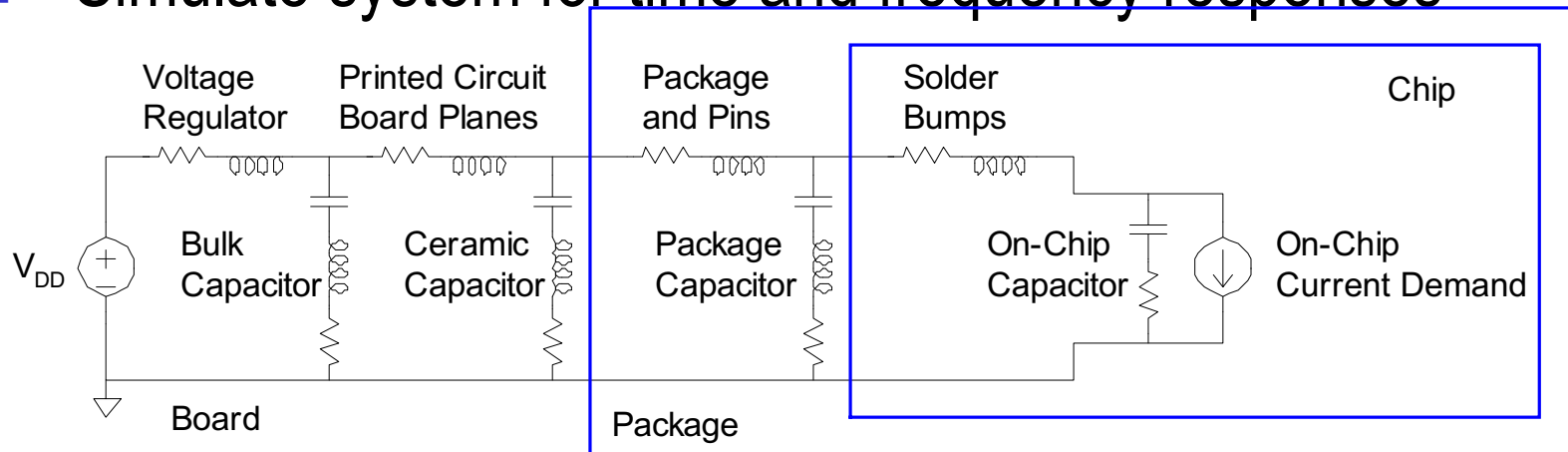
# Power System Model


- Power comes from regulator on system board
  - Board and package add parasitic R and L
  - Bypass capacitors help stabilize supply voltage
  - But capacitors also have parasitic R and L
- Simulate system for time and frequency responses





 
# Imperfect Bypass Capacitors

- Even with the addition of bypass capacitance there are still sources of inductance in the current loop which can cause power supply noise.
  - Plane inductance
    - Determined by the shape of the plane (pH/sq) and dielectric thickness
    - E.g. 15cm radius to 2cm radius = 70pH
  - Bypass capacitor parasitics
  - Capacitor Mounting
    - Solder land, trace to via, ***\*via itself\****



 
# Bypass Capacitors

- Need low supply impedance at all frequencies
- Ideal capacitors have impedance decreasing with  $\omega$
- Real capacitors have parasitic R and L
  - Leads to resonant frequency of capacitor  $\omega_{cap} = 1 / \sqrt{LC}$



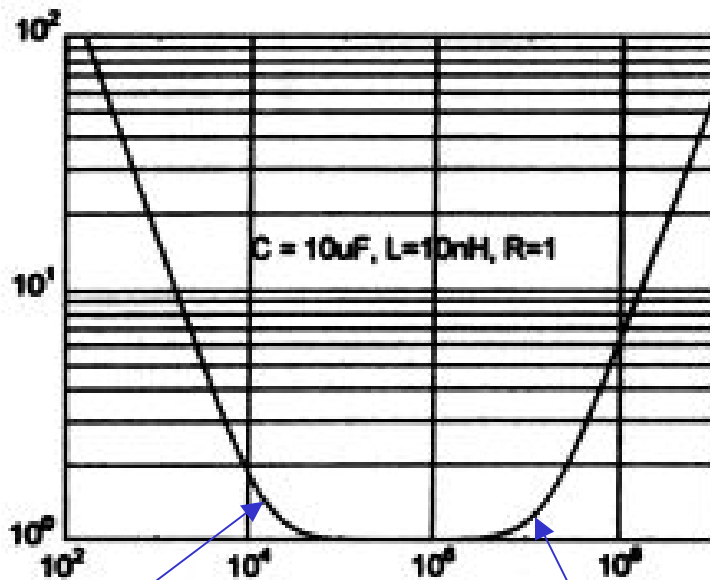
# Chip Bypass Capacitors

- Series Resistance can create alternative breaks:
  - Often need to parallel capacitors to achieve lower inductance



$$\omega_{RC} = 1 / RC$$


$$\omega_{LR} = R / L$$

 

$$\omega_{cap} = 1 / \sqrt{LC}$$

 
# Frequency Response

- Use multiple capacitors in parallel
  - Large capacitors near regulator have low impedance at low frequencies
  - also low resonant frequency (ineffective at high freq)
  - Small capacitors near and on chip have low impedance at high frequencies
- Choose caps to get low impedance at all frequencies


 
# Aggregate Bypass Network

- Simulation is needed to view network impedance profile
  - Should cover frequencies from 100 kHz to 300MHz (Board/Package)
  - Impedance should be low and flat over this range



# Board Vias – Parallel Connection



## ■ Mounted Capacitor Parasitics

■ $L_C$	Capacitor self-inductance	0.7nH - 1.2nH
■ $L_{LD}, L_{LC}$	Solder land inductance of device and cap	0.1nH - 0.4nH
■ $L_P$	Power plane inductance	0.03nH - 0.4nH
■ $L_{VP}$	Via pair inductance	<b>0.3nH - 3.2nH</b>

- Via parasitic can be biggest contributor
- Board thickness is critical factor if caps on the bottom
  - 62mil finished thickness -- typical  $L_{VP} = 1.5nH$
  - 127mil finished thickness -- typical  $L_{VP} = 3.2nH$
 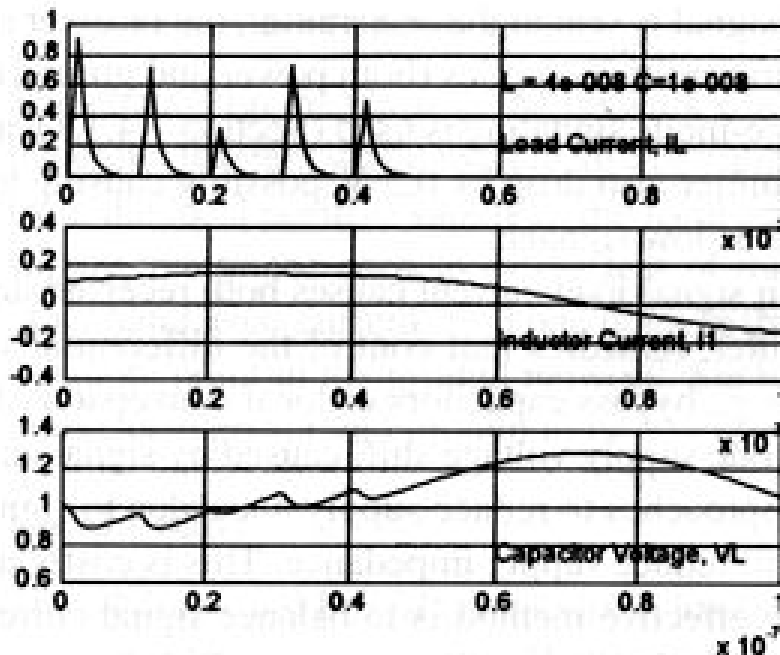
# Power Supply Inductance

- Average current through inductor subject to low frequency variations
  - Must control excursions of voltage across the capacitor
  - Inductor does not see high frequency components as long as capacitor can supply bulk of current
  - MUST stay away from resonant frequency of LC circuit



## Bypass Reprise: LC step response

- Low Frequency steps in current trigger resonant response

$$V_c = Q_L / C \quad V_L = L \frac{dI(t)}{dt} \quad V_c = V_L \Rightarrow V_c = LC \frac{d^2 V_c}{dt^2}$$

- Solution:  $V_c(t) = \frac{I_{avg}}{\omega_c C} \sin(\omega_c t) + V_{dd}$

- Solving for C given restriction on V:

$$C > L \left( \frac{I_{avg}}{V_{droop}} \right)^2$$






# Basic Bypass Rules

---

- Use small capacitor packages
  - Parasitic L is proportional to pkg. Size and aspect ratio
- Use largest value subject to resonant point
  - L is dominated by pkg, so choose C at limit of frequency
- Connect cap lands directly to planes
- NEVER share cap vias
- Keep trace between land and via short!!
  - Benefit of small package is lost otherwise

# Spy-Hole vs. Backside Measurements

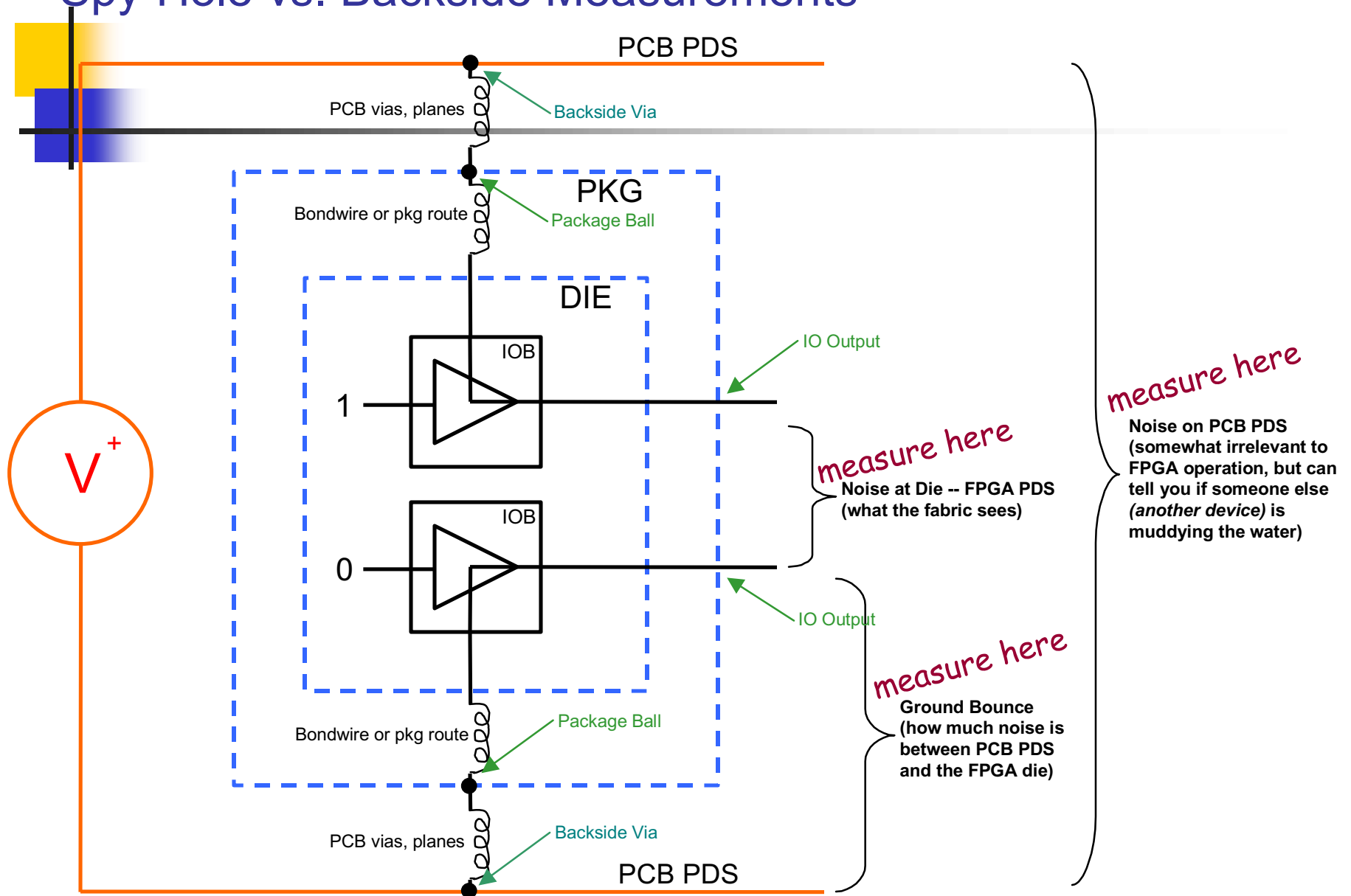



# Simultaneous Switching Noise

- Issue: Modern packages have hundreds of I/O pins
  - Each pin is driving 50-60Ω tmline on pc-board
  - Rise/fall time of line must be smaller than Bandwidth/3

- Potential for very large  $dI/dt$  spike if synchronized:

$$\frac{dI}{dt} = \frac{V_{swing}}{50\Omega * 1.8t_r} \approx \frac{28mA}{t_r} \quad L < \frac{V_{droop}}{dI / dt} = t_r \frac{V_{droop}}{N_{pins} 28mA}$$

- For 333MHz DDR – 80pins at  $t_r=0.5nS$  (50%):
  - 4.5GA/s => at 0.3V drop, need 63pH power supply inductance
- Solution: mixture of on-chip bypass in the pad drivers and lots of connections to power and ground to lower inductance